
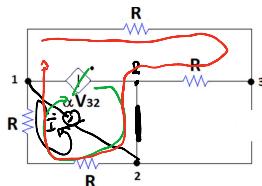


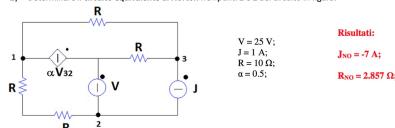
1) Determinare il circuito equivalente di Norton fra i punti 1 e 2 del circuito in figura.



$$\left\{ \begin{array}{l} V_{s2} = R I_x \\ 4R I_x + 2R \times V_{32} - 2RI_p = 0 \\ 4R I_x + 2R^2 \alpha I_x - 2RI_p = 0 \\ I_x = \frac{2RI_p}{4R + 2R^2 \alpha} = \frac{2I_p}{4 + 2R\alpha} \end{array} \right.$$

$$V_p = 2RI_p - 2R I_x - 2R^2 \alpha I_x = 2RI_p - \frac{4RI_p}{4 + 2R\alpha} - \frac{4R^2 \alpha I_p}{4 + 2R\alpha}$$

$$R_{NO} = \frac{V_p}{I_p} = 2R - \frac{4R}{4 + 2R\alpha} - \frac{4R^2 \alpha}{4 + 2R\alpha} = 2,857 \Omega$$

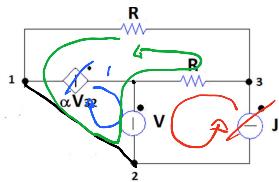 I_{NO} 

$$\left\{ \begin{array}{l} 2R I_x - R J = V \\ V_{s2} = R \delta + V - R I_x \end{array} \right. \quad I_x = \frac{V + RF}{2R}$$



$$V_{s2} = R \delta + V - \frac{V}{2} - \frac{RJ}{2}$$

$$V_{s2} = \frac{RF}{2} + \frac{V}{2} = 17,5 \text{ V}$$

$$I_{NO} = -\alpha V_{s2} + I_x = -8,75 + 1,75 = -7 \text{ A}$$

ES 2

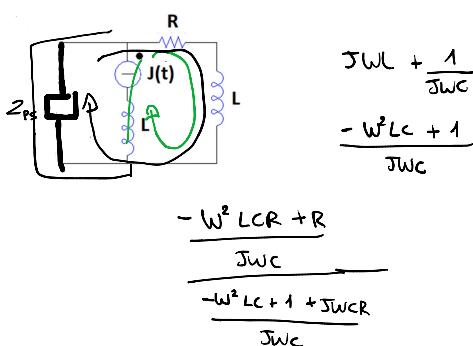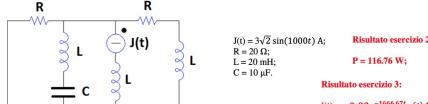2) Determinare la potenza attiva erogata dal generatore di corrente nel circuito in figura.



$$\frac{JWL + \frac{1}{JWC}}{JWC} - \frac{W^2 LC + 1}{JWC}$$

$$\frac{-W^2 LCR + R}{JWC} \frac{-W^2 LC + 1 + JWCR}{JWC}$$

$$Z_{es} = \frac{-W^2 LCR + R}{-W^2 LC + 1 + JWCR} = 18i,82 - 4,73$$

$$Z_{ps} = \frac{-\omega^2 L C R + R}{-\omega^2 L C + 1 + j \omega L R} = 181.82 - 4.73$$

$$(R + Z_{ps} + j\omega L) I_x + j(R + j\omega L) = 0$$


$$I_x = \frac{j(R + j\omega L)}{R + Z_{ps} + j\omega L} = -1.8650 - 0.8105j$$

$$V_S = -I_x Z_{ps} + 3j\omega L = 38.3096 + 66.4885j$$

$$P_S = V_S \cdot S^* \approx 116.76 \text{ W}$$


ES 3

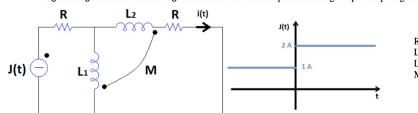3) Determinare l'andamento temporale della corrente $i(t)$ per $-\infty < t < +\infty$, dato l'andamento di corrente erogato dal generatore come da figura a destra. Il circuito è ipotizzato a regime per tempi negativi.




$R = 10 \Omega$;
 $L_1 = 10 \text{ mH}$;
 $L_2 = 20 \text{ mH}$;
 $M = 12 \text{ mH}$

SOLUZIONE DEGLI EFFETTI

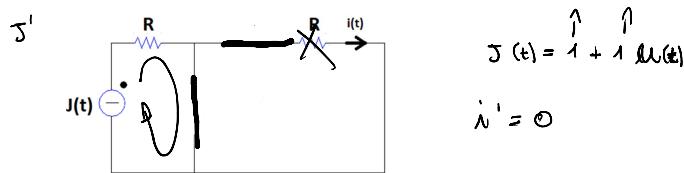

$$J(t) = 1 + 1 \sin(\omega t)$$

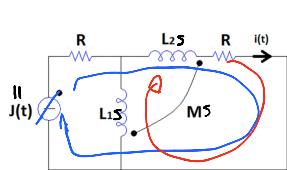

$$(J(s) + I_x) L_2 s - M s I_x + R(J(s) + I_x) + I_x L_1 s - M s (I_x + J(s)) = 0$$

$$I_x(s) (L_2 s + M s + R + L_1 s - M s) + J(s) L_2 s + R J(s) - M s J(s) = 0$$

$$I_x = \frac{L_2 + \frac{R}{s} - M}{R + s(L_2 + L_1)}$$

$$i''(s) = \frac{L_2 + \frac{R}{s} - M}{R + s(L_2 + L_1)} + \frac{1}{s} = \frac{L_2 s + R - M s + R + s L_2 - 2 M s + s L_1}{s(R + s(-2M + L_1 + L_2))} = \frac{2R + s(2L_2 + L_1 - 3M)}{s(R + s(-2M + L_1 + L_2))}$$


$$s_1 = 0 \quad s_2 = -1666.67$$

$$A_1 = \lim_{s \rightarrow 0}$$

$$A_2 = \lim_{s \rightarrow s_2} \frac{3333.33 + s(2,33)}{-1666.67} = 0,33$$

ES 4

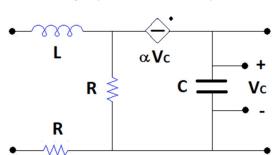4) Determinare la rappresentazione a parametri T della rete a due porte indicata in figura. Si ipotizzi che il circuito si trovi a regime periodico sinusoidale con pulsazione ω .




$R = 10 \Omega$;
 $L = 10 \text{ mH}$;
 $C = 50 \mu\text{F}$;
 $\alpha = 0.8$;
 $\omega = 1000 \text{ rad/sec}$.


Risultati:

$$T = \begin{bmatrix} -0.1 + 0.7j & 10 + 10j \\ 0.02 + 0.05j & 1 \end{bmatrix}$$
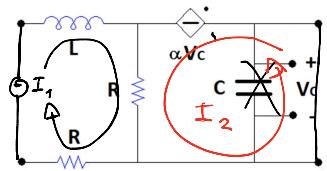
$$\begin{cases} V_1 = A V_2 + B (-I_2) \\ I_1 = C V_2 + D (-I_2) \end{cases} \quad -I_2 = \frac{I_1}{D} - \cancel{\frac{C}{D} V_2} \quad -D I_2 = I_1$$


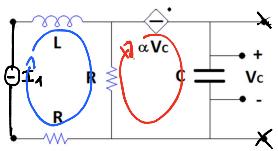
$$\left\{ \begin{array}{l} V_c = 0 \\ I_1 = -I_2 \Rightarrow D = 1 \\ V_1 = (2R + jWL) - I_2 + R I_2 = (R + jWL) - I_2 \Rightarrow B = 10 + 10j8 \end{array} \right.$$



$$\left\{ \begin{array}{l} V_c = \frac{1}{j\omega C} I_x \\ \alpha V_c = -R I_1 + \frac{I_x}{j\omega C} + R I_x \\ I_x \left(\frac{\gamma-1}{j\omega C} - R \right) = -R I_1 \quad I_x = \frac{-R}{\frac{\gamma-1}{j\omega C} - R} \quad I_1 = \gamma I_1 = (0,862 + 0,3448j) I_1 \end{array} \right.$$

$$V_2 = \frac{\gamma I_1}{j\omega C} \quad I_1 = \frac{j\omega C}{\gamma} V_2$$

$$C = 0,02 + 0,05j$$

$$\begin{aligned} V_1 &= (2R + jWL) I_1 - R \gamma I_1 = (2R + jWL) \frac{j\omega C}{\gamma} V_2 - R j\omega C V_2 \\ V_1 &= V_2 \left(\frac{2R j\omega C}{\gamma} + -\frac{\omega^2 LC}{\gamma} - R j\omega C \right) \end{aligned}$$