
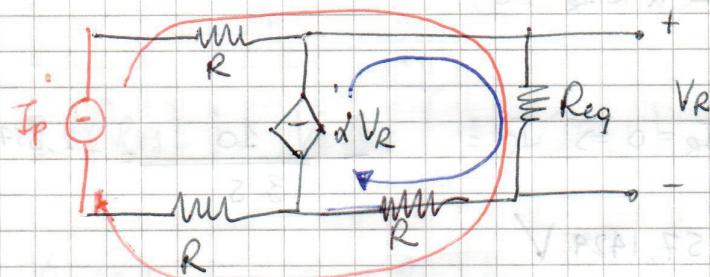
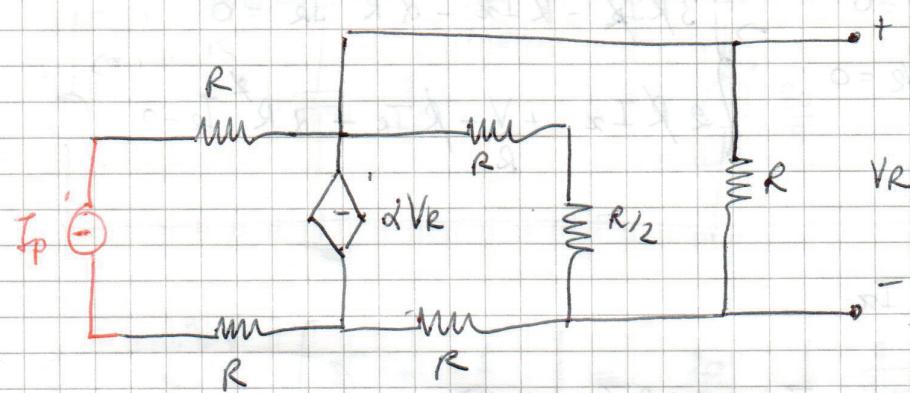


Soluzione compito 22 Luglio 2020

③ R_{TH}

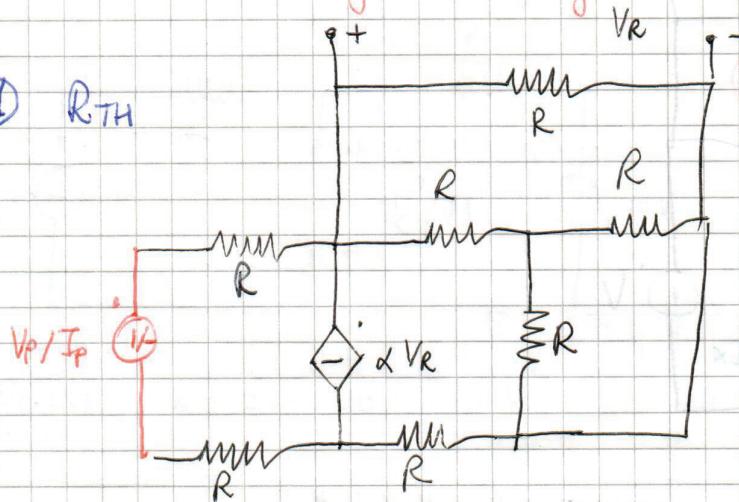


$$R_{eq} = \frac{3}{2} R // R = \frac{\frac{3}{2} R^2}{\frac{5}{2} R} = \frac{3}{5} R = 6 \Omega$$

$$VR = (\alpha VR + I_p) \cdot R_{eq} \Rightarrow VR (1 - \alpha R_{eq}) = R_{eq} I_p \Rightarrow$$

$$\Rightarrow VR = \frac{R_{eq}}{1 - \alpha R_{eq}} I_p = \frac{6}{1 - \frac{1}{2} \cdot \frac{6}{5}} I_p = \frac{6}{\frac{7}{10}} I_p = \frac{60}{7} I_p$$
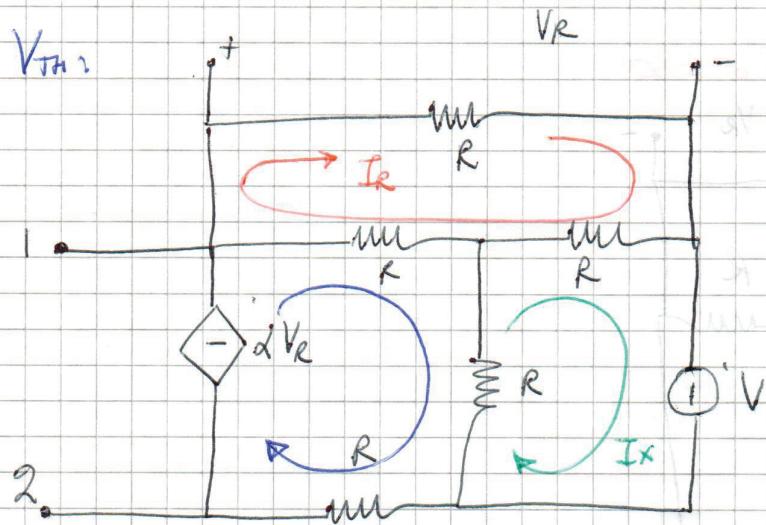
$$R_{TH} = \frac{V_p}{I_p} = \frac{R I_p + VR + R I_p + R I_p + R \alpha VR}{I_p} = \frac{30 + \frac{60}{7} + \frac{30}{7}}{I_p} = \frac{300}{7} I_p = \frac{300}{7} = 42.8571 \Omega$$






$$\begin{cases} 3RI_R - RI_x - R\alpha V_R = 0 \\ 2RI_x + V - RI_R - R\alpha V_R = 0 \\ V_R = R I_R \end{cases} \Rightarrow \begin{cases} 3RI_R - RI_x - R^2 I_R = 0 \\ 2RI_x + V - RI_R - R^2 I_R = 0 \\ V_R = R I_R \end{cases} \Rightarrow$$

$$\Rightarrow \begin{cases} 3I_R - \alpha R I_R = I_x \\ 6I_R + \frac{V}{R} - 2\alpha R I_R - I_R - \alpha R I_R = 0 \end{cases} \Rightarrow$$


$$\Rightarrow 6I_R + 10 - I_R - I_R - 0.5I_R = 0 \Rightarrow I_R = -\frac{10}{3.5} = -2.8571 A$$

$$V_{TH} = R I_R + V + R \cdot \alpha \cdot R I_R = 57.1429 V$$

② Risolviamo con mnr. effetti

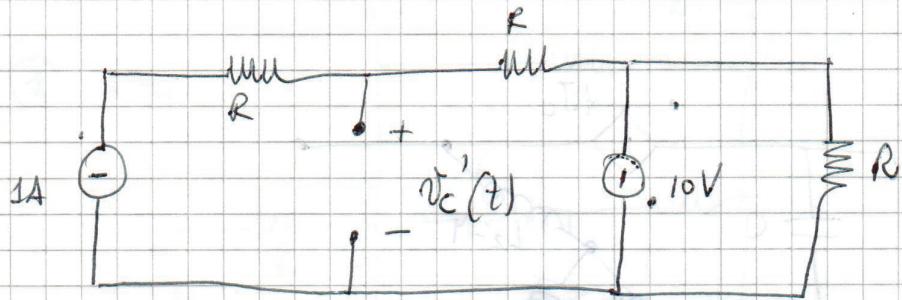
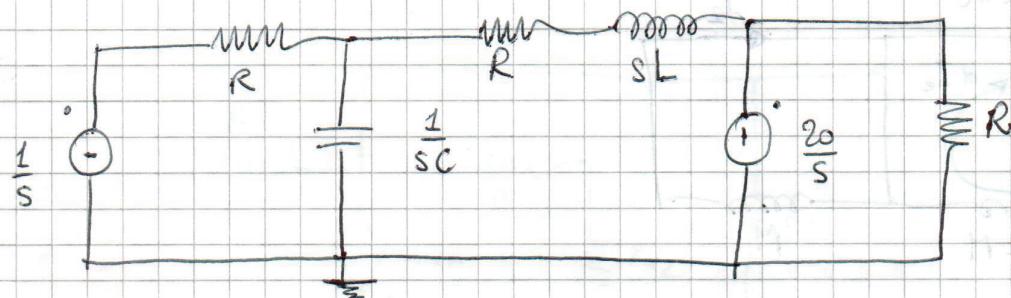
$$V_c'(t) = R \cdot 1 - 10 = 15 \text{ V}$$



$$\frac{1}{s} = V_c(s) \cdot \left[sC + \frac{1}{R+sL} \right] - \frac{20}{s} \cdot \left[\frac{1}{R+sL} \right] \Rightarrow$$

$$\Rightarrow 1(R+sL) = V_c(s) \left[s^2 C (R+sL) + 1 \right] - 20 \Rightarrow$$

$$\Rightarrow V_c(s) = \frac{20 + R + sL}{s(s^2 \cdot LC + s \cdot RC + 1)} = \frac{0.01s + 45}{s(10^{-6}s^2 + 0.0025s + 1)}$$

$$V_c(t) = \left(8.33 e^{-2000t} - 53.33 e^{-500t} + 45 \right) u(t)$$

$$V_c(t) = 15 + \left(8.33 e^{-2000t} - 53.33 e^{-500t} + 45 \right) u(t)$$



$$V_c(0^+) = V_c(0^+) = 15 \text{ V} \quad V_c(+\infty) = 60 \text{ V}$$

$$V_c(+\infty) = R \cdot I(+\infty) + E(+\infty) = 25 \cdot 2 + 10 = 60 \text{ V} \quad \text{OK!}$$

$$\textcircled{3} \quad \dot{V}_1 = \bar{h}_{11} \dot{I}_1 + \bar{h}_{12} \dot{V}_2$$

$$\dot{I}_2 = \bar{h}_{21} \dot{I}_1 + \bar{h}_{22} \dot{V}_2$$

$$\textcircled{1} \quad \dot{V}_2 = 0$$

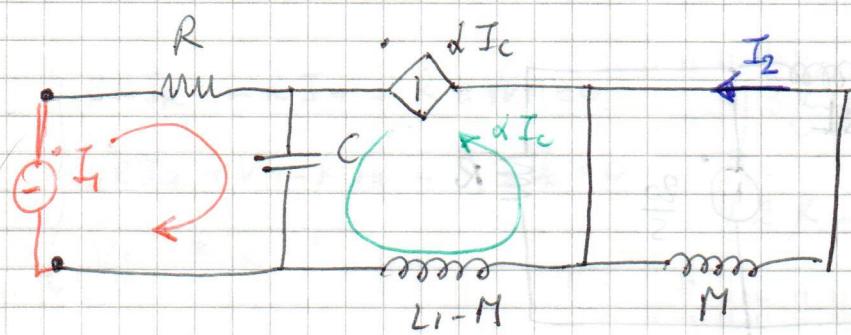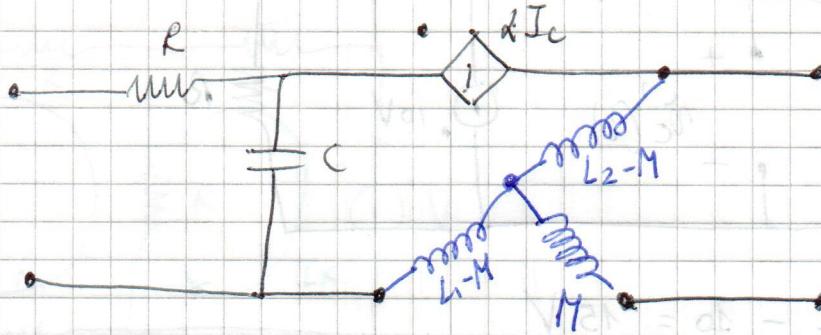


$$\dot{I}_2 = \phi \quad (\text{perché } M \text{ è parallelo ad un corto circuito})$$

$$\dot{I}_c = \dot{I}_1 + \alpha \dot{I}_c \Rightarrow (1 - \alpha) \dot{I}_c = \dot{I}_1 \Rightarrow \dot{I}_c = \frac{1}{1 - \alpha} \dot{I}_1 \Rightarrow \boxed{\bar{h}_{11} = 0}$$

$$\dot{V}_1 = R \dot{I}_1 + \frac{1}{j\omega C} \dot{I}_c = \left(R + \frac{1}{j\omega C} \cdot \frac{1}{1 - \alpha} \right) \dot{I}_1 = \boxed{10 - 12.11j}$$

$$\textcircled{2} \quad \dot{I}_1 = 0$$

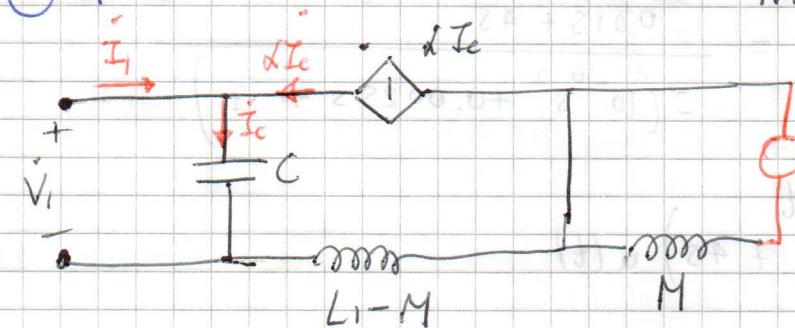

$$\dot{I}_c = \alpha \dot{I}_c \Rightarrow \dot{I}_c = \phi \Rightarrow \dot{V}_1 = \frac{1}{j\omega C} \cdot \dot{I}_c = \phi$$

$$\dot{V}_2 = j\omega M \cdot \dot{I}_2 \Rightarrow \bar{h}_{22} = \frac{1}{j\omega M} = -0.0667j$$

$$h = \begin{bmatrix} 10 - 11.11j & 0 \\ 0 & -0.0667j \end{bmatrix} \quad \dot{I}_1 = \frac{\dot{V}_1}{\bar{h}_{11}} = 2.2376 + 2.4862j$$

$$\dot{I}_c = 3.7165e^{j0.838} \Rightarrow \boxed{i_c(t) = 3.7165\sqrt{2} \sin(100\pi t + 0.838)}$$