

COMPITI D'ESAME SVOLTI DI


ELETTRONICA MAGISTRALE

DAL 2014 AL 2016

SIPAN AHMED

Spero vi facciano comodo!

1) 16/02/2016

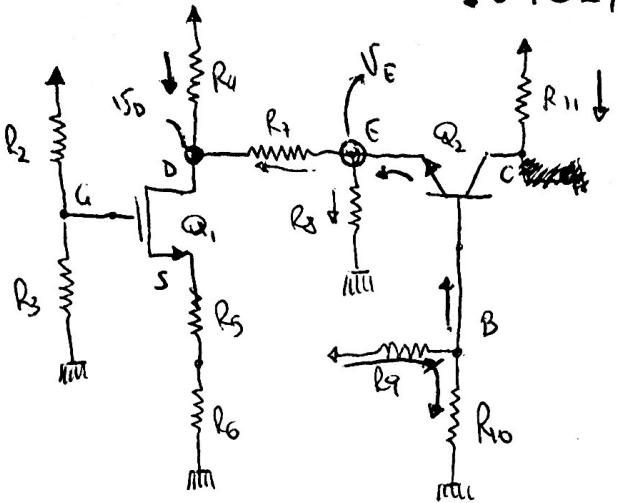

$$\bullet I_B = \frac{V_{CC} - V_D}{R_4} = 2 \cdot 10^{-4} \text{ A}$$

$$\bullet I_S = \frac{V_E}{R_8} = 2 \cdot 10^{-4} \text{ A}$$

$$\bullet I_T = \frac{V_E - V_D}{R_4} = 1.8 \text{ mA}$$

$$\bullet I_E = I_S + I_T = 2 \text{ mA}$$

$$\bullet V_B = V_{CC} \cdot \frac{R_{10}}{R_9 + R_{10}}$$

\rightarrow Si suppone che sia in ZONA ATTIVA DIRETTA : $I_C \gg I_B$

$$I_C = I_E$$

$$\bullet V_C = V_{CC} - R_{11} I_C = 13 \text{ V}$$

DIRESTRO CTE $V_{CE} > V_{CE, SAT} \Rightarrow 5 \text{ V} > 0.2 \text{ V} \rightarrow \text{OK}$

Quindi $f_{FE} = 290 \quad f_{pe} = 300 \quad f_{ce} = 6.8 \text{ k}\Omega$

$$\bullet I_B = \frac{I_C}{h_{FE}} = 6.8965 \mu\text{A}$$

$$\bullet V_{BE} = V_B - V_E \Rightarrow V_B = V_E + V_{BE} = 8.7 \text{ V}$$

$$\bullet I_Q = \frac{V_{CC} - V_B}{R_9} = 5 \cdot 10^{-5} \text{ A} = 50 \mu\text{A}$$

$$\bullet I_{IO} = I_Q - I_B = 43.1035 \mu\text{A}$$

$$\rightarrow R_{10} = \frac{V_B}{I_{IO}} = 201.839.7578 \text{ } \Omega$$

$$I_0 = I_4 + I_7 = 2mA$$

$$\bullet \quad I_D = I_S$$

$$U_S = (R_S + R_0) I_S = 3V$$

$$\frac{F_a}{R_{a,b}} = \frac{F_c}{R_{c,b}}$$

$$J_{CS} = U_T + \sqrt{\frac{I_0}{K}} = 3 \text{ V}$$

VERIFICO LA SATURAZIONE

$$\cdot U_{as} = U_a - U_s \Rightarrow U_a = U_{as} + U_s = 6 \text{ V}$$

$$\bullet \quad I_3 = \frac{V_a}{R_3} = 60 \mu A$$

$$f_2 = \frac{V_{CC} - 15\text{e}}{I_3} = 200\,000 \text{ Hz}$$

VERIFIED 1A SATURDAY

$$U_{DS} > U_{ES} - V_T \rightarrow 6.1 > 2 \quad \text{OK}$$

PUNTI DI RIPOSO

Q

$$h_{FE} = 300 \quad h_{FE} = 290 \quad h_{FE} = k_1 \cdot k_2 \quad I_C = 2 \text{ mA} \quad V_{DS} = 5 \text{ V}$$

. Q₁

$$I_o = 2 \text{ mA}$$


$$S_{\text{PC}} = 6 \cdot 1 \quad \checkmark$$

$$g_m = 2k |(\nu_{as} - \nu_r)| = 2 \cdot 10^{-3} \frac{A}{V}$$

2)

16/02/2016

3)

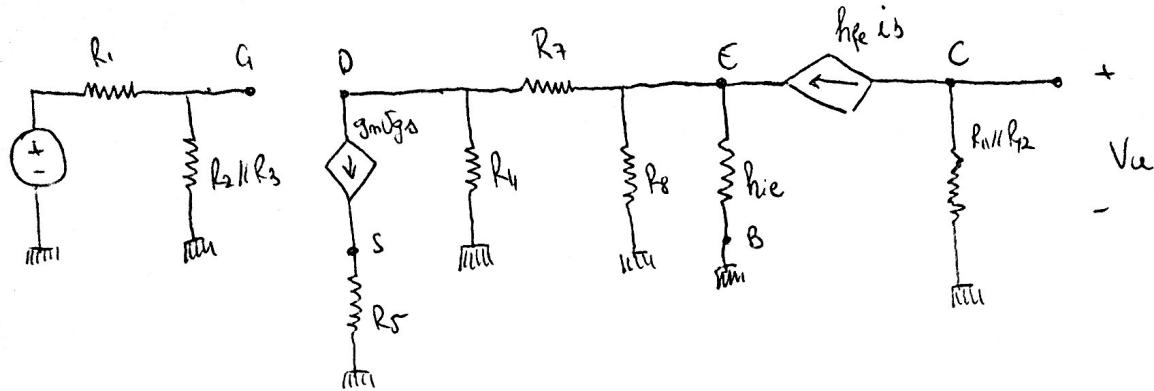

$$\cdot V_u = -h_{fe} i_b (R_u \parallel R_2)$$

$$\cdot i_p = \frac{h_{fe} i_b (R_u + R_f)}{R_u + R_f + R_p} - \frac{g_m V_{gs}}{R_u + R_f + R_p} R_u$$

$$\cdot i_p = h_{fe} i_b R_{eq_1} - g_m V_{gs} R_{eq_2}$$

$$\cdot i_b = i_p \cdot \frac{R_8}{R_8 + \frac{h_{ie}}{h_{fe} + 1}} = i_p \cdot R_{eq_3}$$

$$\cdot \frac{i_b}{R_{eq_3}} = h_{fe} R_{eq_1} i_b - g_m V_{gs} R_{eq_2}$$

$$\cdot i_b \left(\frac{1}{R_{eq_3}} - h_{fe} R_{eq_1} \right) = - g_m V_{gs} R_{eq_2}$$



$$\cdot i_b = - \frac{g_m R_{eq_2}}{\frac{1}{R_{eq_3}} - h_{fe} R_{eq_1}} \cdot V_{gs}$$

$$\cdot V_{gs} = V_g - V_d = V_g - g_m V_{gs} R_5 \Rightarrow V_{gs} = \frac{V_g}{1 + g_m R_5}$$

$$\cdot V_g = V_i \cdot \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3}$$

$$\cdot \frac{V_u}{V_i} = h_{fe} (R_u \parallel R_3) \cdot \frac{g_m R_{eq_2}}{\frac{1}{R_{eq_3}} - h_{fe} R_{eq_1}} \cdot \frac{1}{1 + g_m R_5} \cdot \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3}$$

negativo

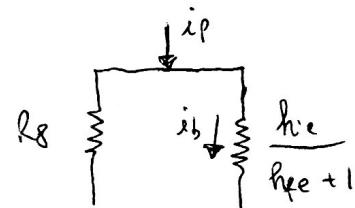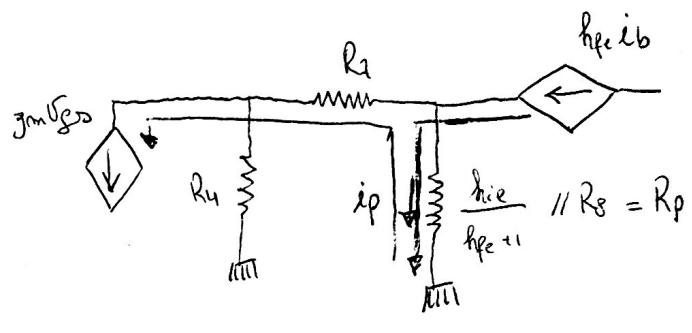

$$\begin{aligned} \cdot R_p &= 15.9404 \Omega \\ \cdot R_{eq_1} &= 0.9997 \Omega \\ \cdot R_{eq_2} &= 0.99062 \Omega \\ \cdot R_{eq_3} &= 0.9996 \Omega \end{aligned}$$

$$\begin{aligned} \cdot R_u \parallel R_2 &= 2222.2222 \Omega \\ \cdot R_2 \parallel R_3 &= 66666.6667 \Omega \end{aligned}$$

$$Y = (\overline{A} + \overline{B})(\overline{C} + \overline{D}\bar{E}) + \overline{A} \cdot \overline{B}(\overline{C} + \bar{E}) + \overline{D}(AB + E)$$



16/02/16

$$Y = (\overline{A} \cdot B)(\overline{C} + \overline{D} + \bar{E}) + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}\bar{E} + \overline{D}AB + \overline{D}\bar{E}$$

$$Y = \overline{ABC} + \overline{ABD} + \overline{ABE} + \overline{AC} + \overline{B}\overline{E} + \overline{AB}\overline{D} + \overline{DE}$$

$$Y = \overline{AC} + \overline{B}\overline{D} + \overline{A}\overline{E} + \overline{D}\bar{E}$$
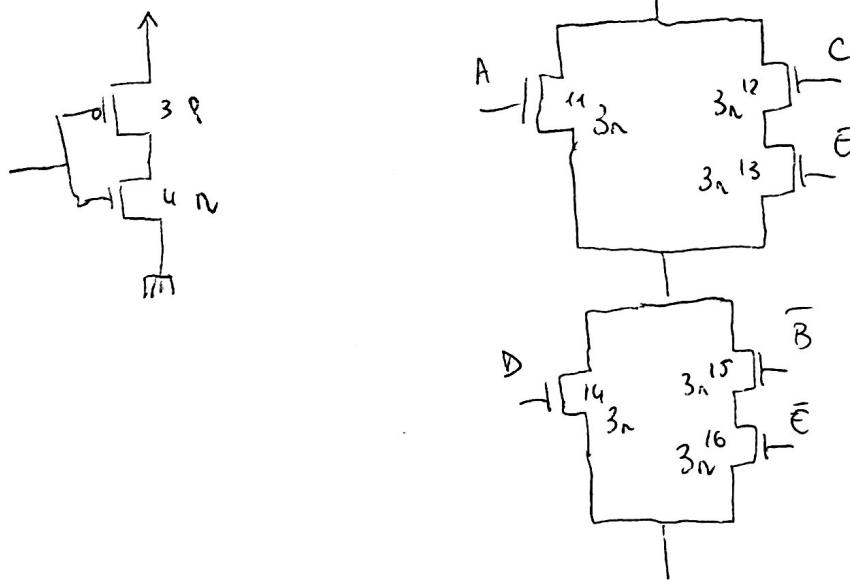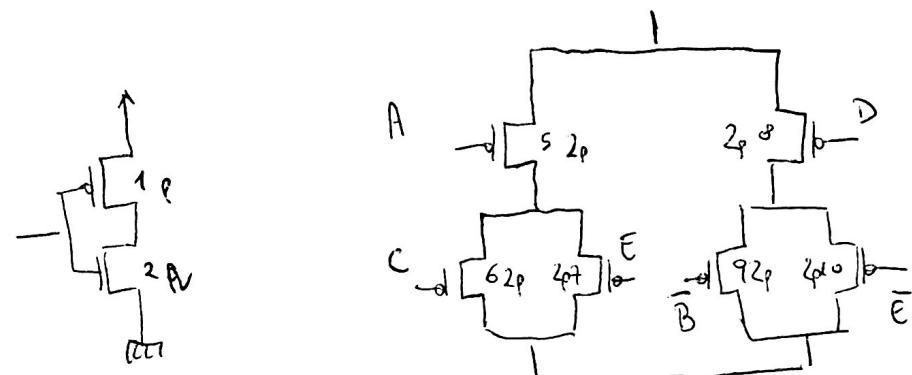
$$Y = \overline{A}(\overline{C} + \bar{E}) + \overline{D}(B + \bar{E})$$



• INVERTER ON BASE

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_3 = P = 5$$

$$\left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_4 = n = 2$$

• PUN

- WORST CASE: Q₅, Q₆ o Q₅, Q₇ o Q₈, Q₉ o Q₈, Q₁₀

$$\left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_6 = x$$

$$\frac{1}{x} \cdot \frac{1}{x} = \frac{1}{P} \Rightarrow \frac{2}{x} = \frac{1}{P} \Rightarrow x = 2P$$

• PDN

(2)

- WORST CASE : $Q_{12}, Q_{13}, Q_{15}, Q_{16} \rightarrow$ Non è possibile avere \bar{E} ed E .

- WORST CASE : $Q_{31}, Q_{15}, Q_{16} \Rightarrow Q_{12}, Q_{13}, Q_{14}$

$$\left(\frac{W}{L}\right)_{11} = \left(\frac{W}{L}\right)_{15} = \left(\frac{W}{L}\right)_{16} = X$$

$$\frac{1}{X} + \frac{1}{X} + \frac{1}{X} = \frac{1}{n} \quad \frac{3}{X} = \frac{1}{n} \Rightarrow X = 3n$$


16/02/2016

(1)

EFERW C)

$$Q=1 \rightarrow D = \text{Hz}$$

$Q_1 \rightarrow \text{OFF}$

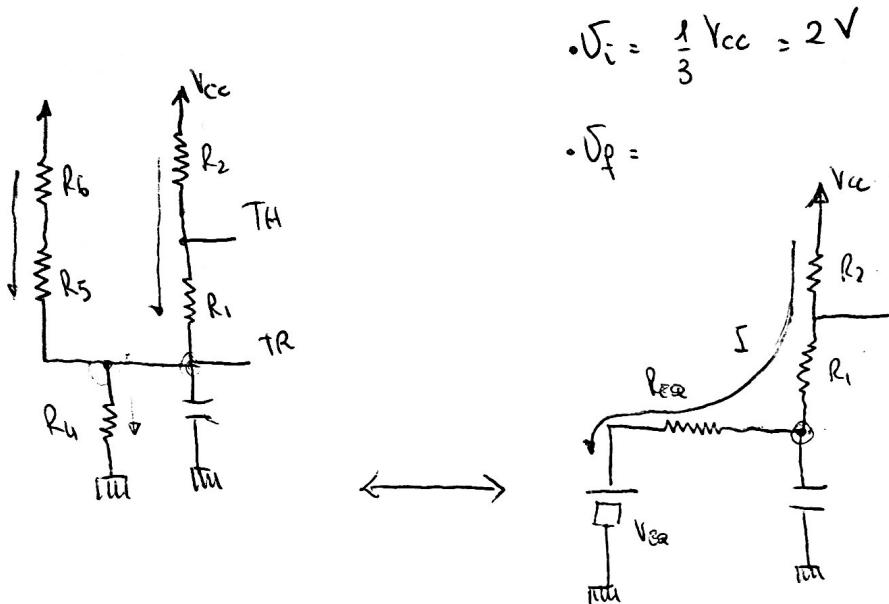

$$\cdot V_i = \frac{1}{3} V_{cc} = 2 \text{ V}$$

$$\cdot V_f =$$

$$V_{eq} = V_{cc} \cdot \frac{R_4}{R_4 + R_5 + R_6} = \frac{90}{17} \text{ V}$$

$$R_{eq} = R_4 \parallel (R_5 + R_6) = \frac{9000}{17} \text{ \Omega}$$

$$I = \frac{V_{cc} - V_{eq}}{R_1 + R_2 + R_{eq}} = \frac{1}{2000} \text{ A} \quad \rightarrow V_f = V_{cc} - (R_1 + R_2) I = 5.6 \text{ V}$$

$$\cdot V_{common} \quad \text{se} \quad V_{TH} = \frac{2}{3} V_{cc} = 6 \text{ V}$$

$$I_2 = \frac{V_{cc} - V_{TH}}{R_2} = \frac{1}{1000} \text{ A}$$

$$V_{common} = V_{TH} - R_1 I_2 = 3 \text{ V}$$

$$\text{VERIFICO: } V_i < V_{common} < V_f \rightarrow \text{OK}$$

$$T_s = T_1 \ln \left(\frac{V_i \cdot V_f}{V_{common} \cdot V_f} \right) = 3.44823 \cdot 10^{-6}$$


temp

$$T_1 = R_1 C = [R_1 + R_2 \parallel (R_4 \parallel (R_5 + R_6))] \cdot C$$

$$= \frac{60000}{17} \cdot C = 7.2667 \cdot 10^{-5} \text{ s}$$

$$= 9.9 \cdot 10^{-6} \text{ s}$$
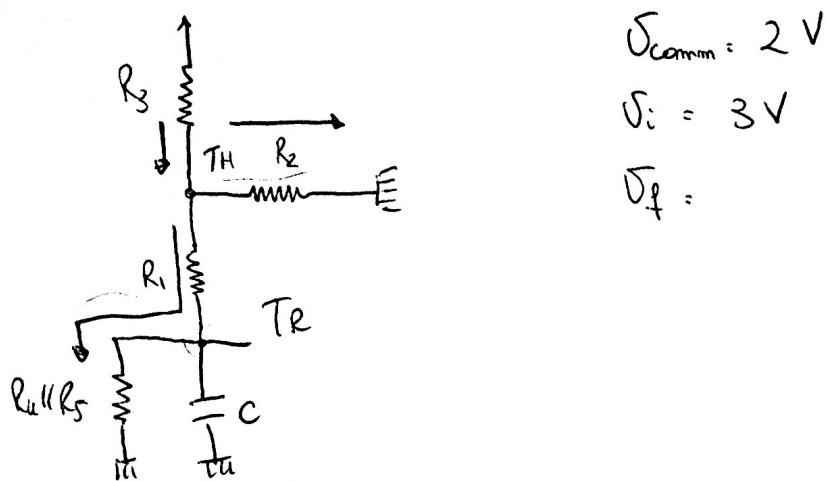
$$Q=0 \rightarrow D=0 \rightarrow Q_1 = ON$$



Per la V_f :

$$\left\{ \begin{array}{l} I_3 = \frac{V_{cc}}{R_3} - \frac{V_{TH}}{R_3} \\ I_2 = \frac{V_{TH}}{R_2} \\ I_1 = -I_2 + I_3 = \frac{V_{TH}}{R_1 + R_{4||R_5}} \end{array} \right.$$

$$* -\frac{V_{TH}}{R_2} + \frac{V_{cc}}{R_3} - \frac{V_{TH}}{R_3} = \frac{V_{TH}}{R_1 + R_{4||R_5}} \rightarrow V_{TH} = \left(\frac{\frac{V_{cc}}{R_3}}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_1 + R_{4||R_5}}} \right) = \frac{201}{446} \text{ V}$$

$$\text{Quindi: } I_1 = \text{sostituendo } V_{TH}: \quad I_1 = \frac{167}{446000}$$

$$V_f = V_{TH} - R_1 I_1 = \frac{27}{223} = 0,121 \text{ V}$$

Sembra che: $V_i > V_{common} > V_f$

$$\overline{T}_2 = T_2 \ln \left(\frac{V_i - V_f}{V_{common} - V_f} \right) = 3.0309 \cdot 10^{-6} \text{ s}$$

$$\overline{T}_2 = T_1 + \overline{T}_2 = 6.67913 \cdot 10^{-6}$$


$f = \frac{1}{T} = 156341.7 \text{ Hz}$

$$T_2 = R_{V_2} C = \left[\frac{\frac{8000}{3}}{R_1 + R_2 || R_3} \parallel \frac{\frac{13000}{49}}{R_{4||R_5}} \right] C = 322.8699 \cdot C = 7,10314 \cdot 10^{-6} \text{ s}$$

28/01/2016

(1)

ESERCIZIO A)

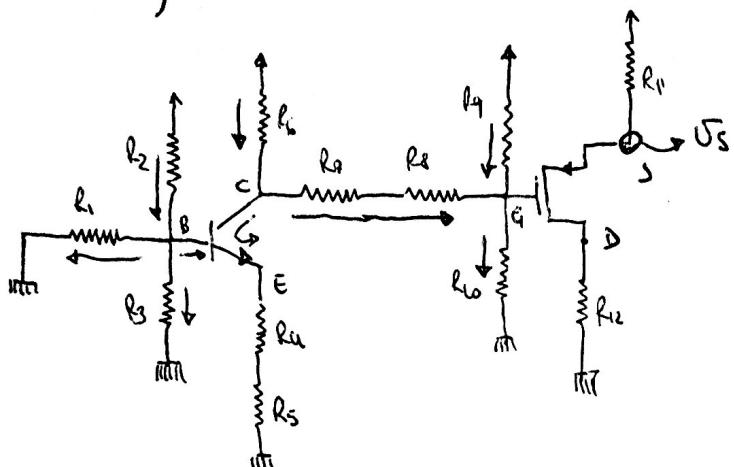

- $I_S = \frac{V_{cc} - V_s}{R_1} = 2 \text{ mA}$

- $I_a = 0 \rightarrow I_S = I_D = 2 \text{ mA}$

- $V_D = R_{12} \cdot I_D = 7 \text{ V}$

PIOTRIZZO ZONA SATURAZIONE $\rightarrow V_{DS} = V_T - \sqrt{\frac{I_D}{K}} = -3 \text{ V}$

- $V_{DS} = V_a - V_s \rightarrow V_a = V_{DS} + V_s = 8 \text{ V}$

VERIFICO ZONA SATURAZIONE $\rightarrow V_{DS} < V_{DSAT} - V_T \rightarrow -4 \text{ V} < -2 \text{ V} \rightarrow \text{OK}$

- $I_Q = \frac{V_{cc} - V_a}{R_Q} = 0,5 \text{ mA}$

- $I_{10} = \frac{V_a}{R_{10}} = 1 \text{ mA}$

- $I_B + I_Q = I_{10} \rightarrow I_B = I_{10} - I_Q = 0,5 \text{ mA}$

- $V_C - V_a = (R_7 + R_8) I_B \rightarrow V_C = V_a + (R_7 + R_8) I_B = 12 \text{ V}$

- $I_6 = \frac{V_{cc} - V_c}{R_6} = 2,5 \text{ mA}$

- $I_C = I_6 - I_B = 2 \text{ mA}$

PIOTRIZZO ZAD $\rightarrow I_C \gg I_B \Rightarrow I_C \approx I_E = 2 \text{ mA}$

- $V_E = (R_u + R_s) I_E = 7 \text{ V}$

VERIFICO Z.A.D : $V_{ce} > V_{cesat} \rightarrow 5 \text{ V} > 0,2 \text{ V}$

- $I_B = \frac{I_C}{h_{FE}} =$

- $V_{BE} = V_B - V_E \rightarrow V_{BE} = V_{BE} + V_E = 7,7 \text{ V}$

(2)

$$\bullet I_2 = \frac{V_{ce} - V_B}{R_2} = 1,03 \text{ mA}$$

$$\bullet I_1 = \frac{V_B}{R_1} = 0,5 \text{ mA}$$

$$\bullet I_2 = I_1 + I_3 + I_B \rightarrow I_3 = I_2 - I_1 - I_B = 0,5231 \text{ mA}$$

$$\bullet R_2 = \frac{V_B}{I_2} = 14719,84 \Omega$$

PUNTI DI RIPOSO


$Q_1:$

$$h_{fe} = 300 \quad h_{FE} = 290 \quad h_e = 6,8 \text{ k}\Omega \quad I_c = 2 \text{ mA} \quad V_{ce} = 15 \text{ V}$$

$Q_2:$

$$I_D = 2 \text{ mA} \quad V_{DS} = -6 \text{ V} \quad g_m = 2k |V_{GS} - V_T| = 2 \frac{\text{mA}}{\text{V}}$$

28/01/2016

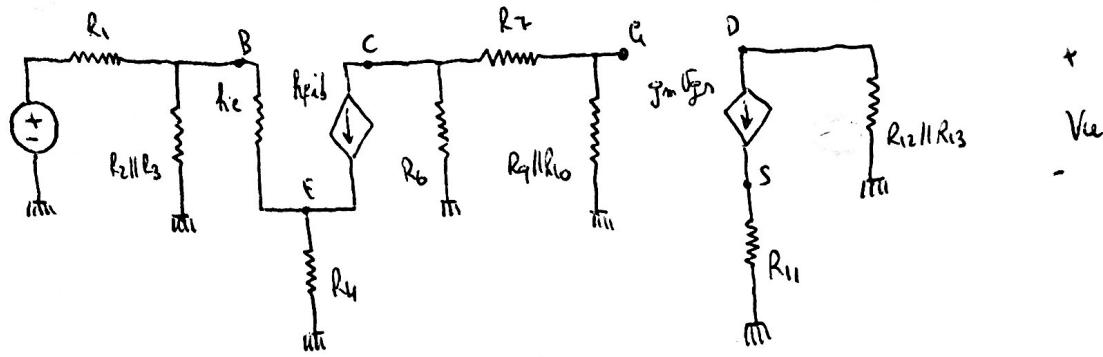


$$\cdot V_{u0} = -g_m V_{gs} (R_{12} || R_{13})$$


$$\cdot V_{gs} = V_g - g_m V_{gs} R_{11} \rightarrow V_{gs} = \frac{V_g}{1 + g_m R_{11}}$$

$$\cdot V_g = -h_{fe} i_b \cdot \frac{R_6 - R_7 || R_{10}}{R_6 + R_7 + R_9 || R_{10}}$$
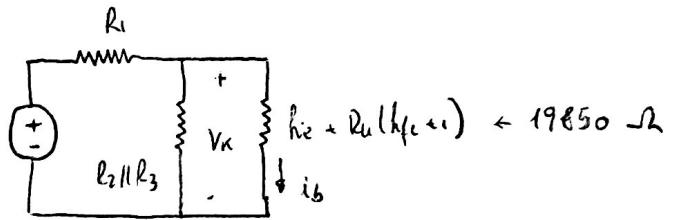
$$\cdot i_b = \frac{V_K}{R_{1e} + (h_{fe}+1) R_u}$$



$$\cdot V_K = V_i \cdot \frac{(R_2 || R_3) || (h_{ie} + R_u(h_{fe}+1))}{R_1 + (R_2 || R_3) || (h_{ie} + R_u(h_{fe}+1))}$$

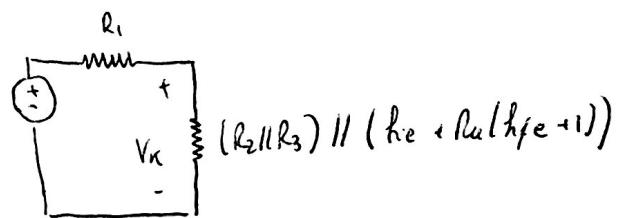

$$\begin{aligned} \underline{V_i} &= \frac{\frac{g_m (R_{12} || R_{13})}{1 + g_m R_{11}} \cdot \frac{h_{fe} \cdot R_6 \cdot R_7 || R_{10}}{R_6 + R_7 + R_9 || R_{10}} \cdot \frac{1}{\frac{1}{19.850}} \cdot \frac{(R_2 || R_3) || (h_{ie} + R_u(h_{fe}+1))}{R_1 + (R_2 || R_3) || (h_{ie} + R_u(h_{fe}+1))}}{54} \\ &= 3.704 \end{aligned}$$

28/01/2016

1

(SERVIZIO B)

$$Y = \overline{AE}(\overline{BC} + \overline{D}) + A\overline{B}\overline{C} + \overline{D}\overline{C}$$



$$Y = (\bar{A} + \bar{E})(\bar{B}C + \bar{D}) + A\bar{B}C + \bar{D}\bar{C}$$

$$Y = \bar{A}\bar{B}C + \bar{A}\bar{D} + \bar{B}C\bar{E} + \bar{D}\bar{E} + A\bar{B}C + \bar{D}C$$

$$Y = \bar{B}C + \bar{A}\bar{B} + \bar{B}C\bar{E} + \bar{D}\bar{E} + \bar{D}\bar{C}$$

$$Y = \bar{B}C + \bar{D}(\bar{A} + \bar{C} + \bar{E})$$

16 mottet

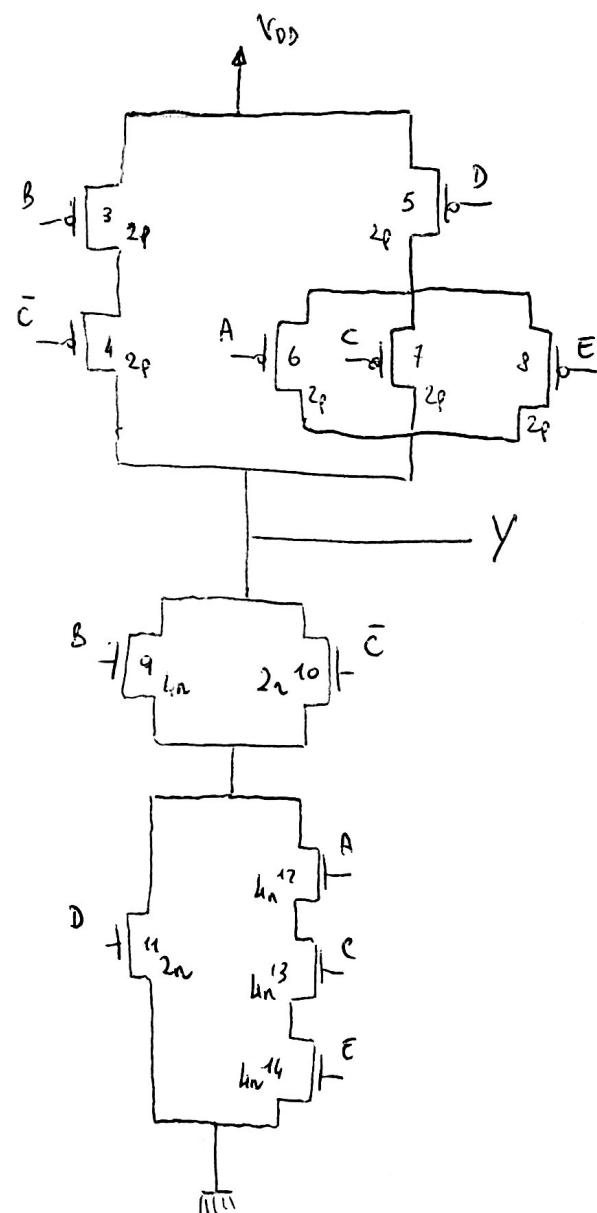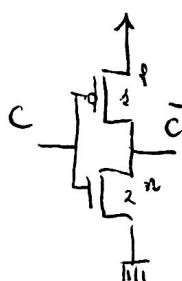

• INVERTER IN BASE

$$\left(\frac{w}{z}\right)_1 = \rho = 5$$

$$\left(\frac{W}{L}\right)_2 = n=2$$

• PUN

-WORST CASE: $Q_3, Q_4 \circ Q_5, Q_6, \circ Q_7, Q_8 \circ Q_9, Q_{10}$

$$\binom{w}{2}_{3,4,5,6,7,8} = x$$

$$\frac{1}{x} + \frac{1}{x} = \frac{1}{n} \rightarrow \frac{2}{x} = \frac{1}{n} \rightarrow x = 2n = 10$$

• PDN

-WORST CASE $\begin{cases} Q_9, Q_{12}, Q_{13}, Q_{14} \\ Q_{10}, Q_{12}, Q_{13}, Q_{14} \end{cases} \rightarrow$ Non possibile perché C e C sono presenti

$$\binom{w}{2}_{9,12,13,14} = x$$

$$\frac{1}{x} + \frac{1}{x} + \frac{1}{x} + \frac{1}{x} = \frac{1}{n} \rightarrow \frac{4}{x} = \frac{1}{n} \rightarrow x = 4n = 8$$

-WORST CASE ②:

2 casi possibili $\begin{cases} 1) Q_{10}, Q_{11} \\ 2) Q_9, Q_{11} e poi Q_{10}, Q_{11} \end{cases}$

1) Q_{10}, Q_{11}

$$\binom{w}{2}_{10,11} = y$$

$$\frac{1}{y} + \frac{1}{y} = \frac{1}{n} \rightarrow \frac{2}{y} = \frac{1}{n} \rightarrow y = 2n = 4$$

2) Q_9, Q_{11}

$$\binom{w}{2}_{11} = z$$

$$\frac{1}{z} + \frac{1}{4n} = \frac{1}{n} \rightarrow \frac{1}{z} = \frac{3}{4n} \rightarrow 3z = 4n \Rightarrow z = \frac{4n}{3}$$

Q_{10}, Q_{11}

$$\binom{w}{2}_{10} = k$$

$$\frac{1}{k} + \frac{1}{2} = \frac{1}{n} \rightarrow \frac{1}{k} = \frac{3}{4n} = \frac{1}{n} \rightarrow \frac{1}{k} = \frac{4-3}{4n} \rightarrow \frac{1}{k} = \frac{1}{4n} \rightarrow k = 4n = 8$$

AREE:

$$1) 2n + 2n = 4n = 8$$

→ SCELGO QUESTA CONFESSIONE


$$2) \frac{4}{3}n + 4n = \frac{8}{3}n + 8 = \frac{32}{3} (\approx 10,67)$$

28/01/2016

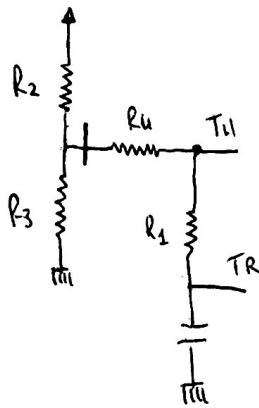ESEMPIO C)

$$Q=1 \rightarrow D=1\text{Hz}$$

$$V_{C_{in}} = V_{cc} \quad V_{S_1} = V_{cc} \quad \rightarrow V_{C_{in}} = 0V > V_{T_1} = -1V \quad \Rightarrow Q_1 = \text{OFF}$$




$$\cdot V_i = \frac{1}{3} V_{cc} = 2V$$

$$\cdot V_f : V_{cc} \cdot \frac{R_3}{R_2 + R_3} = \frac{24}{5} V \quad (= 4.8V)$$

$$\cdot V_{C_{out}} \quad \text{se} \quad V_{TH} = \frac{2}{3} V_{cc} = 4V$$

Applico THEVENIN

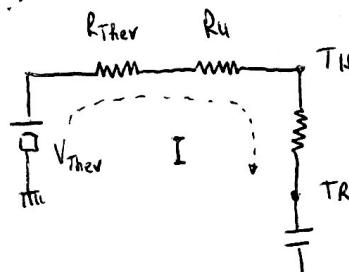

$$V_{Thev} = V_{cc} \cdot \frac{R_3}{R_2 + R_3} = 4.8V \quad R_{TR} = R_2 \| R_3$$

$$I = \frac{V_{Thev} - V_{TH}}{R_{Thev} + R_4} = 8 \cdot 10^{-4} A$$

$$V_{C_{out}} = V_{TH} - R_1 I = 3.04 V$$

VERIFICO CHE $V_i < V_{C_{out}} < V_f \rightarrow \text{OK}$


$$T_1 = T_1 \ln \left(\frac{V_i - V_f}{V_{C_{out}} - V_f} \right)$$

$$T_1 = R_{V_1} \cdot C = [R_1 + R_4 + R_2 \| R_3] \cdot C = 220 \Omega \cdot C = 1.034 \cdot 10^{-4} s$$

$$T_1 = 4.801 \cdot 10^{-5} s$$

$$Q=0 \rightarrow D=0$$
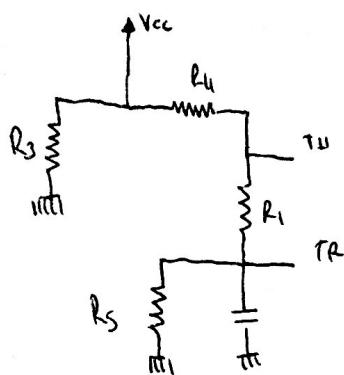
$$V_{C_{in}} = 0 \quad V_{S_1} = V_{CC} \quad V_{S_{11}} = -V_{CC} = -6V \quad V_{T_1} = -1V \quad Q_1 = ON$$



$$\cdot V_i = 3.04 \text{ V}$$

$$\cdot V_{C_{out}} = 2 \text{ V}$$

$$\cdot V_f = V_{CC} \cdot \frac{R_S}{R_E + R_S} = 0.75 \text{ V}$$

VERIFICO CHE $V_i > V_{C_{out}} > V_f \rightarrow OK$

$$T_2 = T_1 \cdot \ln \left(\frac{V_i - V_f}{V_{C_{out}} - V_f} \right)$$

$$T_1 = R_{V_1} \cdot C = [R_S \parallel (R_E + R_U)] \cdot C = 175 \cdot C = 8.225 \cdot 10^{-6} \text{ s}$$

$$T_2 = 4.97968299 \cdot 10^{-6} \text{ s}$$

$$T = T_1 + T_2 = 5.298868287 \cdot 10^{-5} \text{ s}$$

$$f = \frac{1}{T} = 18871,95 \text{ Hz}$$

08/01/2016


(1)

ESEMPIO c)

$$Q_1 \rightarrow D = 'H2$$

$$\begin{array}{lll} U_{S_1} = 0V & U_{S_1} = 0V & U_{S_1} = 0V < U_{T_1} = 2V \\ J_{S_1} = 0V & J_{S_2} = V_{CC} & U_{S_2} = -6V < U_{T_2} = -1V \end{array}$$

Q_1 OFF
 Q_2 ON

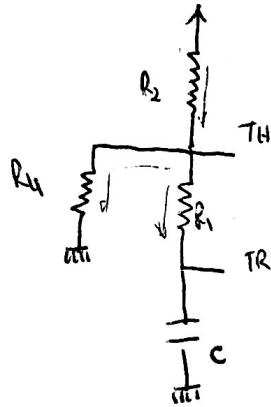

$$\bullet V_i = \frac{1}{3} V_{CC} = 2V$$

$$\bullet V_f = V_{CC} \cdot \frac{R_4}{R_2 + R_4} = 5V$$

$$\bullet V_{common} = V_{TH} = \frac{2}{3} V_{CC} = 4V$$

$$I_2 = \frac{V_{CC} - V_{TH}}{R_2} = 2mA$$

$$I_u = \frac{V_{TH}}{R_4} = \frac{1}{1250} A$$

$$I_1 = I_2 - I_u = 1.2mA$$

$$\bullet V_{common} = V_{TH} - R_1 I_1 = 3.4V$$

VERIFICO CHE $V_i < V_{common} < V_f$ → OK

$$T_1 = T_1 \ln \left(\frac{V_i - V_f}{V_{common} - V_f} \right)$$

$$T_1 = R_{V_1} \cdot C = \left[R_1 + R_2 / (R_u) \right] \cdot C = \frac{1000}{3} \cdot C = \frac{17}{187500} s$$

$$T_1 = 5,699385179 \cdot 10^{-5} s$$


$$Q=0 \rightarrow D=0$$

$$\cdot U_{G1} = V_{cc} \quad U_{S1} = 0V \quad U_{GS1} = 6V > V_{T1} = 1V$$

Q_1 ON

$$\cdot U_{G2} = V_{cc} \quad U_{S2} = V_{cc} \quad U_{GS2} = 0V > U_{T2} = -1V$$

Q_2 OFF

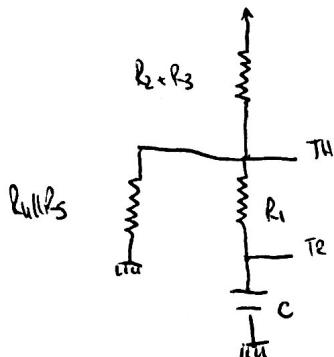

$$\cdot V_i = 3,6V$$

$$\cdot U_{com} = 2V$$

$$\cdot U_f = V_{cc} \cdot \frac{R4 \parallel R_S}{R2 + R3 + R4 \parallel R_S} = \frac{30}{47} V$$

$$T_2 = T_2 \ln \left(\frac{V_i - U_f}{U_{com} - U_f} \right)$$

$$T_2 = R_{V2} \cdot C = \left[R_1 + R_{4\parallel R_S} \parallel (R_2 + R_3) \right] \cdot C = \frac{33500}{47} \cdot C = 6.866808511 \cdot 10^{-5} s$$

$$T_2 = 3.627235107 \cdot 10^{-5} s$$


$$T = T_1 + T_2 = 9.126620286 \cdot 10^{-5} s$$

$$f = \frac{1}{T} = 10956.95853 \text{ Hz}$$

1)

2/09/2015

4

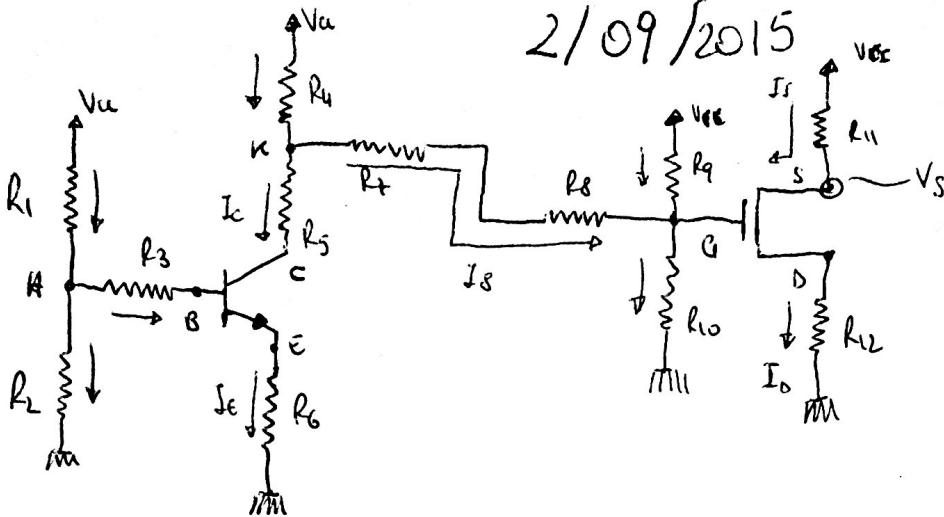

- $I_S = \frac{V_{CC} - V_S}{R_{12}} = 2.25 \text{ mA}$
- $I_G = 0 \Rightarrow I_S = I_D = 2.25 \text{ mA}$
- $V_D = R_{12} I_D = 6.75 \text{ V}$
- $V_{ES} = V_T \pm \sqrt{\frac{I_D}{K}}$ ma poiché deve valere $J_{ES} < V_i < 0 \Rightarrow V_{ES} = V_T - \sqrt{\frac{I_D}{K}} = -6 \text{ V}$
- $V_{ES} = V_A - V_S \Rightarrow V_A = V_S + V_{ES} = 8.6 \text{ V}$

VERIFICO LA SATURAZIONE $[V_{DS} < V_{ES} - V_T \Rightarrow -5.85 < -3]$ OK

- $I_Q = \frac{V_{CC} - V_E}{R_Q} = 0.5 \text{ mA}$
 - $I_{IO} = \frac{V_E}{R_{IO}} = 1 \text{ mA}$
 - $I_B = I_{IO} - I_Q = 0.5 \text{ mA}$
 - $V_K - V_E = (R_7 + R_8) I_B \Rightarrow V_K = 10 \text{ V}$
 - $I_H = \frac{V_{CC} - V_K}{R_H} = 2.5 \text{ mA}$
 - $I_S = I_H - I_B = 2 \text{ mA}$
 - $I_C = I_S = 2 \text{ mA}$
- IPOTIZZO 2. A.D $\Rightarrow I_B \ll I_C \Rightarrow I_C \approx I_C = 2 \text{ mA}$
- $V_E = R_6 I_E = 3 \text{ V}$

(2)

$$\cdot V_K - V_C = R_S I_C \Rightarrow V_C = V_K - R_S I_C = 8V$$

VERIFICÓ LA Z.A.D [$V_{CE} > V_{CE,SNR} \Rightarrow 5 > 0.2 V$]

$$\cdot V_{BE} = V_B - V_E \Rightarrow V_B = 3.7 V$$

$$\cdot I_B = \frac{I_C}{h_{FE}} = 6.8965 \mu A$$

$$\cdot V_H - V_B = h_3 I_B \Rightarrow V_H = 3.7275 V$$

$$\cdot I_1 = \frac{V_{CC} - V_H}{R_1} = 0.7136 mA$$

$$\cdot I_2 = I_1 - I_B = 0.7067 mA$$

$$\boxed{\cdot R_2 = \frac{V_H}{I_2} = 5274.51 \Omega}$$

Q₁

$$h_{FE} = 290 \quad h_{FE} > 300 \quad h_{ie} = 6.8 k\sqrt{2} \quad I_C = 2mA \quad V_{CE} = 5V$$


Q₂

$$g_m = |2k(V_{DS} - V_T)| = 1.5 \frac{mA}{V} \quad I_D = 2.25 mA \quad V_{DS} = 5.85 V$$

2)

2109 / 2015

3

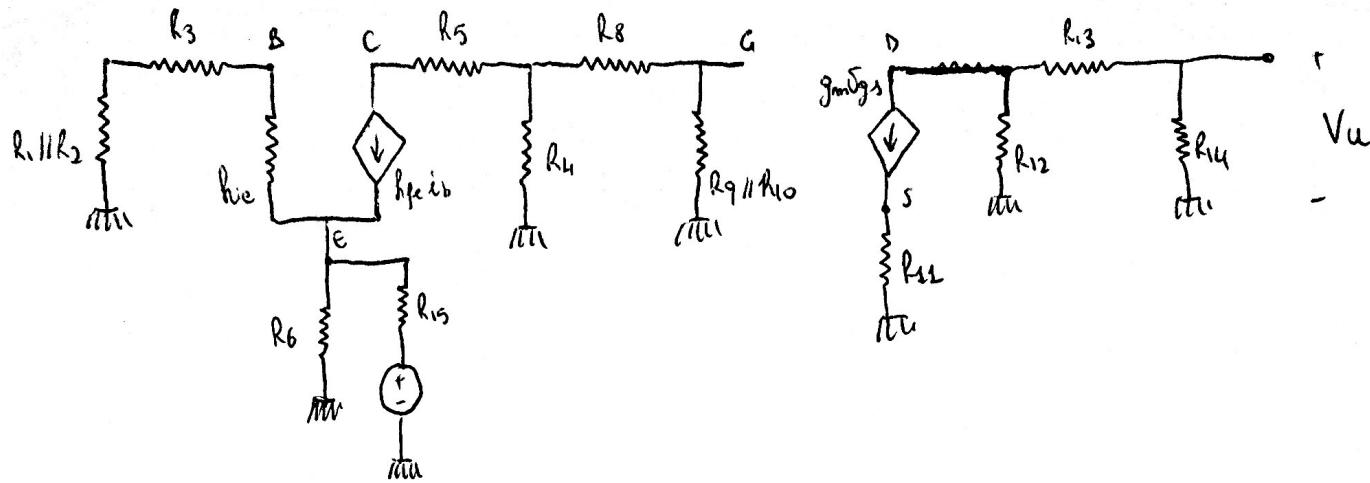

$$\bullet V_u = -g_m \frac{V_{gs}}{R_2 + R_3 + R_{14}} \cdot R_{13}$$

$$\bullet V_{gs} = V_g - V_s = V_g - g_m V_{gs} R_{11} \Rightarrow V_{gs} = \frac{V_g}{1 + g_m R_{11}}$$


$$\bullet V_g = -h_{fe} i_b \frac{R_4}{R_4 + R_8 + R_9 || R_{10}} \cdot R_9 || R_{10}$$

$$\bullet (h_{fe} + 1) i_b = -\frac{V_K}{R_S} \cdot \frac{R_6 || R_5}{(h_{fe} + 1)}$$



 $(h_{fe} + 1) i_b$

Sia:

$$R_1 || R_2 + R_3 + h_{ie} = R_S$$

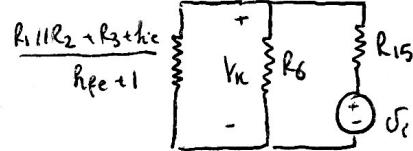


$$\bullet V_K = V_i \frac{R_6 || \frac{R_S}{h_{fe} + 1}}{R_{15} + R_6 || \frac{R_S}{h_{fe} + 1}}$$

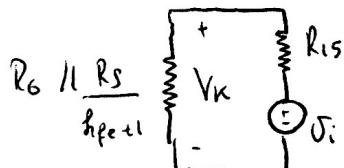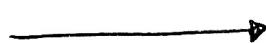

$$\bullet \frac{V_u}{V_i} = -g_m \frac{R_{12} - R_{14}}{R_{12} + R_3 + R_{14}} \cdot \frac{1}{1 + g_m R_{11}} \cdot h_{fe} \frac{R_{11} \cdot R_9 || R_{10}}{R_{11} + R_8 + R_9 || R_{10}} \cdot \frac{1}{R_S} \cdot \frac{R_6 || \frac{R_S}{h_{fe} + 1}}{R_{15} + R_6 || \frac{R_S}{h_{fe} + 1}} = -16,9$$

21/07/15

1)

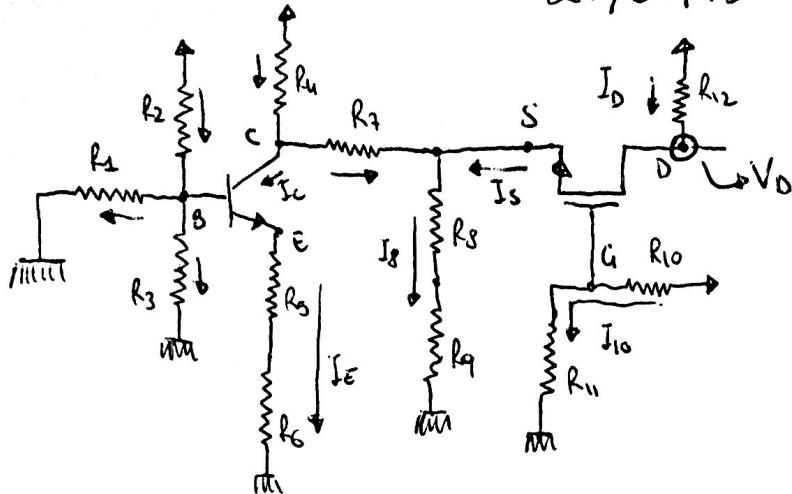

$$\bullet I_D = \frac{V_{cc} - V_D}{R_{12}} = 2 \text{ mA} \quad \text{poiché } I_E = 0 \Rightarrow I_S = 2 \text{ mA} > I_D$$

$$\bullet V_{es} = V_T + \sqrt{\frac{I_D}{\kappa}} = V_T + \sqrt{\frac{I_D}{\kappa}} \quad (\text{perché deve valere } V_{es} > V_T > 0) \Rightarrow V_{es} = 3 \text{ V}$$

$$\bullet I_{10} = \frac{V_{cc}}{R_{10} + R_{11}} = 60 \mu\text{A}$$

$$\bullet V_a = I_{10} \cdot R_{11} = 12 \text{ V}$$

$$\bullet V_{as} = V_a - V_s \Rightarrow V_s = V_a - V_{as} = 9 \text{ V}$$

VERIFICHEMO LA SATURAZIONE $[V_{os} > V_{es} - V_T \quad \text{ovvero} \quad 12.5 - 9 > 3 - 1 \rightarrow 3.5 > 2]$

$$\bullet I_8 = \frac{V_s}{R_8 + R_9} = 1 \text{ mA}$$

$$\bullet I_s + I_7 = I_8 \Rightarrow I_7 = I_8 - I_s = -1 \text{ mA} \quad (\text{la corrente è negativa perché abbiamo sbagliato verso. Ma non è un problema})$$

$$\bullet V_c - V_s = R_7 \cdot I_7 \Rightarrow V_c = R_7 I_7 + V_s = 8 \text{ V}$$

$$\bullet I_u = \frac{V_{cc} - V_c}{R_u} = 1 \text{ mA}$$

$$\bullet I_c = I_u - I_7 = 2 \text{ mA}$$

SUPPONIAMO Z.A.D $\Rightarrow I_B \ll I_C \Rightarrow I_E \approx I_C = 2 \text{ mA}$

$$\bullet V_{EB} = (R_5 + R_6) I_E = 3 \text{ V}$$

$$\bullet V_{BE} = V_B - V_E \Rightarrow V_B = 3.7 \text{ V}$$

$$\bullet V_{CE} = V_C - V_E = 5 \text{ V}$$

Con $I_C = 2 \text{ mA}$ e $V_{CE} = 5 \text{ V}$ abbiamo: $\beta_{FE} = 290$ $\beta_{FE} = 300$ $R_E = 6.8 \text{ k}\Omega$ ②

VERIFICHiamo Z.A.D $[V_{CE} > V_{CE, SAT} \text{ ovvero } 5 > 0.2 \text{ V}] \checkmark$

$$I_B = \frac{I_C}{\beta_{FE}} = 6.8965 \mu\text{A}$$

$$\cdot I_3 = \frac{V_B}{R_3} = 60 \mu\text{A}$$

$$\cdot I_1 = \frac{V_B}{R_1} = 3.7 \text{ mA}$$

$$\cdot I_2 = I_B + I_1 + I_3 = 3.76689 \text{ mA}$$

$$\boxed{\cdot R_2 = \frac{V_C - V_B}{I_2} = 3816,49 \Omega}$$

PUNTI DI FISSO

Q₁:

$$\cdot I_C = 2 \text{ mA} \quad V_{CE} = 5 \text{ V} \quad \beta_{FE} = 290 \quad \beta_{FE} = 300 \quad R_E = 6.8 \text{ k}\Omega$$


Q₂:

$$\cdot I_D = 2 \text{ mA} \quad V_{DS} = 3.5 \text{ V} \quad g_m = |2k(V_{GS} - V_T)| = \frac{2 \text{ mA}}{V}$$

3

21/07/15

2)

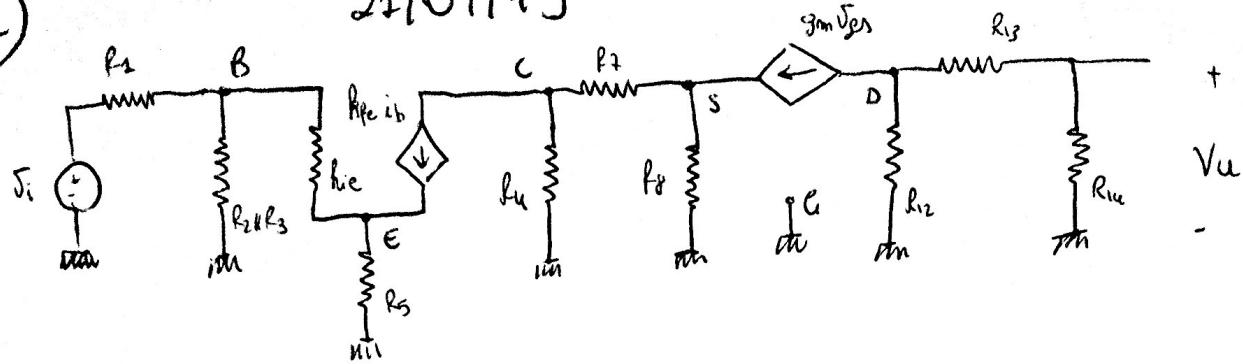


$$\bullet V_u = -g_m V_{GS} \frac{R_{12}}{R_{12} + R_{13} + R_{11}} \cdot R_{14}$$

$$\bullet V_{GS} = V_g - V_s = -V_s$$

$$\bullet V_s = R_8 I_8$$

PRINZIPLE DER SPANNUNGSFOLGE

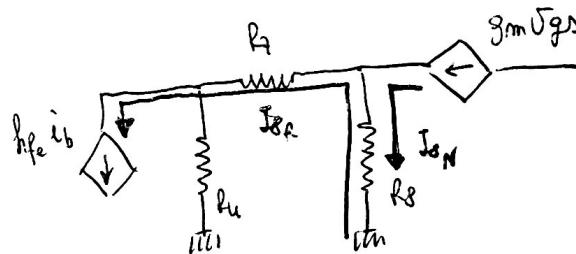
$$I_{8\text{FOSSO}} = -\frac{h_{FE} i_b \cdot R_u}{R_u + R_7 + R_8}$$



$$I_8 = -\frac{g_m V_s (R_u + R_7)}{R_u + R_7 + R_8} - \frac{h_{FE} i_b R_u}{R_u + R_7 + R_8}$$


$$\bullet V_s = R_8 \left(-\frac{g_m V_s (R_u + R_7)}{R_u + R_7 + R_8} - \frac{h_{FE} i_b R_u}{R_u + R_7 + R_8} \right) \Rightarrow V_s \left(1 + \frac{g_m (R_u + R_7) R_8}{R_u + R_7 + R_8} \right) = -\frac{h_{FE} i_b R_u R_8}{R_u + R_7 + R_8}$$
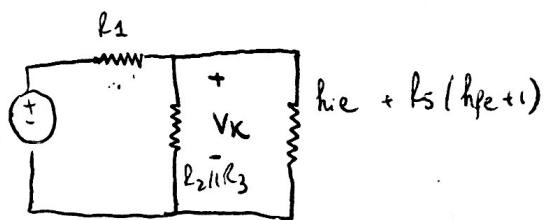
$$V_s = -\frac{h_{FE} R_u R_8}{R_u + R_7 + R_8 + (R_u + R_7) R_8 g_m} \cdot i_b$$



$$\bullet i_b = \frac{V_K}{h_{FE} + R_5 (h_{FE} + 1)}$$


$$\bullet V_K = V_i \frac{(R_2 || R_3) // (h_{FE} + R_5 (h_{FE} + 1))}{R_1 + [(R_2 || R_3) // (h_{FE} + R_5 (h_{FE} + 1))]}$$

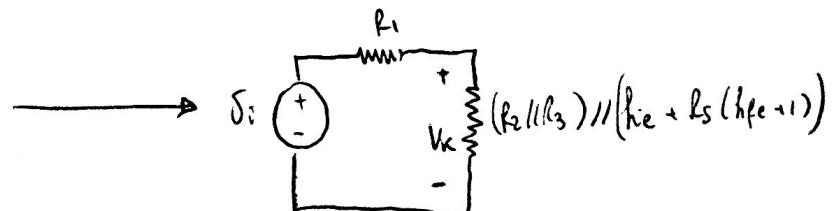

$$\bullet \frac{V_u}{V_i} = -g_m \frac{R_{12} R_{14}}{R_2 + R_3 + R_{11}} \cdot \frac{h_{FE} R_u R_8}{R_u + R_7 + R_8 + (R_u + R_7) R_8 g_m} \cdot \frac{1}{h_{FE} + R_5 (h_{FE} + 1)} \cdot \frac{(R_2 || R_3) // (h_{FE} + R_5 (h_{FE} + 1))}{R_1 + [(R_2 || R_3) // (h_{FE} + R_5 (h_{FE} + 1))]} = [-6,47]$$

9/6/15

1)

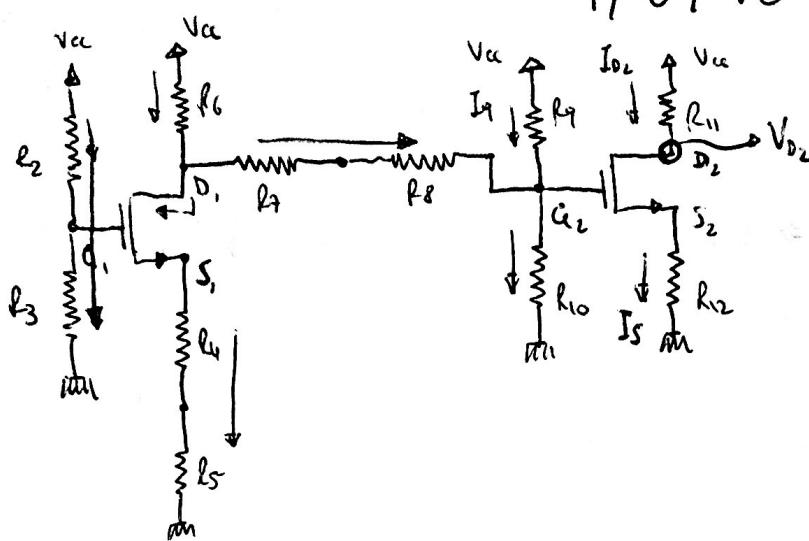

- $I_{D_2} = \frac{V_{cc} - V_{D_2}}{R_{11}} = 2 \text{ mA}$ poiché $I_{e_2} = 0 \Rightarrow I_{S_2} = 2 \text{ mA} = I_{D_2}$
- $V_{S_2} = R_{12} I_{S_2} = 5 \text{ V}$
- $V_{G_{S_2}} = V_T \pm \sqrt{\frac{I_{D_2}}{K}} = V_T + \sqrt{\frac{I_{D_2}}{K}}$ perché deve valere $V_{G_{S_2}} > V_T > 0 \Rightarrow V_{G_{S_2}} = 3 \text{ V}$
- $V_{G_{S_2}} = V_{G_2} - V_{S_2} \Rightarrow V_{G_2} = 8 \text{ V}$
- VERIFICO LA SATURAZIONE $[V_{D_2} > V_{G_{S_2}} - V_T \text{ ovvero } 10 - 5 > 3 - 1 \rightarrow 5 > 2 \quad \checkmark]$
- $I_g = \frac{V_{cc} - V_{G_2}}{R_g} = 0.5 \text{ mA}$
- $I_{10} = \frac{V_{G_2}}{R_{10}} = 1 \text{ mA}$
- $I_8 = I_{10} - I_g = 0.5 \text{ mA}$
- L'incognita non la posso trovare momentaneamente. Continuo il circuito per poi tornare indietro.
- $I_6 = \frac{V_{cc} - V_{D_1}}{R_6}$
- $V_{D_1} - V_{G_2} = (R_7 + R_8) I_8 \Rightarrow V_{D_1} = V_{G_2} + (R_7 + R_8) I_8$
- $I_{D_1} = I_6 - I_8$
- $V_{S_1} = (R_4 + R_5) I_{D_1}$
- $V_{G_1} = R_3 I_3 = 6 \text{ V}$
- $I_3 = I_2 = \frac{V_{cc}}{R_2 + R_3} = 60 \mu\text{A} \quad (\text{perché } I_{e_1} = 0)$

(2)

$$U_{DS_1} = U_{CE_1} - U_{S_1} = 6 - (R_u + R_S) I_{D_1}$$

$$\text{Supponiamo che } I_{D_1} = k (U_{DS_1} - V_T)^2 = k (6 - (R_u + R_S) I_{D_1} - 1)^2 = k (5 - (R_u + R_S) I_{D_1})^2$$

$$I_{D_1} = k ((R_u + R_S)^2 I_{D_1}^2 - 10 (R_u + R_S) I_{D_1} + 25) \Rightarrow k (R_u + R_S)^2 I_{D_1}^2 - (1 + 10 (R_u + R_S) k) I_{D_1} + 25k = 0$$

$$1125 I_{D_1}^2 + 8.5 I_{D_1} + \frac{1}{80} = 0 \quad \begin{cases} I_{D_1}' = 2 \text{ mA} \\ I_{D_1}'' = 5.56 \text{ mA} \end{cases}$$

Dobbiamo scegliere fra le due:

Aumento:

$$\begin{array}{lll} V_{S_1}' = 3 \text{ V} & I_6' = 2.5 \text{ mA} & V_{D_1}' = 9 \text{ V} \\ V_{S_1}'' = 8.25 & I_6'' = 6.05 \text{ mA} & V_{D_1}'' = -3.78 \text{ V} \end{array} \leftarrow \text{sceglie } I_{D_1} = I_{D_1}'$$

Quindi:

$$V_{D_1} - U_{CE_2} = R_7 I_8 + R_8 I_8 \Rightarrow R_8 = \frac{V_{D_1} - U_{CE_2} - R_7 I_8}{I_8} \Rightarrow R_8 = 1900 \Omega$$

Verificare la saturazione $\Rightarrow [U_{DS_1} > U_{DS_1} - V_T \text{ ovvero } 6 > 2]$

- - - - -
PUNTI DI RIPOSO

Q₁:

$$I_D = 2 \text{ mA} \quad V_{DS} = 6 \text{ V} \quad g_m = |2k(U_{DS} - V_T)| = 2 \cdot 10^{-3} \frac{\text{A}}{\text{V}}$$


Q₂:

$$I_D = 2 \text{ mA} \quad V_{DS} = 6 \text{ V} \quad g_m = |2k(U_{DS} - V_T)| = 2 \cdot 10^{-3} \frac{\text{A}}{\text{V}}$$

2)

9/06/15

3

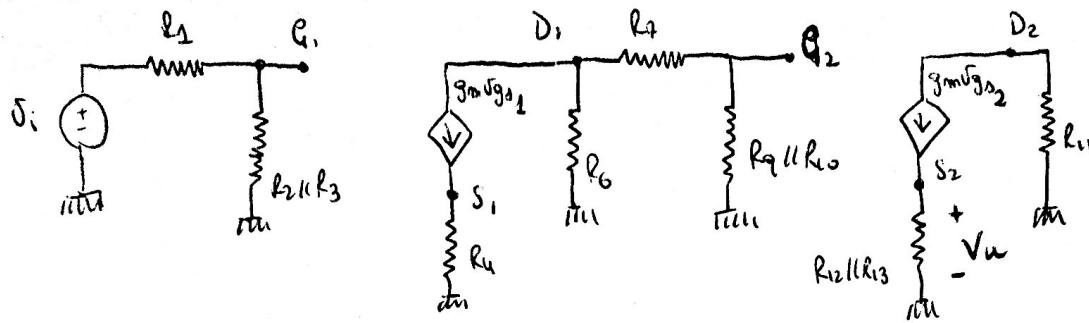

$$\bullet V_u = g_m V_{gD2} (R_{12} \parallel R_{13})$$

$$\bullet V_{gD2} = V_{g2} - V_{s2} = V_{g2} - g_m V_{gD2} (R_{12} \parallel R_{13}) \Rightarrow V_{gD2} = \frac{V_{g2}}{1 + g_m (R_{12} \parallel R_{13})}$$


$$\bullet V_{g2} = -g_m V_{gD1} \cdot \frac{R_6}{R_6 + R_7 + R_9 \parallel R_{10}} \cdot R_9 \parallel R_{10}$$

neg ig 5

$$\bullet V_{gD1} = V_{g1} - V_{s1} = V_{g1} - g_m V_{gD1} \cdot R_u \Rightarrow V_{gD1} = \frac{V_{g1}}{1 + g_m R_u}$$

$$\bullet V_{g1} = V_i \cdot \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3}$$
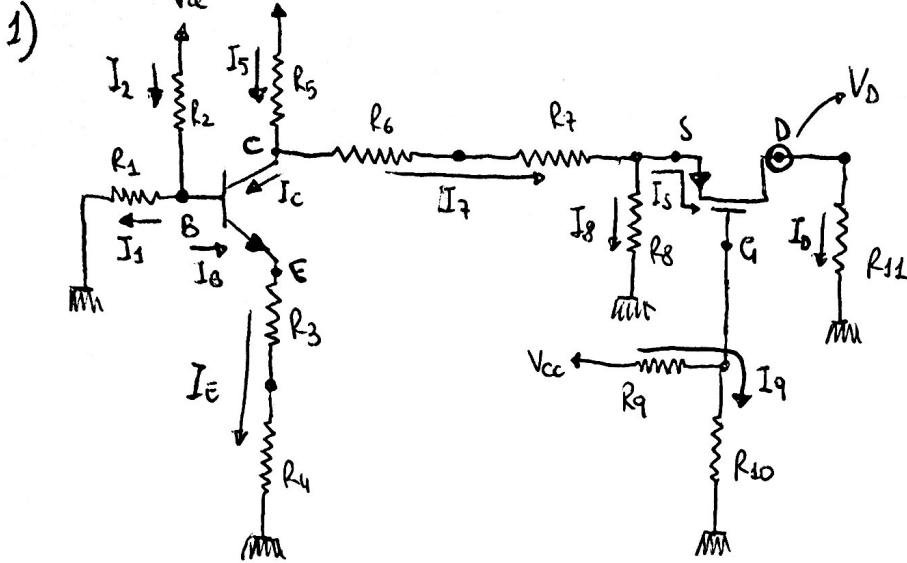
$$\bullet \frac{V_u}{V_i} = \frac{g_m^2 (R_{12} \parallel R_{13})}{1 + g_m (R_{12} \parallel R_{13})} \cdot \frac{R_6 \cdot (R_9 \parallel R_{10})}{R_6 + R_7 + (R_9 \parallel R_{10})} \cdot \frac{1}{1 + g_m R_u} \cdot \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} = \boxed{-2.91}$$



- $I_d = \frac{V_d}{R_{11}} = 2 \text{ mA} = I_d$
- Poiché $I_a = 0 \Rightarrow I_s = I_d = 2 \text{ mA}$
- $V_{as} = V_T - \sqrt{\frac{I_d}{K}} = -3 \text{ V}$ (il segno - perché deve valere $V_{as} < V_T < 0$)
- $I_q = \frac{V_{cc}}{R_q + R_{10}} = 0.9 \text{ mA}$
- $V_a = R_{10} I_q = 9 \text{ V}$
- $V_{as} = V_a - V_s \Rightarrow V_s = V_a - V_{as} = 12 \text{ V}$

VERIFICO LA SATURAZIONE $[V_{ds} < V_{as} - V_T \Rightarrow 8 - 12 < -3 + 1 \Rightarrow -4 < -2 \text{ OK}]$

- $I_8 = \frac{V_s}{R_8} = 0.5 \text{ mA}$
- $I_7 = I_8 + I_s = 2.5 \text{ mA}$
- $V_c - V_s = (R_6 + R_7) I_7 \Rightarrow V_c = V_s + (R_6 + R_7) I_7 = 13.5 \text{ V}$
- $I_5 = \frac{V_{cc} - V_c}{R_5} = 4.5 \text{ mA}$
- $I_c = I_5 - I_7 = 2 \text{ mA}$
- IPOTIZZO ZONA ATTIVA DELLETA $\Rightarrow I_B \ll I_C \Rightarrow I_E \approx I_C$
- $V_E = (R_3 + R_4) I_E = 8.5 \text{ V}$
- $V_{CE} = V_c - V_E = 5 \text{ V}$

③

VERIFICO Z.A.D $\Rightarrow V_{CE} > V_{CESAT} \Rightarrow 5 > 0.2 \text{ V}$ OK

Se $I_C = 2 \text{ mA}$ e $V_{CE} = 5 \text{ V}$, allora $h_{FE} = 290$ $h_{FE} = 300$ $h_{ie} = 4.8 \text{ k}\Omega$

$$\bullet V_{BE} = V_B - V_E \Rightarrow V_B = 9.2 \text{ V}$$

$$\bullet I_B \cdot \frac{I_C}{h_{FE}} = 6.8965 \mu\text{A}$$

$$\bullet I_2 = \frac{V_{CC} - V_B}{R_2} = 50 \mu\text{A}$$

$$\bullet I_1 = I_2 - I_B = 43.1035 \mu\text{A}$$

$$\bullet R_1 = \frac{V_B}{I_1} = 213439.74 \Omega$$

Q_1 : $h_{FE} = 290$ $h_{FE} = 300$ $h_{ie} = 4.8 \text{ k}\Omega$ $V_{CE} = 5 \text{ V}$ $I_C = 2 \text{ mA}$


$$Q_2: g_m = |2 \times (V_{DS} - V_t)| = 2 \frac{\text{mA}}{\text{V}}$$

$$I_D = 2 \text{ mA}$$

$$V_{DS} = -4$$

2) 16/6/2015

3)

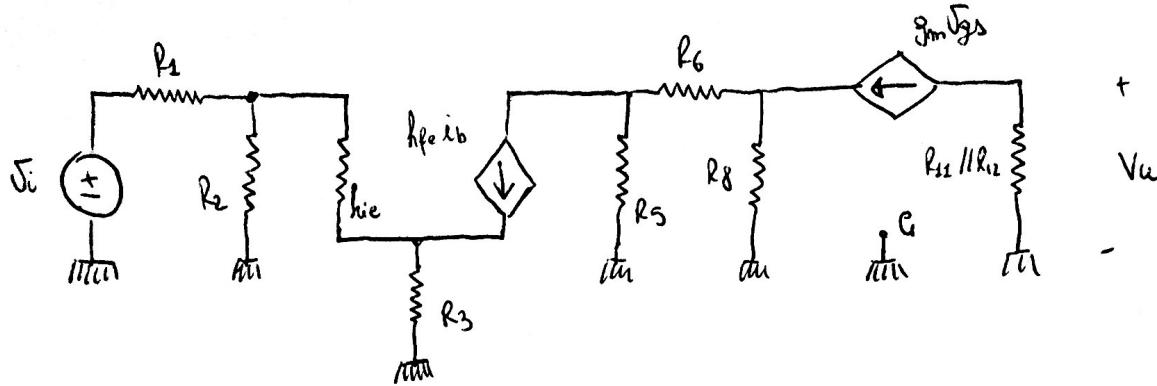

$$\bullet V_u = -g_m V_{gs} \cdot R_8 \parallel R_2$$


$$\bullet U_{gs} = U_g - U_S = -U_S$$

$$\bullet J_S = R_8 I_S$$

Principe di sovrapposizione

$$I_{S\text{ROSSO}} = -\frac{h_{fe} i_b R_S}{R_5 + R_6 + R_8}$$
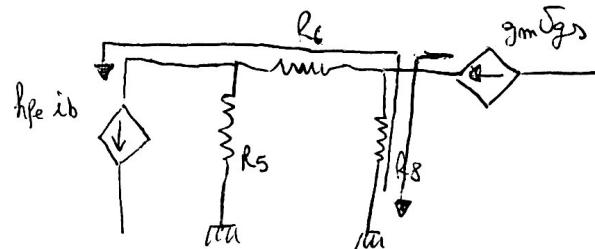
$$I_{S\text{NERO}} = \frac{g_m V_{gs} (R_5 + R_6)}{R_5 + R_6 + R_8}$$




$$J_S = \frac{g_m V_{gs} (R_5 + R_6)}{R_5 + R_6 + R_8} - \frac{h_{fe} R_S i_b}{R_5 + R_6 + R_8}$$


$$\bullet V_S = R_8 \left(\frac{g_m U_S (R_5 + R_6)}{R_5 + R_6 + R_8} - \frac{h_{fe} R_S i_b}{R_5 + R_6 + R_8} \right) \Rightarrow V_S \left(1 + \frac{R_8 (R_5 + R_6) g_m}{R_5 + R_6 + R_8} \right) = -\frac{h_{fe} R_S i_b R_S}{R_5 + R_6 + R_8}$$

$$V_S = -\frac{h_{fe} R_S R_8 i_b}{R_5 + R_6 + R_8 + (R_5 + R_6) R_8 g_m}$$

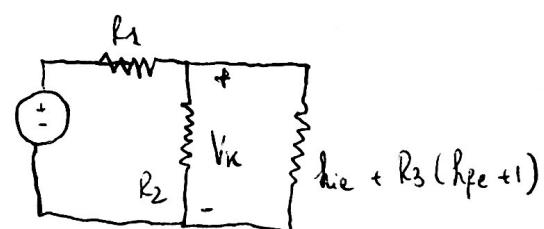
$$\bullet i_b = \frac{V_K}{h_{ie} + R_3 (h_{fe} + 1)}$$


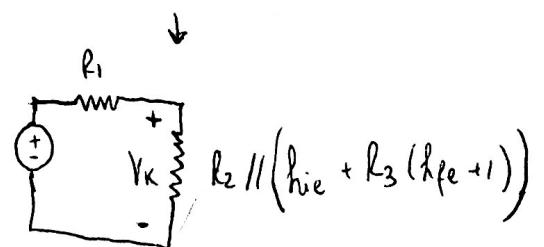
$$\bullet V_K = V_i \cdot \frac{R_2 \parallel (h_{ie} + R_3 (h_{fe} + 1))}{R_1 + R_2 \parallel (h_{ie} + R_3 (h_{fe} + 1))}$$


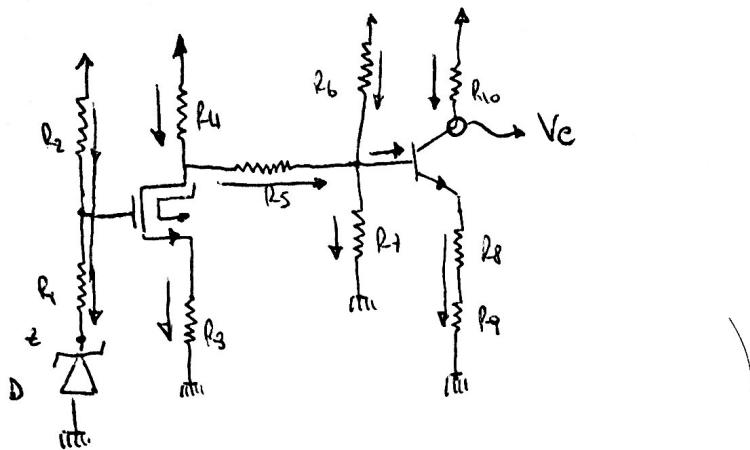
$$\bullet \frac{V_u}{V_i} = -g_m R_{12} \parallel R_{12} \cdot \frac{h_{fe} R_S R_8}{R_5 + R_6 + R_8 + (R_5 + R_6) R_8 g_m} \cdot \frac{1}{h_{ie} + R_3 (h_{fe} + 1)} \cdot \frac{R_2 \parallel (h_{ie} + R_3 (h_{fe} + 1))}{R_1 + R_2 \parallel (h_{ie} + R_3 (h_{fe} + 1))} = -1,73$$



$$\bullet I_c = \frac{V_{cc} - V_c}{R_{10}} = 2 \text{ mA}$$

IPOTEZI ZAD $I_c \gg I_B \rightarrow I \approx I_c = 2 \text{ mA}$

$$\bullet V_E = (R_8 + R_9) I_E = 5 \text{ V}$$

VERIFICO ZAD $\Rightarrow V_{ce} > V_{cesat} \rightarrow 5 \text{ V} > 0.2 \text{ V} \rightarrow \text{OK}$

$$\bullet I_B = \frac{I_c}{h_{FE}} = 6.8965 \mu\text{A}$$

$$\bullet V_{BE} = V_B - V_E \rightarrow V_B = V_E + V_{BE} = 5.7 \text{ V}$$

$$\bullet I_6 = \frac{V_{cc} - V_B}{R_6} = 20 \mu\text{A}$$

$$\bullet I_7 = \frac{V_B}{R_7} = 0.19 \text{ mA}$$

$$\bullet I_5 + I_6 = I_7 + I_B \rightarrow I_5 = I_7 + I_B - I_6 = 1.768965 \cdot 10^{-4} \text{ A}$$

$$\bullet U_D = R_5 I_5 + V_B = \frac{8151}{1160} = 7.026724 \text{ V}$$

$$\bullet I_u = \frac{V_{cc} - V_B}{R_4} = 3.376392573 \text{ mA}$$

$$\bullet I_D = I_u - I_5 = 3.199696021 \text{ mA}$$

$$\bullet I_a = 0 \rightarrow I_S = I_D = 0$$

IPOTEZZATO SATURAZIONE: $U_{as} = V_T + \sqrt{\frac{I_D}{k}} = 3.529622905 \text{ V}$

IPOTEZZATO ZENER IN BREAKDOWN $\Rightarrow U_Z = 3.6 \text{ V}$

$I_Z = \frac{V_{cc} - V_Z}{R_2 + R_1} = 2 \text{ mA} \rightarrow \text{VERIFICATA IPOTESI DI DIODO IN BREAKDOWN, poiché } I_Z > 0 \text{ da ANODO A CATHODE}$

$$\cdot V_{ce} = V_{ce} - R_2 I_2 = 6 \text{ V}$$

$$\cdot V_{os} = V_{ce} - V_s \rightarrow V_s = V_{ce} - V_{os} = 2.670377095 \text{ V}$$

VERIFICO SATURAZIONE: $V_{os} > V_{es} - V_T \rightarrow 9.697101233 \text{ V} > 2.529622905 \text{ V}$

$$\boxed{\cdot R_3 = \frac{V_s}{I_s} = 772,114 \Omega}$$

PUNTI DI LAVORO

$Q_1:$

$$I_o = 3.199696021 \text{ mA}$$

$$V_{os} = 9.697101233 \text{ V}$$

$$g_m = 2k |V_{es} - V_T| = 2.529622905 \frac{\text{mA}}{\text{V}}$$

$Q_2:$


$$I_c = 2 \text{ mA} \quad V_{ce} = 5 \text{ V} \quad h_{fe} = 300 \quad h_{re} = 290 \quad h_{re} = 6.8 \text{ k}\Omega$$

$D:$

$$V_2 = 3.6 \text{ V} \quad I_2 = 2 \text{ mA}$$

$$r_d = \frac{V_T}{I_2} = 13 \Omega$$

16/02/2015

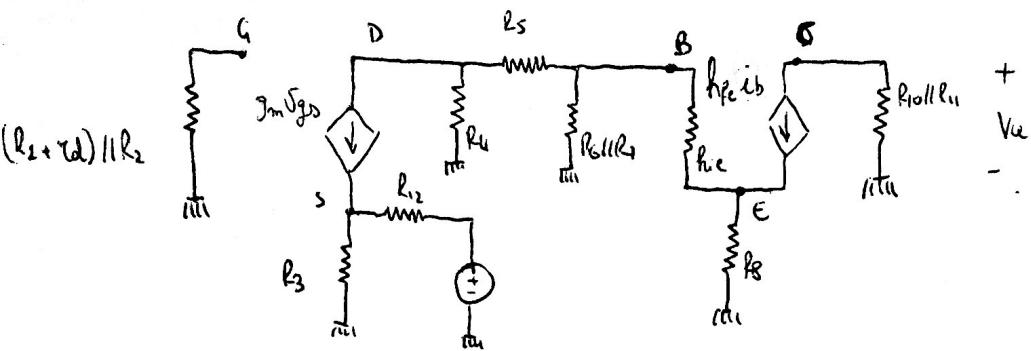

$$\bullet V_u = -h_{fe} i_b (R_{10} \parallel R_{11})$$

$$\bullet i_p = -g_m V_{gs} \frac{R_4}{R_u + R_S + R_p}$$

$$\bullet i_b = i_p \cdot \frac{R_6 \parallel R_7}{R_6 \parallel R_7 + R_S}$$

$$\bullet V_{gs} = V_g - V_S = -V_S$$

$$\left\{ \begin{array}{l} V_S = R_3 I_3 \\ V_S - V_i = R_{12} I_{12} \end{array} \right.$$

$$\left\{ \begin{array}{l} g_m V_{gs} = I_3 + I_{12} \rightarrow -g_m V_S = I_3 + I_{12} \end{array} \right.$$

$$-g_m V_S = \frac{V_S}{R_3} + \frac{V_S}{R_{12}} - \frac{V_i}{R_{12}} \rightarrow V_S \left(g_m + \frac{1}{R_3} + \frac{1}{R_{12}} \right) \rightarrow V_S = \frac{V_i}{R_{12}} \left(g_m + \frac{1}{R_3} + \frac{1}{R_{12}} \right)^{-1}$$

$$\bullet \frac{V_u}{V_i} = -h_{fe} \underbrace{\left(R_{10} \parallel R_{11} \right)}_{960000} \cdot \underbrace{\frac{R_4}{g_m}}_{3,105865793 \cdot 10^{-4}} \cdot \underbrace{\frac{R_6 \parallel R_7}{R_6 \parallel R_7 + h_{fe} + R_L (h_{fe} + 1)}}_{0,4506339567} \cdot \underbrace{\frac{1}{R_{12}} \left(g_m + \frac{1}{R_3} + \frac{1}{R_{12}} \right)^{-1}}_{0,8396628682} = [-112,74]$$

16/02/2015

①

ESEMPIO B)

$$Y = (\bar{A}C + \bar{B})(\bar{B}D + \bar{D}) + \bar{E}(\bar{B} + D)$$

$$Y = (\bar{A} + \bar{C} + \bar{B})(\bar{B}D + \bar{D}) + \bar{E}\bar{B} + D\bar{E}$$



$$Y = \bar{A}\bar{B}\bar{D} + \bar{A}\bar{D} + \bar{B}\bar{C}\bar{D} + \bar{C}\bar{D} + \bar{B}D + \bar{B}\bar{D} + \bar{B}\bar{E} + D\bar{E}$$

$$Y = \bar{A}\bar{B}\bar{D} + \bar{A}\bar{D} + \bar{B}\bar{C}\bar{D} + \bar{C}\bar{D} + \bar{B} + \bar{B}\bar{E} + D\bar{E}$$

$$Y = \bar{B}(\bar{A}\bar{D} + \bar{C}\bar{D} + 1 + \bar{E}) + \bar{A}\bar{D} + \bar{C}\bar{D} + D\bar{E}$$

$$Y = \bar{B} + \bar{D}(\bar{A} + \bar{C}) + D\bar{E}$$

14 mosfet

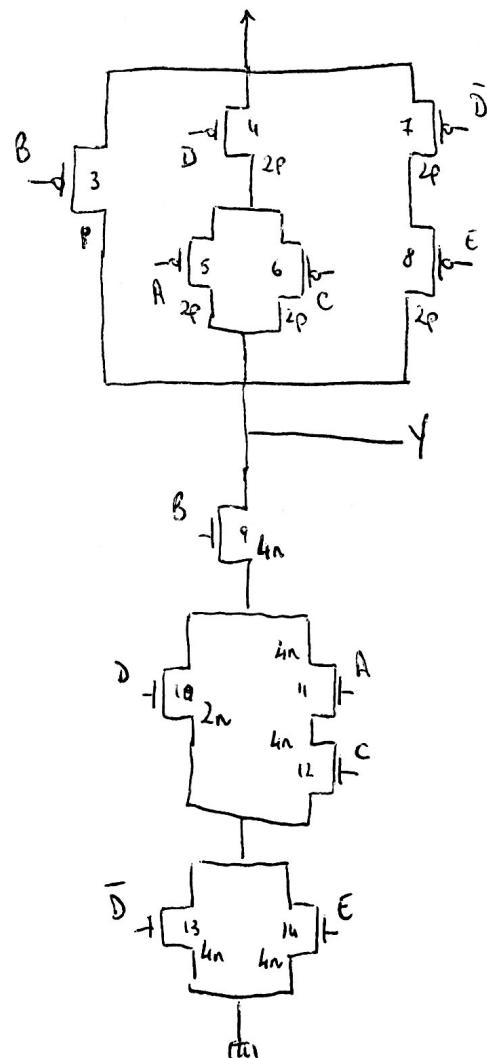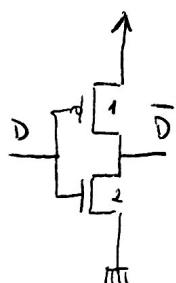

. INVERTER DI BASE

$$\left(\frac{W}{L}\right)_1 = P = 5$$

$$\left(\frac{W}{L}\right)_2 = n = 2$$

• PVN

WORST CASE : $Q_4, Q_5 \circ Q_6, Q_7 \circ Q_8, Q_9$

$$\left(\frac{W}{L}\right)_{4,5,6,7,8} = x$$

$$\frac{1}{x} + \frac{1}{x} = \frac{1}{p} \rightarrow \frac{2}{x} = \frac{1}{p} \rightarrow x = 2p = 10$$

WORST CASE ② Q_3 :

$$\left(\frac{W}{L}\right)_3 = y$$

$$\frac{1}{y} = \frac{1}{p} \rightarrow y = p = 5$$

• PDN:

WORST CASE : $Q_9, Q_{10}, Q_{12}, Q_{13} \circ Q_9, Q_{10}, Q_{12}, Q_{14}$

$$\left(\frac{W}{L}\right)_{9,10,12,13,14} = x$$

$$\frac{1}{x} + \frac{1}{x} + \frac{1}{x} + \frac{1}{x} = \frac{1}{n} \rightarrow \frac{4}{x} = \frac{1}{n} \rightarrow x = 4n = 8$$

WORST-CASE ② : $Q_9, Q_{10}, Q_{13} \rightarrow$ Now POSSIBLE CASE PRESENTLY $D = \overline{0}$
 Q_9, Q_{10}, Q_{14}

$$\left(\frac{W}{L}\right)_{10} = y$$

$$\frac{1}{y} + \frac{1}{y} + \frac{1}{y} = \frac{1}{n} \rightarrow \frac{3}{y} = \frac{1}{4n} \rightarrow \frac{1}{y} = \frac{1}{12n} \rightarrow y = 12n = 4$$

16/02/2015


①

ESEMPIO 2 c)

$$Q_1 = 1 \rightarrow Q_2 = \text{ON}$$


$$\cdot U_{G_2} = V_{cc} \quad U_{S_2} = 0V \quad U_{GS_2} = V_{cc} - 6V > V_T = 1V \quad Q_2 = \text{ON}$$
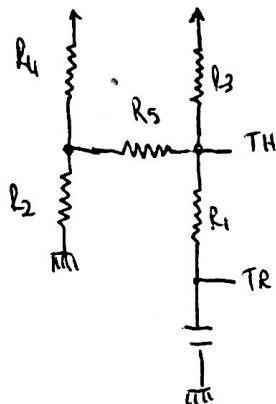
$$\cdot U_{G_1} = 0V \quad U_{S_1} = 0V \quad U_{GS_1} = 0V < V_T = 1V \quad Q_1 = \text{OFF}$$



$$\boxed{\cdot I_i = \frac{1}{3} V_{cc} = 2V}$$

Applico Thévenin

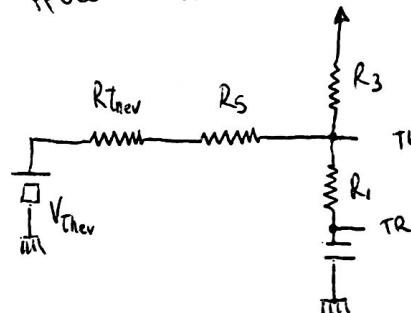

$$U_{\text{Thevenin}} = V_{cc} \cdot \frac{R_2}{R_2 + R_4} = 3V \quad R_{\text{Thevenin}} = R_2 // R_4 = 1000 \Omega$$

$\cdot V_f \rightarrow$ se non nasce collegate sul condensatore

$$I = \frac{V_{cc} - V_{\text{Thevenin}}}{R_3 + R_S + R_{\text{Thevenin}}} = 1,5 \text{ mA}$$

$$\boxed{V_f = V_{cc} - R_3 I = 6,95 V}$$

$$\cdot V_{\text{comm}} \quad \text{se} \quad U_{TH} = \frac{2}{3} V_{cc} = 6V$$

$$I_3 = \frac{V_{cc} - V_{TH}}{R_3} = \frac{1}{350} A \quad I_{\text{Thevenin}} = \frac{V_{TH} - V_{\text{Thevenin}}}{R_S + R_{\text{Thevenin}}} = \frac{1}{1300} A \quad I_1 = I_3 - I_{\text{Thevenin}} = \frac{19}{9100} A$$

$$\cdot V_{\text{comm}} = V_{TH} - R_1 \cdot I_1 = \frac{269}{91} V$$

 $\rightarrow \text{OK}$ VERIFICO CHE $U_i \approx V_{\text{comm}} \approx V_f$

$$\bar{T}_1 = T_1 \ln \left(\frac{U_i - V_f}{U_{\text{comm}} - V_f} \right)$$


$$T_1 = R_{V_1} \cdot C = \left[R_1 + R_3 // (R_S + R_{\text{Thevenin}}) \right] \cdot C = 955 \cdot C = 6,496 \cdot 10^{-5} \text{ s}$$

$$T_1 = 2,563599624 \cdot 10^{-5} \text{ s}$$

$$Q_1 = 0 \rightarrow D = 0$$

$$U_{C_2} = 0V \quad U_{S_2} = 0V \quad U_{ES_2} = 0V < U_T = 1V \quad Q_2 \text{ OFF}$$
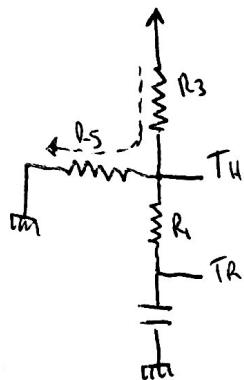
$$U_{E1} = V_{cc} \quad U_{S_1} = 0V \quad U_{ES_1} = V_{cc} = 6V > U_T = 1V \quad Q_1 \text{ ON}$$



$$\cdot U_i = \frac{269}{91} V$$

$$\cdot U_{comu} = 2V$$

$$\cdot U_f = V_{cc} - \frac{R_S}{R_3 + R_S} = \frac{9}{5} V = 1,8 V$$

VERIFICO CHE $U_i > U_{comu} > U_f \rightarrow OK$

$$T_2 = T_2 \ln \left(\frac{U_i - U_f}{U_{comu} - U_f} \right)$$

$$T_2 = R_{V_2} \cdot C = [R_1 + R_3]/R_S \cdot C = 710 \cdot C = 6,828 \cdot 10^{-5} \rightarrow$$


$$T_2 = 6,828 \cdot 10^{-5} \text{ s}$$

$$T = T_1 + T_2 = 1,101606398 \cdot 10^{-4} \text{ s}$$

$$\boxed{f = \frac{1}{T} = 9079,31 \text{ Hz}}$$

27/01/2015

(1)

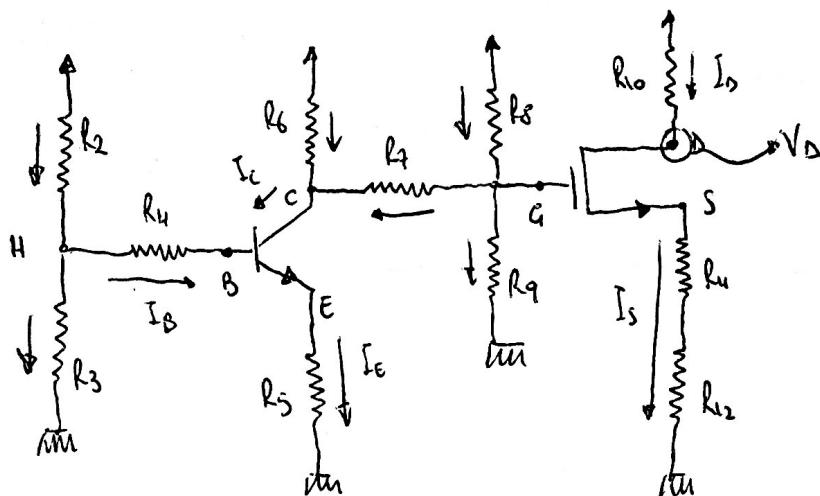

$$V_o = 12 \text{ V}$$

$$R_3 = 2 \text{ k}\Omega$$

- $I_D = I_{10} = \frac{V_{ce} - V_o}{R_{10}} = 8 \text{ mA}$

- $I_E = 0 \Rightarrow I_S = I_D$

- $V_S = (R_{11} + R_{12}) I_S = 5 \text{ V}$

- $V_{ces} = V_T \pm \sqrt{\frac{I_D}{K}} \rightarrow \text{scelgo } V_{ces} = V_T + \sqrt{\frac{I_D}{K}} \text{ perché deve valere } V_{ces} > V_T > 0$

- $V_{ces} = 5 \text{ V}$

- $V_{ces} - V_a - V_S \Rightarrow V_a = V_{ces} + V_S = 10 \text{ V}$

VERIFICO LA SATURAZIONE $[V_{os} > V_{ei} - V_T \text{ ovvero } T > h]$ ✓

- $I_B = \frac{V_{ce} - V_a}{R_8} = 1 \text{ mA}$

- $I_Q = \frac{V_a}{R_9} = 0.5 \text{ mA}$

- $I_T = I_B - I_Q = 0.5 \text{ mA}$

- $V_a - V_c = R_7 I_T \Rightarrow V_c = V_a - R_7 I_T = 9 \text{ V}$

- $I_6 = \frac{V_{ce} - V_c}{R_6} = 1.5 \text{ mA}$

- $I_C = I_T + I_6 = 2 \text{ mA}$

(2)

$$1 \text{ PNP1220 } 2.\text{A.D} \Rightarrow I_B \ll I_C \Rightarrow I_E \approx I_C$$

$$\cdot V_E = R_S \cdot I_E = 1. \text{V}$$

$$\text{VERIFICO 2.A.D } [V_{CE} > V_{CE,\text{SAT}} \text{ overo } S > 0.2 \text{ V}]$$

Quindi so che: $h_{FE} = 300$ $h_{FE} = 290$ $h_{ie} = 1.8 \text{ k}\Omega$

$$\cdot I_B = \frac{I_C}{h_{FE}} = 6.8965 \mu\text{A}$$

$$\cdot V = V_{BE} + V_E = 4.7 \text{ V}$$

$$\cdot V_H = V_B + R_H I_B = 4.768965 \text{ V}$$

$$\cdot I_2 = \frac{V_{CC} - V_H}{R_2} = 22.051725 \mu\text{A}$$

$$\cdot I_3 = I_2 - I_B = 15.155225 \mu\text{A}$$

$$\boxed{\cdot R_3 = \frac{V_H}{I_3} = 314674,64}$$


Q_1
 $h_{FE} = 290$ $h_{ie} = 1.8 \text{ k}\Omega$ $h_{FE} = 300$ $I_C = 2 \text{ mA}$ $V_{CE} = 5 \text{ V}$

Q_2
 $I_D = 8 \text{ mA}$ $V_{DS} = 7 \text{ V}$ $g_m = |2k(V_{GS} - V_T)| = 4 \text{ mA/V}$

2)

27/01/2015

③

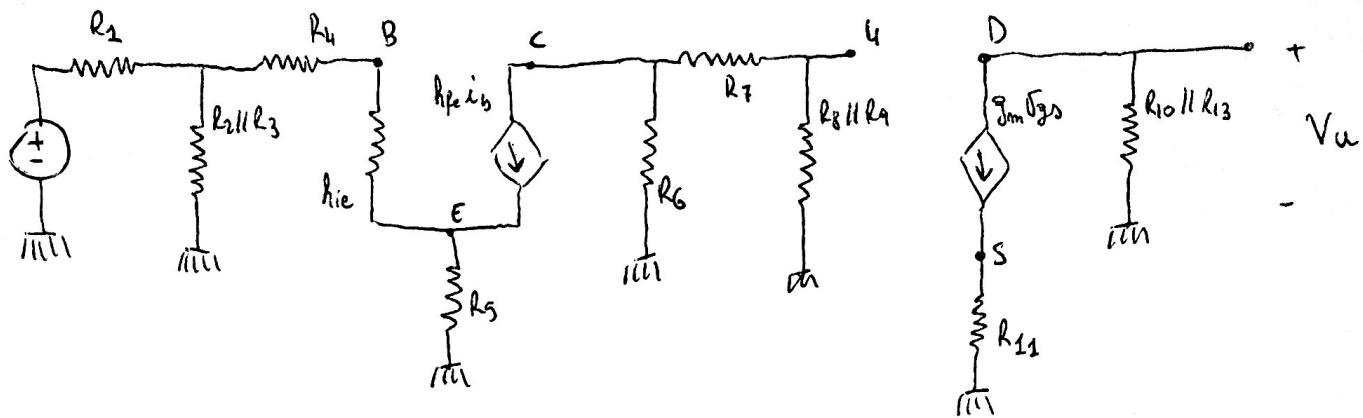

$$\cdot V_u = -g_m V_{gs} \cdot R_{10} // R_{13}$$


$$\cdot V_{gs} = V_g - V_s = V_g - g_m V_{gs} R_{11} \Rightarrow V_{gs} = \frac{V_g}{1 + g_m R_{11}}$$

$$\cdot V_g = -h_{fe} i_b \frac{R_6}{R_6 + R_7 + R_8 // R_9} \cdot R_8 // R_9$$


$$\cdot i_b = \frac{V_K}{R_S}$$

$$\cdot V_K = V_i \cdot \frac{(R_2 // R_3) // R_S}{1 + (R_2 // R_3) // R_S}$$
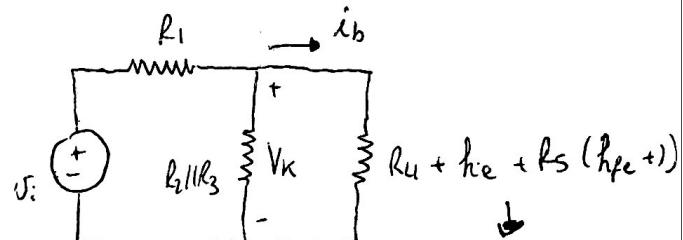
$$\cdot \frac{V_u}{V_i} = g_m R_{10} // R_{13} \cdot \frac{1}{1 + g_m R_{11}} \cdot \frac{h_{fe} R_6 R_8 // R_9}{R_6 + R_7 + R_8 // R_9} \cdot \frac{1}{R_S} \cdot \frac{(R_2 // R_3) // R_S}{1 + (R_2 // R_3) // R_S} = \boxed{3.08}$$




$$R_S = R_4 + h_{ie} + R_5 (h_{fe} +)$$

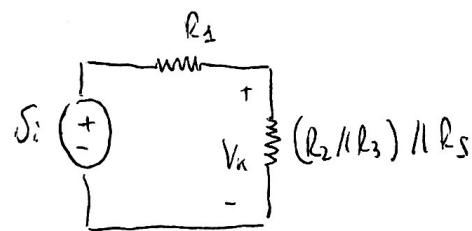

9/04/2015

EJERCICIO A)

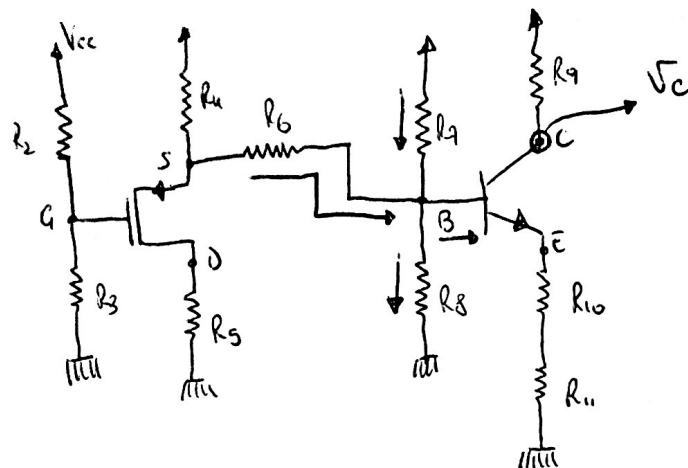

$$\bullet I_q = \frac{V_{cc} - V_c}{R_9} = 2 \text{ mA} = I_c$$

$$\text{SUSTENIENDO Z.A.D} \Rightarrow I_c \gg I_b \Rightarrow I_c = I_e = 2 \text{ mA}$$

$$\bullet V_E = (R_{10} + R_{11}) I_E = 8 \text{ V}$$

$$\bullet V_{BE} = V_B - V_E \Rightarrow V_B = V_{BE} + V_E = 8.7 \text{ V}$$

$$\bullet \text{VERIFICANDO ZAD} \rightarrow V_{BE} > V_{CESAT} \rightarrow 5 > 0.2 \text{ OK}$$

$$\bullet I_B = \frac{I_C}{h_{FE}} = 6.8965 \mu\text{A}$$

$$\bullet I_7 = \frac{V_{cc} - V_B}{R_7} = 20 \mu\text{A}$$

$$\bullet I_8 = \frac{V_B}{R_8} = 0.435 \text{ mA} = 435 \mu\text{A}$$

$$\bullet I_7 + I_6 = I_8 + I_B \Rightarrow I_6 = I_8 + I_B - I_7 = 421.8965 \mu\text{A}$$

$$\bullet V_S - V_B = R_6 I_6 \Rightarrow V_S = V_B + R_6 I_6 = 12.918965 \text{ V}$$

$$\bullet I_4 = \frac{V_{cc} - V_S}{R_4} = 5.0811 \text{ mA}$$

$$\bullet I_S = I_4 - I_6 = 4.6592 \text{ mA}$$

$$\bullet I_D = I_S = 4.6592 \text{ mA}$$

$$\bullet V_D = I_S \cdot R_S = 4.6592 \text{ V}$$


$$\bullet V_{us} = V_i - \sqrt{\frac{I_D}{K}} = -3.1585 \text{ V}$$

VERIFY SATUR. ZONE : $V_{DS} < V_{DS} - V_T \rightarrow -8,259 < -2,1585$ OK (2)

• $V_{DS} = U_C - U_S \Rightarrow U_a = U_{DS} \cdot U_S = 16,000 - 9,760,665 \text{ V}$


• $I_2 = \frac{U_{CC} - U_A}{R_2} = 0,82395 \text{ mA}$

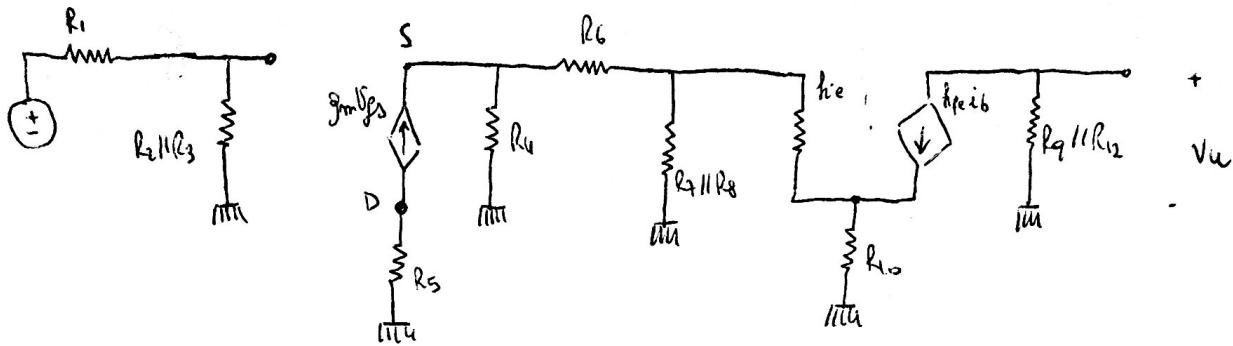• $R_3 = \frac{U_A}{I_2} = 11865,94 \Omega$





$$\cdot V_u = - h_{fe} i_b \cdot (R_q || R_{12})$$
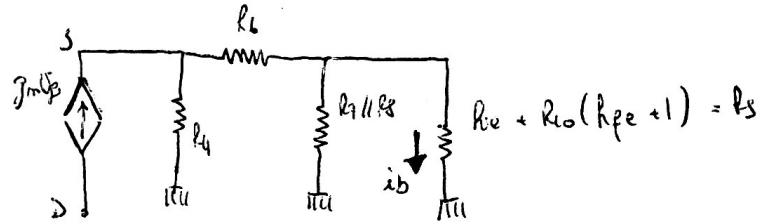
$$\cdot i_p = g_m V_{gs} \cdot \frac{R_4}{R_6 + R_p + R_u}$$



$$\cdot i_b = i_p \cdot \frac{R_7 || R_8}{R_s + R_7 || R_8}$$

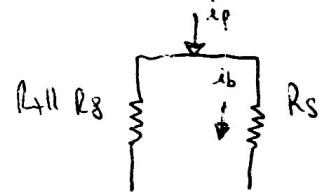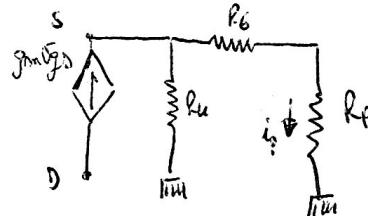

$$\cdot V_{gs} = V_g - V_d$$

$$\cdot I_u = g_m V_{gs} \cdot \frac{R_6 + R_p}{R_u + R_6 + R_p}$$

$$\cdot J_g = \cancel{R_2 \cdot g_m V_g} \quad R_u \cdot I_u = R_u \cdot g_m V_{gs} \cdot \frac{R_6 + R_p}{R_u + R_6 + R_p}$$

$$\cdot J_{gs} = V_g - R_u g_m V_{gs} \frac{R_6 + R_p}{R_u + R_6 + R_p} = J_g - g_m R_u \cdot R_{eq1} \cdot V_{gs} \Rightarrow V_{gs} = \frac{V_g}{1 + g_m R_{eq1} R_u}$$

$$\cdot J_g = V_i \cdot \frac{R_2 || R_3}{R_1 + R_2 || R_3}$$

$$\cdot \underline{\underline{V_u}} = - h_{fe} (R_q || R_{12}) \cdot \frac{R_7 || R_8}{R_s + R_7 || R_8} \cdot g_m \frac{R_u}{R_6 + R_u + R_p} \cdot \frac{1}{1 + g_m R_{eq1} R_u} \cdot \frac{R_2 || R_3}{R_1 + R_2 || R_3}$$

9/01/2015

(1)

$$Y = (\bar{A} + C)(\bar{C}D + \bar{D}E) + (\bar{D} + \bar{E})(A + B\bar{C}) + B\bar{C} + \bar{D}E$$

$$Y = (A \cdot \bar{C})(\bar{C}D + \bar{D}E) + (\bar{D} \cdot \bar{E})(A + B\bar{C}) + B\bar{C} + \bar{D}E$$



$$Y = A\bar{C}D + A\bar{C}\bar{D}E + A\bar{D}E + B\bar{C}\bar{D}E + B\bar{C} + \bar{D}E$$

$$Y = A\bar{D}E + A\bar{C}D + B\bar{C}\bar{D}E + B\bar{C} + \bar{D}E$$

$$Y = A\bar{C}D + A\bar{D}E + B\bar{C}(1 + \bar{D}E) + \bar{D}E \quad , \quad Y = A\bar{D}E + A\bar{C}D + B\bar{C} + \bar{D}E(1 + B\bar{C})$$

$$Y = A\bar{C}D + \bar{D}E(1 + A) + B\bar{C}$$
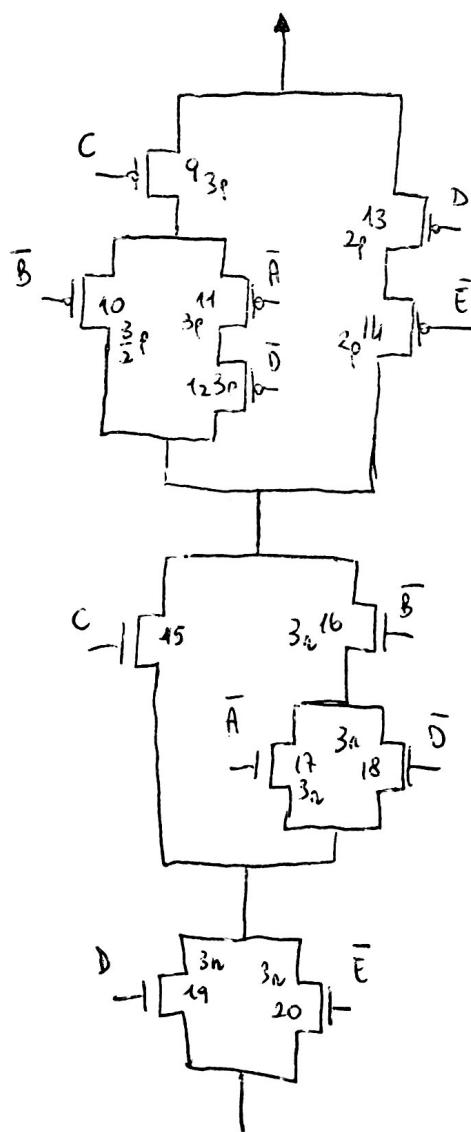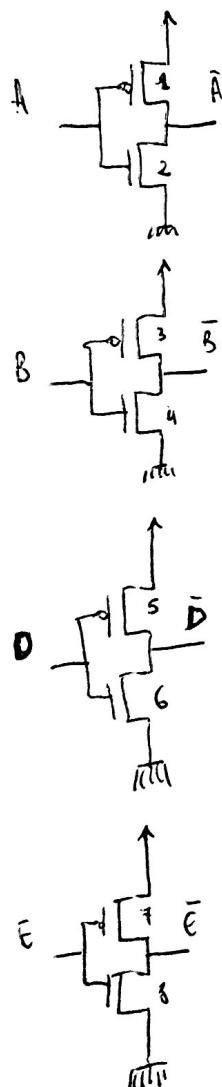
$$Y = B\bar{C} + \bar{D}E + A\bar{C}D = \bar{C}(B + AD) + \bar{D}E$$



INVERTER

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_7 = p = 5$$

$$\left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_6 = \left(\frac{W}{L}\right)_8 = n = 2$$

PDN

- WORST CASE Q_9, Q_{12}, Q_{11}

$$\left(\frac{W}{L}\right)_9 = \left(\frac{W}{L}\right)_{11} = \left(\frac{W}{L}\right)_{12} = x$$

$$\frac{1}{x} + \frac{1}{x} + \frac{1}{x} = \frac{1}{p} \Rightarrow \frac{3}{x} = \frac{1}{p} \Rightarrow x = 3p$$

- WORST CASE 2 : $Q_{13}, Q_{14} \Rightarrow Q_9 - Q_{10}$

$$\left(\frac{W}{L}\right)_{13} = \left(\frac{W}{L}\right)_{14} = 4$$

$$\frac{1}{4} + \frac{1}{4} = \frac{1}{p} \Rightarrow \frac{2}{4} = \frac{1}{p} \Rightarrow 4 = 2p$$

$$\left(\frac{W}{L}\right)_9 = 3p \quad \left(\frac{W}{L}\right)_{10} = z$$

$$\frac{1}{z} + \frac{1}{3p} = \frac{1}{p} \rightarrow \frac{1}{z} = \frac{2}{3p} \Rightarrow z = \frac{3}{2}p$$

• PDN

- WORST CASE : $Q_{16}, Q_{17}, Q_{19} \Rightarrow Q_6, Q_7, Q_8 \Rightarrow Q_{16}, Q_{18}, Q_{20}$ Q_{16}, Q_{18}, Q_{19} non si puo' ferire sono presenti $D = \bar{D}$

$$\left(\frac{W}{L}\right)_{16} = \left(\frac{W}{L}\right)_{17} = \left(\frac{W}{L}\right)_{19} = x$$

$$\frac{1}{x} + \frac{1}{x} + \frac{1}{x} = \frac{1}{n} \Rightarrow x = 3n$$

$$\left(\frac{W}{L}\right)_{16} = \left(\frac{W}{L}\right)_{17} = 3n \quad \left(\frac{W}{L}\right)_{20} = 4$$

$$\frac{1}{4} + \frac{1}{3n} + \frac{1}{3n} = \frac{1}{n} \rightarrow \frac{1}{4} = \frac{1}{n} - \frac{2}{3n} \rightarrow \frac{1}{4} = \frac{1}{3n} \rightarrow 4 = 3n$$

- WORST CASE 2 : $Q_{15}, Q_{19} \Rightarrow Q_{15}, Q_{20}$

$$\left(\frac{W}{L}\right)_{15} = z \quad \left(\frac{W}{L}\right)_{19} = 3n$$


$$\frac{1}{z} + \frac{1}{3n} = \frac{1}{n} \rightarrow z = \frac{3}{2}n$$

9/01/2015

①

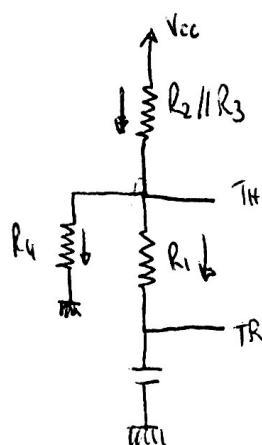EJERCICIO C)

$$Q_i = 1 \rightarrow D = 1/2 \rightarrow Q_1 = ON$$



$$\bullet V_i = \frac{1}{3} V_{cc} = 2V$$

$$\bullet V_f = V_{cc} \frac{R_4}{R_4 + R_2/R_3} = 5,6782 V = \frac{126}{23} V$$

$$V_{common} \neq 0 \text{ calcula con } V_{TH} = \frac{2}{3} V_{cc} = 4V$$

$$I_{213} = \frac{V_{cc} - V_{TH}}{R_2/R_3} = \frac{21}{1500} A$$

$$I_u = \frac{V_{TH}}{R_4} = \frac{4}{1000} A \rightarrow I_1 = I_{213} - I_u = \frac{17}{1000} A$$

$$\bullet V_{common} = V_{TH} - R_1 I_1 = \frac{63}{20} V = 3.15$$

VERIFICO CHE: $V_i < V_{common} < V_f \rightarrow OK$


$$T_1 = T_1 \ln \left(\frac{V_i - V_f}{V_{common} - V_f} \right) =$$

$$T_1 = R_{V_1} \cdot C = \left[R_1 + R_2/R_3/R_4 \right] \cdot C = \frac{3150}{23} \cdot C = \frac{63}{460000} \text{ s} \approx 1,36956 \cdot 10^{-4} \text{ s}$$

$$T_1 = 5,6975832 \cdot 10^{-5} \text{ s}$$

$$Q = 0 \rightarrow D = 0 \rightarrow Q_1 = \text{OFF}$$

(2)

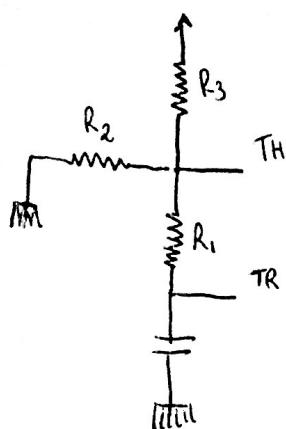

- $V_i = 3.15 \text{ V}$
- $V_{\text{com}} = 2 \text{ V}$
- $V_f = V_{\text{cc}} \cdot \frac{R_2}{R_2 + R_3} = \frac{2}{7} \text{ V}$

VERIFICO CHE $V_i > V_{\text{com}} > V_f \rightarrow \text{OK}$

$$T_2 = \tau_b \ln \left(\frac{V_i - V_f}{V_{\text{com}} - V_f} \right)$$

$$T_2 = R_{V_2} \cdot C = [R_1 + R_2 // R_3] \cdot C = \frac{3050}{21} \cdot C = \frac{61}{420000} \text{ s} \approx 1.4523809 \cdot 10^{-4} \text{ s}$$

$$T_2 = \frac{2.5571809}{7.155398272} \cdot 10^{-5} \text{ s}$$


$$T = T_1 + T_2 = 5.155355009 \cdot 10^{-5} \text{ s} \quad 1.295298147 \cdot 10^{-4} \text{ s}$$

$f = \frac{1}{T} = 7720 \text{ Hz}$

15/09/2014

1

(EXERCICIO A)

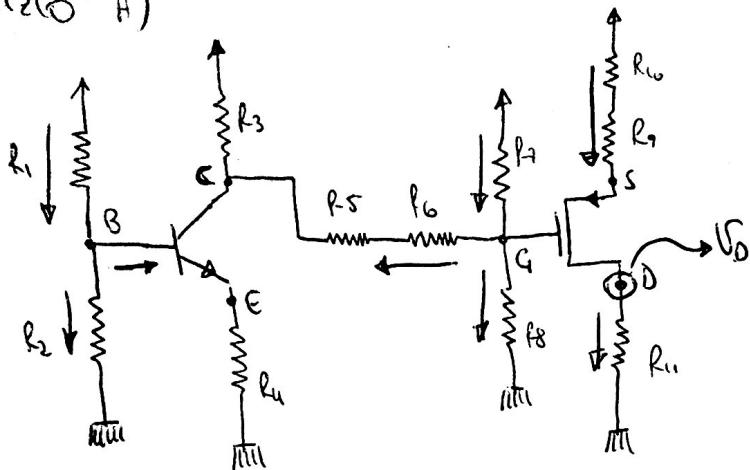

- $I_D = \frac{V_D}{R_{11}} = 4.5 \text{ mA}$
- $I_G = 0 \Rightarrow I_S = I_D = 4.5 \text{ mA}$
- $U_S = U_{CC} - (R_4 + R_{10}) I_S = 13.5 \text{ V}$
- $U_{DS} = -V_T - \sqrt{\frac{2\alpha}{K}} = -1 - \sqrt{4} = -4 \text{ V}$
- VERIFICO LA SATURAZIONE $U_{DS} < U_{DS} - V_T \rightarrow -6.3 < -3 \text{ OK}$
- $U_{GS} = U_G - U_S \rightarrow U_G = U_{GS} + U_S = 9.5 \text{ V}$
- $I_7 = \frac{U_{CC} - U_G}{R_7} = 2 \text{ mA}$
- $I_8 = \frac{U_G}{R_8} = 0.5 \text{ mA}$
- $I_5 = I_7 - I_8 = 1.5 \text{ mA}$
- $U_C = U_G - (R_5 + R_6) I_5 = 8 \text{ V}$
- $I_3 = \frac{U_{CC} - U_C}{R_3} = 0.5 \text{ mA}$
- $I_C = I_3 + I_5 = 2 \text{ mA}$
- SUPONIARO Z.A.D $I_C \gg I_B \Rightarrow I_E \approx I_C = 2 \text{ mA}$
- $U_E = R_E \cdot I_E = 3 \text{ V}$
- VERIFICARO Z.A.D $U_E > U_{ESAT} \rightarrow 5 \text{ V} > 0.2 \text{ V OK}$
- $I_B = \frac{I_C}{h_{FE}} = 6.8965 \mu\text{A}$

$$\bullet V_{BE} = U_B - U_E \Rightarrow I_B \cdot (U_E + U_{BE}) = 3,7 \text{ V}$$

$$\bullet J_1 = \frac{U_{CC} - U_B}{R_1} = 20 \mu\text{A}$$

$$\bullet J_2 = J_1 \cdot J_3 = 13,1035 \mu\text{A}$$

$$\bullet f_2 = \frac{U_B}{J_2} = 282367,3066 \Omega$$

PUNTI DI FILOJO

Q_1 :


$$h_{FE} = 300 \quad h_{FEE} = 290 \quad h_{ie} = 6,8 \text{ k}\Omega \quad I_c = 2 \text{ mA} \quad U_{UE} = 5 \text{ V}$$

Q_2 :

$$I_D = 6,5 \text{ mA} \quad U_{DS} = -6,3 \text{ V} \quad g_m = 2k |U_{DS} \cdot U_T| = 3 \frac{\text{mA}}{\text{V}}$$

15/09/2016

(3)

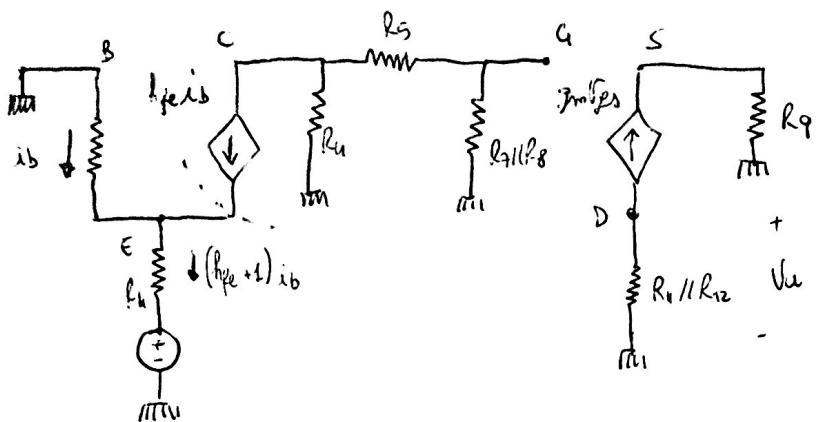

$$\cdot \bar{V}_a = -g_m \bar{V}_{gs} (R_1 || R_{12})$$


$$\cdot \bar{V}_{gs} = \bar{V}_g - \bar{V}_s = \bar{V}_g - g_m \bar{V}_{gs} R_9 \rightarrow \bar{V}_{gs} = \frac{\bar{V}_g}{1 + g_m R_9}$$

$$\cdot \bar{V}_g = -h_{fe} i_b \cdot \frac{R_3}{R_3 + R_5 + R_7 || R_8} \cdot R_7 || R_8$$

$$\cdot (h_{fe}+1) i_b = - \frac{\bar{V}_i}{R_4 + \frac{h_e}{h_{fe}+1}}$$

$$\cdot (h_{fe}+1) i_b = - \frac{\bar{V}_i}{\frac{(h_{fe}+1) R_4 + h_e}{h_{fe}+1}} \rightarrow i_b = - \frac{\bar{V}_i}{h_{fe} + R_4 (h_{fe}+1)}$$

$$\cdot \frac{\bar{V}_u}{\bar{V}_i} = - g_m (R_1 || R_{12}) \cdot \frac{1}{1 + g_m R_9} \cdot h_{fe} \frac{R_3 \cdot (R_7 || R_8)}{R_3 + R_5 + R_7 || R_8} \frac{1}{h_{fe} + R_4 (h_{fe}+1)} = \boxed{-6,1665}$$

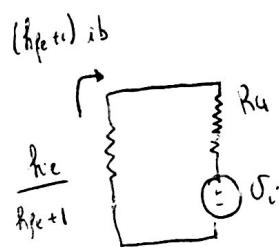

EXERCISE B)

15/09/2014

$$Y = \overline{BC} (\bar{A} + D + \bar{E}) + \bar{B}(\bar{D} + AC) + CD$$



$$Y = (\bar{B} + \bar{C})(\bar{A} + D + \bar{E}) + \bar{B}\bar{D} + A\bar{B}C + CD$$

$$Y = \bar{A}\bar{B} + \bar{B}\bar{D} + \bar{B}\bar{E} + \bar{A}\bar{C} + \bar{E}D + \bar{C}\bar{E} + \bar{B}\bar{D} + \bar{A}\bar{B}C + CD$$

$$Y = \bar{B} + D + \bar{A}\bar{B} + \bar{B}\bar{E} + \bar{A}\bar{C} + \bar{C}\bar{E} + A\bar{B}C$$

$$Y = \bar{B}(1 + \bar{A} + \bar{E} + AC) + D + \bar{A}\bar{C} + \bar{C}\bar{E}$$
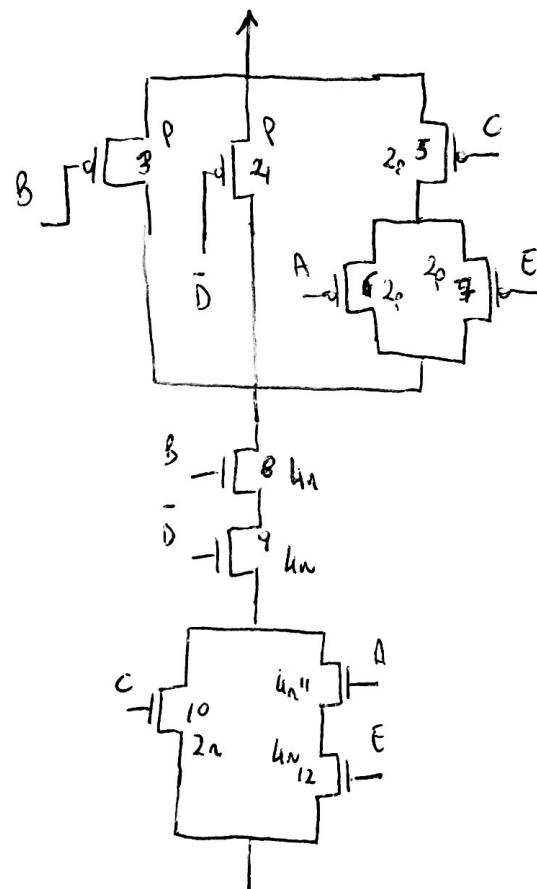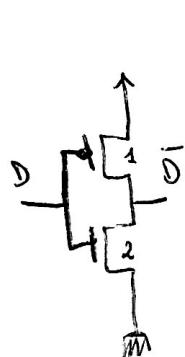
$$Y = \bar{B} + \bar{D} + \bar{C}(\bar{A} + \bar{E})$$



• INVERTER ON BASE

$$\left(\frac{W}{L}\right)_1 = R = 5$$

$$\left(\frac{W}{L}\right)_2 = n = 2$$

• PUN

- WORST CASE : $Q_5, Q_6 \circ Q_5, Q_9$

$$\left(\frac{W}{L}\right)_{5} = \left(\frac{W}{L}\right)_6 = x$$

$$\text{and } \left(\frac{W}{L}\right)_7 = 2p = 10$$

$$\frac{1}{x} + \frac{1}{x} = \frac{1}{p} \Rightarrow 2x = 2p = 10$$

- WORST CASE : $Q_3 \circ Q_u$

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_u = y$$

$$\frac{1}{y} = \frac{1}{p} \Rightarrow y = p = 5$$

• PDN

- WORST CASE : Q_8, Q_9, Q_u, Q_{12}

$$\left(\frac{W}{L}\right)_{8,9,11,12} = x$$

$$\frac{1}{x} + \frac{1}{x} + \frac{1}{x} + \frac{1}{x} = \frac{1}{n} \rightarrow \frac{4}{x} = \frac{1}{n} \rightarrow x = 4n = 8$$

- WORST CASE : Q_8, Q_9, Q_{10}

$$\left(\frac{W}{L}\right)_{8,9} = 4n \quad \left(\frac{W}{L}\right)_{10} = y$$


$$\frac{1}{4n} + \frac{1}{4n} + \frac{1}{y} = \frac{1}{n} \rightarrow \frac{1}{y} = \frac{1}{n} - \frac{1}{2n} \rightarrow \frac{1}{y} = \frac{1}{2n} \rightarrow y = 2n = 4$$

$$Q_1 = 1 \rightarrow D = 'H2$$

~~OFF~~ ~~ON~~

$$U_{g1} = 0 \rightarrow U_{S1} = 0 \Rightarrow U_{GS} = 0 \text{ V} < U_{T1} = 1 \text{ V} \Rightarrow Q_1 = OFF$$
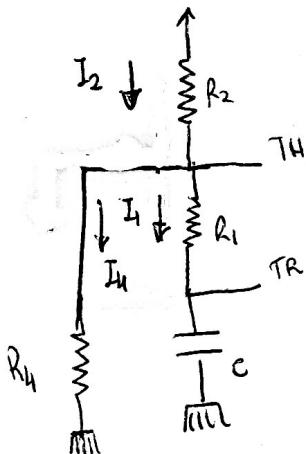
$$U_{g2} = 0 \rightarrow U_{S2} = U_{CC} \rightarrow U_{ES2} = -U_{CC} < U_{T2} = -1 \text{ V} \Rightarrow Q_2 = ON$$



$$\bullet U_i = \frac{1}{3} V_{CC} = 2 \text{ V}$$

$$\bullet V_f = V_{CC} - \frac{R_u}{R_u + R_2} = 5 \text{ V}$$

$$\bullet U_{comm} \text{ con } U_{TH} = \frac{2}{3} V_{CC} = 4 \text{ V}$$

$$I_2 = \frac{V_{CC} - U_{TH}}{R_2} = 2 \text{ mA} \quad I_4 = \frac{V_{TH}}{R_u} = 8 \cdot 10^{-4} \text{ A}$$

$$V_{comm} = U_{TH} - R_1 I_2 = V_{TH} - R_1 (I_2 - I_u) = 2.8 \text{ V}$$

VERIFICO CHE: $U_i < U_{comm} < V_f \rightarrow OK$

$$T_2 = T_1 \ln \left(\frac{U_i - V_f}{U_{comm} \cdot V_f} \right)$$

$$T_1 = R_u \cdot C = [R_1 + R_2 / (R_u)] \cdot C = \frac{5500}{3} \cdot C = \frac{11}{60000} \text{ s}$$


$$T_2 = 5.68617 \cdot 10^{-5} \text{ s}$$

$$Q = 0 \rightarrow D = 0$$

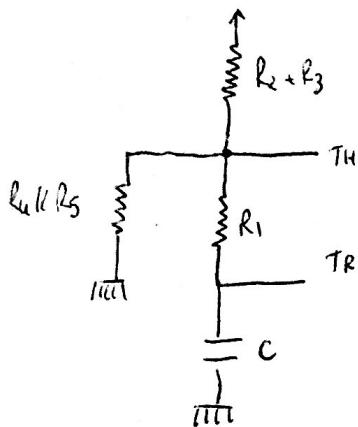(2)

$$U_{G_1} = V_{CC} \quad U_S = 0V \quad U_{GS} = V_{CC} = 6V > U_{T_1} = 1V \Rightarrow Q_1 = ON$$

$$U_{G_2} = V_{CC} \quad U_S = V_{CC} \quad U_{GS_2} = 0V > U_{T_2} = -1V \Rightarrow Q_2 = OFF$$



$$\bullet U_i = 2.8V$$

$$\bullet U_{GS_{min}} = 2V$$

$$\bullet U_f = V_{CC} \cdot \frac{R_4 \parallel R_5}{R_2 + R_3 + R_4 \parallel R_5} = \frac{3}{5} = 0.6V$$

VERIFICO CHE $U_i > U_{GS_{min}} > U_f \rightarrow OK$

$$T_2 = T_2 \ln \left(\frac{U_i - U_f}{U_{GS_{min}} - U_f} \right)$$

$$T_2 = R_{V_2} \cdot C = \left[R_1 + (R_2 + R_3) \parallel (R_4 \parallel R_5) \right] \cdot C = 3250 \cdot C = \frac{13}{60000} s$$

$$T_2 = 1.4689516 \cdot 10^{-4} s$$


- - -

$$T = T_1 + T_2 = 2.037568 \cdot 10^{-4} s$$

$$f = \frac{1}{T} = 4907.81 \text{ Hz}$$

21/07/2014

1

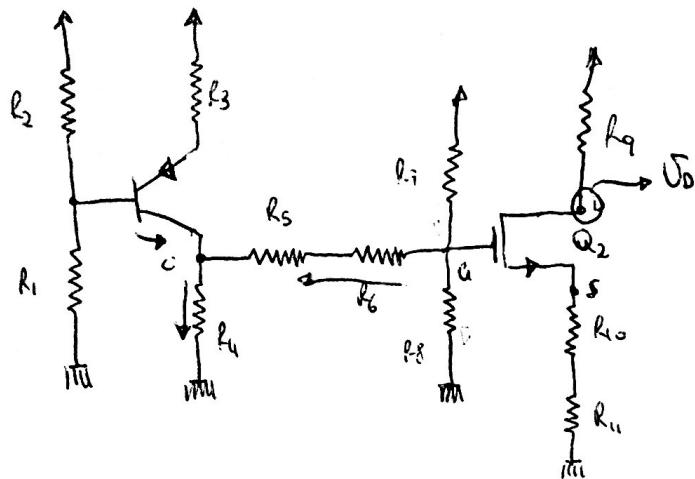

- $I_D = \frac{V_{CC} - V_D}{R_D} = 1 \text{ mA} = I_D$
- $I_a = 0 \rightarrow I_S = 1 \text{ mA} = I_0$
- $V_S = (R_{10} + R_{11}) I_S = 4 \text{ V}$
- $V_{DS} = V_T + \sqrt{\frac{I_D}{k}} = 5 \text{ V}$
- VERIFICO SATURAZIONE: $V_{DS} > V_{DS} \cdot V_T \rightarrow 6 > 4 \text{ OK}$
- $V_{DS} = V_a \cdot V_S \rightarrow V_a = V_{DS} + V_S = 9 \text{ V}$
- $I_T = \frac{V_{CC} - V_a}{R_T} = 1 \text{ mA}$
- $I_B = \frac{V_a}{R_B} = 0.5 \text{ mA}$
- $I_6 = I_T - I_B = 0.5 \text{ mA}$
- $V_E = V_a - (R_5 + R_6) I_6 \Rightarrow V_E: V_E - (R_5 + R_6) I_6 = 3.7 \text{ V}$
- $I_u = \frac{V_C}{R_u} = 2.5 \text{ mA}$
- $I_C = I_u - I_6 = 2 \text{ mA}$ (in realtà è la corrente da E a C, positiva).
(La corrente da C ad E è negativa)
- $V_B = V_{CC} \cdot \frac{R_1}{R_1 + R_2} = 8 \text{ V}$

$$\cdot U_{ce} \cdot U_B - U_E \Rightarrow U_E = U_B - U_{BE} = 8.7 \text{ V}$$

(2)

$$\cdot U_{CE} = U_C - U_E = -5 \text{ V}$$

$$\cdot I_C = I_E \quad \text{poiché} \quad I_B = 0$$

$$\cdot R_3 = \frac{V_{cc} - U_E}{I_E} = 1650 \Omega$$

PUNTI DI RIPOSO


Q₁:

$$I_C = -2 \text{ mA} \quad U_{CE} = -5 \text{ V} \quad h_{fe} = 260 \quad h_{ie} = 2.7 \text{ k}\Omega$$

Q₂:

$$I_D = 6.5 \text{ mA} \quad U_{DS} = 6 \text{ V} \quad g_m = 2k |U_{ds} U_r| = 2 \frac{\text{mA}}{\text{V}}$$

21/07/2016

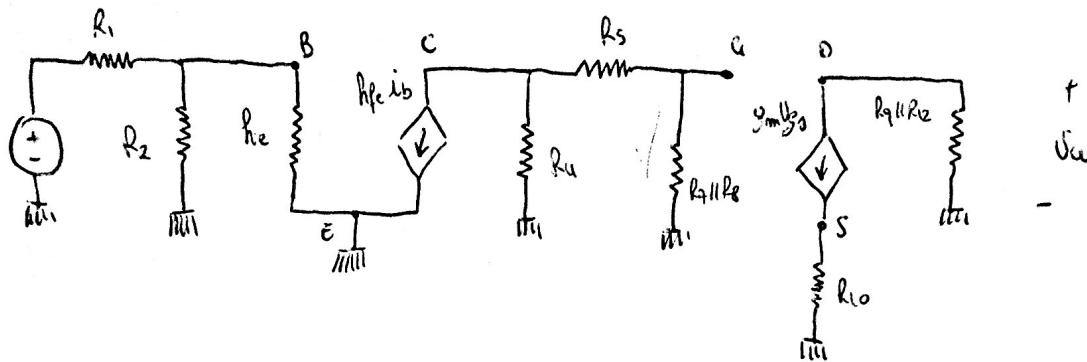



$$\frac{V_{in}}{V_{out}} = -g_m U_{gs} (R_7 \parallel R_8)$$

$$U_{gs} = U_g - U_s = U_g - g_m U_{gs} R_{lo} \rightarrow U_{gs} = \frac{U_g}{1 + g_m R_{lo}}$$

$$U_g = -h_{fe} i_{eb} \frac{R_u}{R_u + R_S + R_7 \parallel R_8} \cdot R_7 \parallel R_8$$

$$i_{eb} = \frac{V_{re}}{h_{fe}}$$
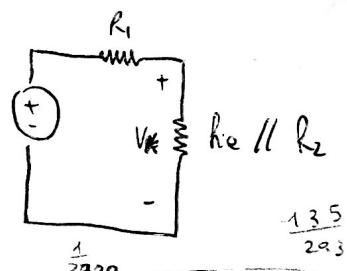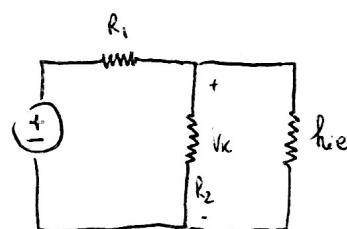
$$U_{re} = U_i \cdot \frac{h_{ie} \parallel R_2}{R_1 + h_{ie} \parallel R_2}$$



$$\frac{V_{in}}{U_i} = \overbrace{g_m (R_7 \parallel R_8)}^{\frac{4}{41}} \cdot \overbrace{\frac{1}{1 + g_m R_{lo}}}^{\frac{5}{6}} \cdot \overbrace{h_{fe} \cdot \frac{R_u \cdot R_7 \parallel R_8}{R_u + R_S + R_7 \parallel R_8}}^{285762, 5763} \cdot \overbrace{\frac{1}{h_{ie}}}^{\frac{1}{2400}} \cdot \overbrace{\frac{h_{ie} \parallel R_2}{R_1 + h_{ie} \parallel R_2}}^{\frac{135}{203}} = \boxed{3.964}$$

21/07/2014

ESERCIZIO 3)



$$Y = \overline{AC} (\bar{B}C + \bar{C}\bar{D}) + \bar{B}(\bar{A} + C) + \bar{D}E$$

$$Y = (\bar{A} + \bar{C})(\bar{B}C + \bar{C}\bar{D}) + \bar{A}\bar{B} + \bar{B}C + \bar{D}E$$

$$Y = \bar{A}\bar{B}C + \bar{A}\bar{C}\bar{D} + \bar{C}\bar{D} + \bar{A}\bar{B} + \bar{B}C + \bar{D}E$$

$$Y = \bar{C}\bar{D} + \bar{A}\bar{B} + \bar{B}C + \bar{D}E$$
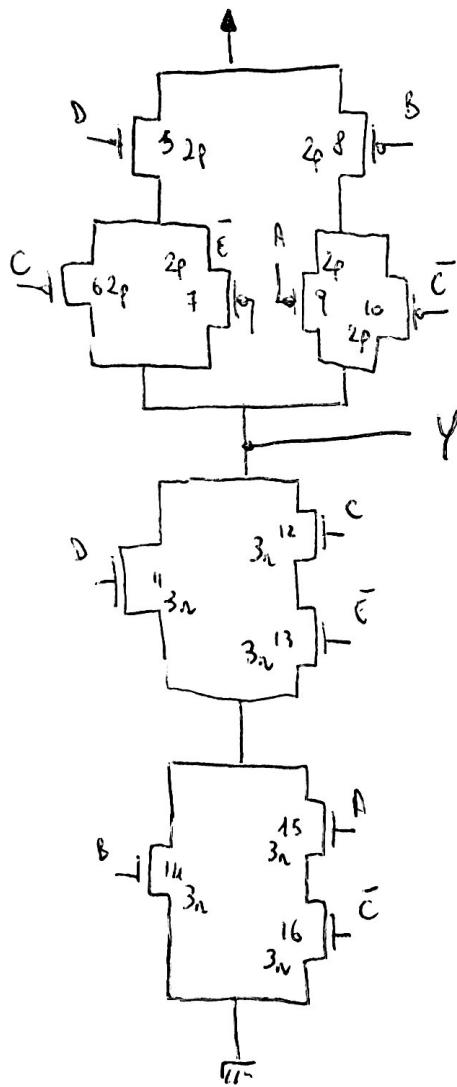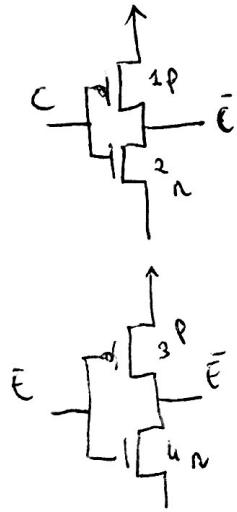
$$Y = \bar{D}(\bar{C} + E) + \bar{B}(\bar{A} + C)$$



• INVERTER ON BASE

$$\left(\frac{W}{L}\right)_L = \left(\frac{W}{L}\right)_S = P = 5$$

$$\left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_U = n = 2$$

(2)

• PUN

- WORST CASE: $Q_5, Q_6 \circ Q_5, Q_7 \circ Q_8, Q_9 \circ Q_8, Q_{10}$

$$\binom{W}{L}_S = \binom{W}{L}_C = X$$

$$\frac{1}{x} + \frac{1}{x} = \frac{1}{p} \rightarrow \frac{2}{x} = \frac{1}{p} \rightarrow x = 2p = 10$$

$$\binom{W}{L}_{S, 6, 7, 8, 9, 10} = 2p = 10$$

• PDN

- WORST CASE: $Q_{12}, Q_{13}, Q_{15}, Q_{16}$ ma non è possibile perché presenti C e \bar{C} .

- WORST CASE 2): $Q_{11}, Q_{15}, Q_{16} \circ Q_{12}, Q_{13}, Q_{14}$

$$\binom{W}{L}_{11, 12, 13, 14} = X$$

$$\frac{1}{x} + \frac{1}{x} + \frac{1}{x} = \frac{1}{n} \rightarrow \frac{3}{x} = \frac{1}{n} \rightarrow x = 3n = 6$$


$$\binom{W}{L}_{11, 12, 13, 14, 15, 16} = 3n = 6$$

21/7/2014

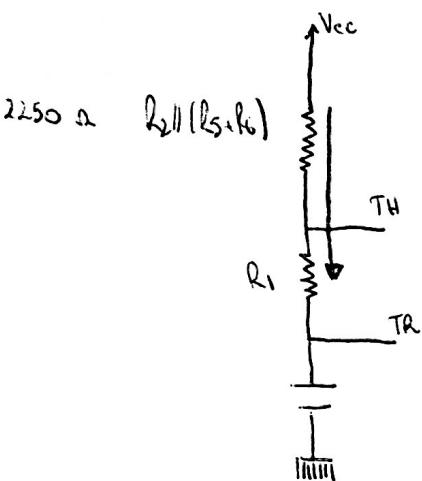EXERCIZIO C

$$Q_1 = 1 \rightarrow D = H2$$

$$V_{G1} = V_{CC} \cdot \frac{R_3}{R_3 + R_4} = 1V \quad V_{S1} = V_{CC} = 5V \quad V_{GS1} = -6V < V_T = -1V \quad Q_1 = ON$$



- $V_i = \frac{1}{3} V_{CC} = \frac{5}{3} V$
- $S_f = V_{CC}$
- V_{comm} $\Rightarrow V_{TH} = \frac{2}{3} V_{CC} = \frac{10}{3} V$

$$I = \frac{V_{CC} - V_{TH}}{R_2 \parallel (R_5 + R_6)} = \frac{1}{1350} A$$

$$\bullet V_{comm} = V_{TH} - R_1 I = \frac{70}{27} V$$

VERIFICO CHE $V_i < V_{comm} < S_f \rightarrow OK$

$$T_1 = \gamma_1 \ln \left(\frac{V_i - S_f}{V_{comm} - S_f} \right)$$


$$T_1 = f_{V1} \cdot C = \left[R_1 + R_2 \parallel (R_5 + R_6) \right] \cdot C = 3250 \cdot C = \frac{629}{600000} s$$

$$T_1 = 3.690155265 \cdot 10^{-4} s$$

$$Q = 0 \rightarrow D = 0$$

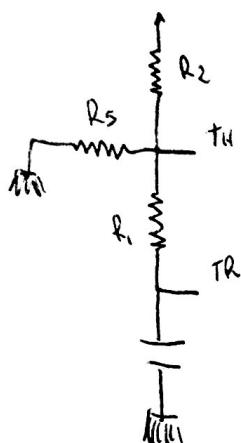(2)

$$U_{\text{in}} = 0 \quad U_{\text{S1}} = V_{\text{cc}} = 5 \text{ V} \quad U_{\text{S2}} = -V_{\text{cc}} = -5 < V_T = -1 \text{ V} \quad Q_1 = \text{ON}$$



$$\cdot U_i = \frac{10}{27} \text{ V}$$

$$\cdot U_{\text{source}} = \frac{5}{3} \text{ V}$$

$$\cdot U_f = V_{\text{cc}} \cdot \frac{R_s}{R_2 + R_5} = \frac{1}{2} \text{ V}$$

VERIFIKATION CKE $U_i > U_{\text{source}} > U_f \rightarrow \text{OK}$

$$T_2 = T_2 \ln \left(\frac{U_i - U_f}{U_{\text{source}} - U_f} \right)$$

$$T_2 = R_{\text{V2}} \cdot C = [R_1 + R_2/R_5] \cdot C = 1900 \cdot C = 6.27 \cdot 10^{-4} \text{ s}$$

$$T_2 = 3.663266889 \cdot 10^{-4}$$

- - -


$$T = T_1 + T_2 = 7.153622136 \cdot 10^{-4} \text{ s}$$

$$f \cdot \frac{1}{T} = 1397.93 \text{ Hz}$$

30/06/2014

1

(EXPERIMENTO A)

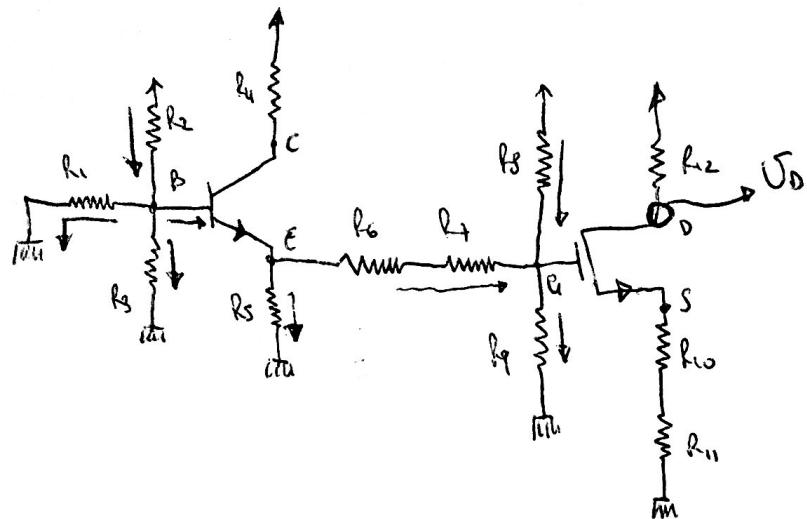

- $I_D = \frac{V_{cc} - V_D}{R_{12}} = 2 \text{ mA}$
- $I_E = 0 \rightarrow I_S = I_D = 2 \text{ mA}$
- $V_S = (R_{10} + R_{11}) \cdot I_S = 6 \text{ V}$
- $V_{ES} = V_T + \sqrt{\frac{I_D}{n}} = 3 \text{ V}$
- VERIFICO SATURAZIONE $V_{DS} > V_{ES} - V_T \rightarrow h > 2 \text{ OK}$
- $V_{GS} = V_E - V_S \Rightarrow V_E = V_{GS} + V_S = 9 \text{ V}$
- $I_B = \frac{V_{cc} - V_E}{R_8} = 0,5 \text{ mA}$
- $I_Q = \frac{V_E}{R_9} = 1,5 \text{ mA}$
- $I_T = I_Q - I_B = 1 \text{ mA}$
- $V_E - V_{ce} = (R_6 + R_7) I_T \Rightarrow V_E = V_{ce} + (R_6 + R_7) I_T = 10 \text{ V}$
- $I_S = \frac{V_E}{R_5} = 1 \text{ mA}$
- $I_E = 2 \text{ mA}$
- SUPONIAMO ZAD $\Rightarrow I_C \gg I_B \Rightarrow I_C \approx I_E \Rightarrow I_C = 2 \text{ mA}$
- $V_{cc} - V_c = R_4 I_C \rightarrow V_c = V_{cc} - R_4 I_C = 15 \text{ V}$

VERIFICO ZAD: $V_{CE} > V_{CE_{SAT}}$ $\rightarrow 5 \text{ V} > 0.2 \text{ V}$ $\rightarrow \text{OK}$

• $I_E = \frac{I_C}{h_{FE}} = 6.8965 \mu\text{A}$

• $V_B = U_{BE} + V_E = 10.7 \text{ V}$

• $I_3 = \frac{V_B}{R_3} = 21.4 \cdot \mu\text{A}$

• $I_1 = \frac{V_B}{R_1} = 1.07 \text{ mA}$

• $I_2 = I_1 + I_3 + I_B = 1.0982965 \cdot \cancel{mA}$

• $R_2 = \frac{V_{CC} - V_B}{I_2} = 6646.65 \Omega$

- - - - -
PUNTI DI RIPOSO

• $Q_1:$


$$h_{FE} = 290 \quad h_{FE} = 300 \quad h_{ie} = 6.3 \text{ k}\Omega \quad I_E = 2 \text{ mA} \quad V_{CE} = 5 \text{ V}$$

• $Q_2:$

$$I_D = 2 \text{ mA} \quad V_{DS} = 1 \text{ V} \quad g_m = 2k |V_{GS} - V_T| = 2 \text{ mA} \frac{1}{V}$$

30/06/2016

(3)

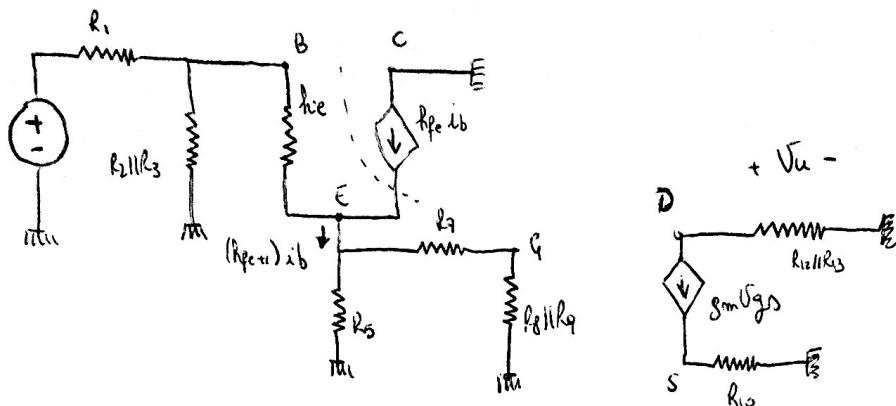


$$\cdot V_u = -g_m V_{gs} (R_2 || R_3)$$


$$\cdot V_{gs} = V_g - V_d = V_g - g_m V_{gs} R_{lo} \rightarrow V_{gs} = \frac{V_g}{1 + g_m R_{lo}}$$

$$\cdot V_g = (h_{fe} + 1) i_b \cdot \frac{R_5}{R_5 + R_7 + R_8 || R_9} \cdot R_8 || R_9$$

$$\cdot i_b = \frac{V_K}{h_{ie} + (h_{fe} + 1) [R_2 || (R_7 + R_8 || R_9)]}$$

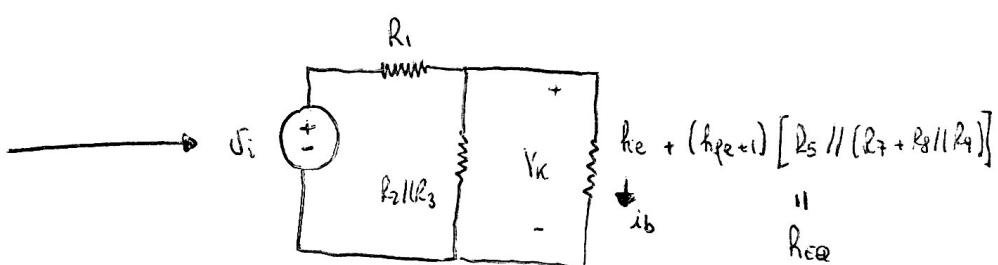

$$\cdot V_K = V_i \frac{R_2 || R_3 // \{ h_{ie} + (h_{fe} + 1) [R_5 // (R_7 + R_8 || R_9)] \}}{R_1 + R_2 || R_3 // \{ h_{ie} + (h_{fe} + 1) [R_5 // (R_7 + R_8 || R_9)] \}}$$

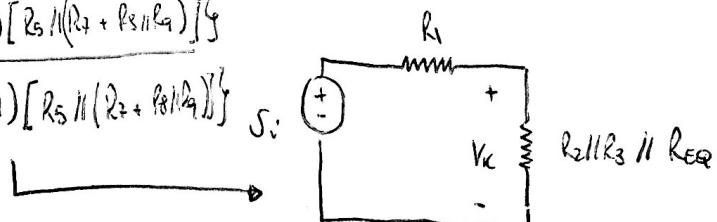

$$\cdot \frac{V_u}{V_i} = -\frac{g_m (R_2 || R_3)}{1 + g_m R_{lo}} \cdot \frac{(h_{fe} + 1) \cdot R_5 \cdot R_8 || R_9}{R_5 + R_7 \cdot R_8 || R_9} \cdot \frac{1}{h_{ie} + (h_{fe} + 1) [R_5 // (R_7 + R_8 || R_9)]}$$

$$\frac{R_2 || R_3 // \{ h_{ie} + (h_{fe} + 1) [R_5 // (R_7 + R_8 || R_9)] \}}{R_1 + R_2 || R_3 // \{ h_{ie} + (h_{fe} + 1) [R_5 // (R_7 + R_8 || R_9)] \}}$$

$$\boxed{\frac{V_u}{V_i} = -2,01636}$$

30/06/2014

(1)

(SEPARAR B)





$$Y = (\bar{B} + \bar{C})(\bar{A}\bar{B} + D + \bar{B}\bar{E}) + \bar{C}\bar{E}(\bar{A} + BD + \bar{E}) + A\bar{B}$$

$$Y = (\bar{B} \cdot C)(\bar{A}\bar{B} + D + \bar{B}\bar{E}) + (C + \bar{E})(\bar{A} + BD + \bar{E}) + A\bar{B}$$

$$Y = A\bar{B}C + \bar{B}CD + \bar{B}C\bar{E} + \bar{A}C + BCD + C\bar{E} + \bar{A}\bar{E} + BDE + \bar{E} + A\bar{B}$$

$$Y = A\bar{B} + \bar{E} + CD + \bar{A}C + \bar{B}CE$$
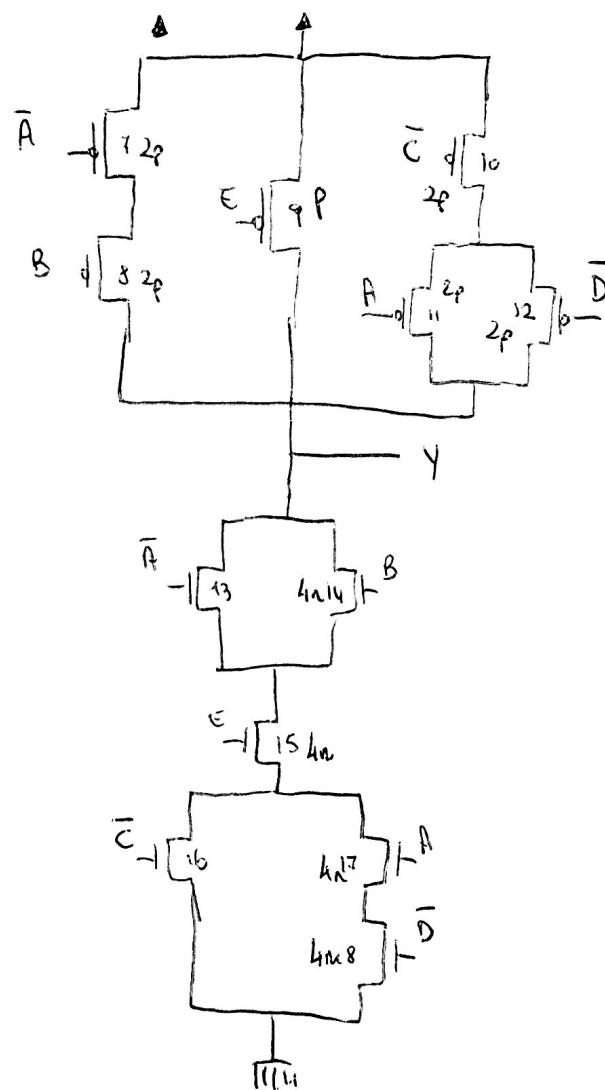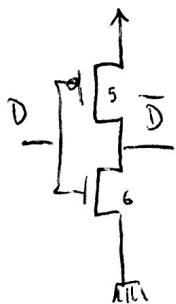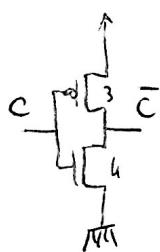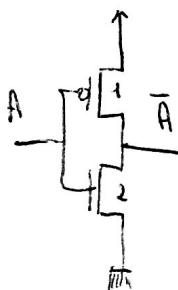
$$Y = A\bar{B} + \bar{E} + CD + \bar{A}C = A\bar{B} + \bar{E} + C(\bar{A} + D)$$



• INVERTER ON BASE

$$\left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_5 = P = 5$$

$$\left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_6 = n = 2$$

• FUN

- WORST CASE : $Q_7, Q_8 \rightarrow Q_{10}, Q_{11} \rightarrow Q_{10}, Q_{12}$

$$\binom{W}{L}_{7,8,10,11,12} = x$$

$$\frac{1}{x} + \frac{1}{x} = \frac{1}{p} \rightarrow \frac{2}{x} = \frac{1}{p} \rightarrow x = 2p = 10$$

- WORST CASE : Q_9

$$\binom{W}{L}_9 = x$$

$$\frac{1}{y} = \frac{1}{p} \rightarrow y = p = 5$$

• PDN

- WORST CASE : $Q_{13}, Q_{15}, Q_{17}, Q_{18}$ non possibile perché $A \in \bar{A}$.
 $Q_{14}, Q_{15}, Q_{17}, Q_{18}$

$$\binom{W}{L}_{14,15,17,18} = x$$

$$\frac{1}{x} + \frac{1}{x} + \frac{1}{x} + \frac{1}{x} = \frac{1}{n} \rightarrow x = 4n = 8$$

- WORST CASE (2)

Due scelte:

1) Q_{14}, Q_{15}, Q_{16} e scelto la 16

$$\frac{1}{ln} + \frac{1}{ln} + \frac{1}{8} = \frac{1}{n} \rightarrow \frac{1}{y} = \frac{1}{n} - \frac{1}{2n} \rightarrow \frac{1}{y} = \frac{1}{2n} \rightarrow y = 2n$$

Poi scelto

Q_{13}, Q_{15}, Q_{16}

$$\binom{W}{L}_{13} = 2$$

$$\frac{1}{2} + \frac{1}{2n} + \frac{1}{ln} = \frac{1}{n} \rightarrow \frac{1}{2} = \frac{-1+2+4}{4n} \rightarrow \frac{1}{2} = \frac{1}{ln} \rightarrow 2 = ln$$

2) Q_{13}, Q_{15}, Q_{16}

$$\binom{W}{L}_{13} = \binom{W}{L}_{16} = k$$

$$\frac{1}{k} + \frac{1}{k} + \frac{1}{ln} = \frac{1}{n} \Rightarrow \frac{2}{k} = \frac{4-1}{4n} \Rightarrow \frac{2}{k} = \frac{3}{4n} \rightarrow 3k = 8n \quad k = \frac{8}{3} n$$

SCELGO A SECONDA DEL'ALGO

$$1) ln + ln + ln + ln + 2n + ln = 64$$

$$2) ln + ln + ln + ln + \frac{8}{3}n + \frac{8}{3}n = 62,67 \rightarrow \text{SCELGO QUESTO CASO}$$


30/06/2016

(1)

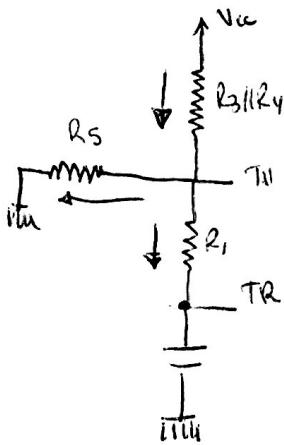ESEMPIO C)

$$Q=1 \rightarrow D=1 \text{ Hz}$$

$$V_{C_{in}} = 0 \text{ V} \quad V_{S_1} = 0 \text{ V} \quad V_{C_{S_1}} = 0 \text{ V} < V_{T_1} = 1 \text{ V} \Rightarrow Q_1 = \text{OFF}$$



$$\bullet V_i = \frac{1}{3} V_{CC} = \frac{5}{3} \text{ V}$$

$$\bullet V_f = V_{CC} \cdot \frac{R_S}{R_S + R_3//R_4} = 4 \text{ V}$$

$$\bullet V_{\text{comm}} \text{ se } V_{T_{H+}} = \frac{2}{3} V_a = \frac{10}{3} \text{ V}$$

$$I_3 = \frac{V_{CC} - V_{T_{H+}}}{R_3//R_4} = \frac{1}{600} \text{ A}$$

$$I_5 = \frac{V_{T_{H+}}}{R_S} = \frac{1}{1200} \text{ A} \Rightarrow I_1 = I_3 \cdot I_5 = \frac{1}{1200} \text{ A}$$

$$\bullet V_{\text{comm}} = V_{T_H} - R_1 I_1 = \frac{35}{12} \text{ V}$$

VERIFICO CHE $V_i < V_{\text{comm}} < V_f \rightarrow \text{OK}$


$$T_1 = T_H \ln \left(\frac{V_i - V_f}{V_{\text{comm}} - V_f} \right)$$

$$T_1 = R_{V_1} \cdot C = \left[h_T + R_3//R_4//R_S \right] \cdot C = 1300 \cdot C = \frac{13}{10000} \text{ s}$$

$$T_1 = 9.974316985 \cdot 10^{-6} \text{ s}$$

$$Q = 0 \rightarrow D = 0$$
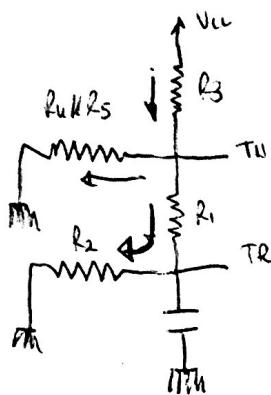
$$V_{A_1} = V_{cc} \quad V_{S_1} = 0 \quad V_{C_{S_1}} = V_{cc} = 5V \Rightarrow V_T = 1V \quad Q_1 = 5V$$



$$\bullet V_i = \frac{35}{12} V$$

$$\bullet V_{C_{S_1}} = \frac{5}{3} V$$

$V_f \rightarrow$ calculate V_{in} e poi V_{ir}

$$V_{TH} = V_{cc} \cdot \frac{(R_1 + R_2) \parallel (R_L \parallel R_3)}{R_3 + [(R_1 + R_2) \parallel (R_L \parallel R_3)]} = \frac{10}{9} V$$

$$\bullet V_f = V_{ir} = V_{TH} \cdot \frac{R_2}{R_1 + R_2} = \frac{5}{9} V$$

VERIFICO CHE $V_i > V_{C_{S_1}} > V_f \rightarrow OK$

$$T_2 = T_2 \ln \left(\frac{V_i - V_f}{V_{C_{S_1}} - V_f} \right)$$

$$T_2 = fV_2 \cdot C = \left[R_2 \parallel [R_1 + (R_3 \parallel R_L \parallel R_S)] \right] \cdot C = \frac{3250}{9} \cdot C = \frac{13}{36000} \text{ s}$$

$$T_2 = 2.721953731 \cdot 10^{-4} \text{ s}$$


$$T_4 = T_1 + T_2 = 1.269627072 \cdot 10^{-3} \text{ s}$$

$$f = \frac{1}{T} = 787,6328 \text{ Hz}$$

9/06/2014

(1)

ESEPC (ZW A)

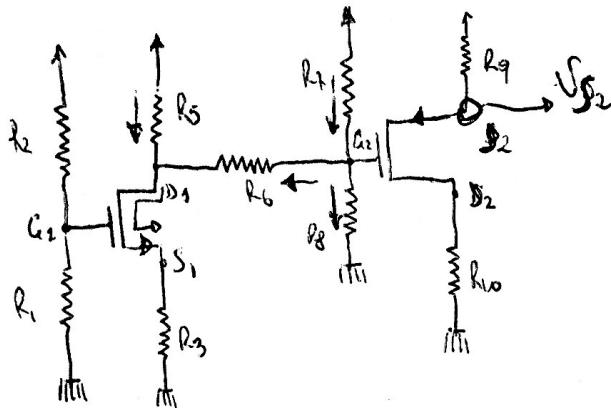

$$\bullet I_{ds2} = \frac{V_{cc} - V_{ds2}}{R_9} = 2 \text{ mA}$$

$$\bullet I_{G2} = 0 \rightarrow I_{D2} = I_{ds2} = 2 \text{ mA}$$

$$\bullet V_{ds2} = R_{10} I_{ds2} = 10 \text{ V}$$

$$\bullet V_{ds2} = V_T - \sqrt{\frac{I_D}{K}} = -3 \text{ V}$$

VERIFICO LA SATURAZIONE

$$I_{DS} < V_{ds} - V_T \rightarrow -5 \text{ V} < -2 \text{ V} \quad \text{OK}$$

$$V_{ds} = V_{ds} - U_s \Rightarrow V_d = V_{ds} + U_s = 12 \text{ V}$$

$$\bullet I_8 = \frac{V_{ds}}{R_8} = \cancel{1.2 \text{ mA}} \quad 0.3 \text{ mA}$$

$$\bullet I_7 = \frac{V_{cc} - V_{ds}}{R_7} = 0.6 \text{ mA}$$

$$\bullet I_6 = I_7 - I_8 = 0.3 \text{ mA}$$

$$\bullet V_{ds} - U_{D1} = R_6 I_6 \rightarrow U_{D1} = V_{ds} - R_6 I_6 = 11.7 \text{ V}$$

$$\bullet I_5 = \frac{V_{cc} - V_{ds1}}{R_5} = 2.1 \text{ mA}$$

$$\bullet I_{D1} = I_6 + I_5 = 2.4 \text{ mA}$$

$$\bullet I_{G1} = 0 \rightarrow I_{S1} = I_{D1} = 2.4 \text{ mA}$$

$$\bullet V_d = V_{cc} \cdot \frac{R_1}{R_1 + R_2} = 9 \text{ V}$$

$$\bullet V_{DS} = V_T + \sqrt{\frac{I_D}{k}} = 3,19089 \text{ V}$$

$$\bullet V_{GS} = V_{GS} - V_S \Rightarrow V_G = V_{GS} - V_{DS} = 5.80911 \text{ V}$$

VERIFICO CHE $V_{DS} > V_{GS} - V_T \rightarrow 5.89089 \text{ V} > 2,19089 \text{ V} \rightarrow \text{OK}$

$$\bullet R_3 = \frac{V_S}{I_S} = 2620,6625 \Omega$$

PUNTI DI RIPOSI

$Q_1:$

$$I_{D1} = 2,4 \text{ mA}$$

$$V_{DS1} = 5.89089 \text{ V}$$

$$g_{m1} = 2k|V_{GS} - V_T| = 2.19089 \cdot m\frac{A}{V}$$

$Q_2:$


$$I_{D2} = 2 \text{ mA}$$

$$V_{DS2} = -5 \text{ V}$$

$$g_{m2} = 2k|V_{GS} - V_T| = 2 \text{ mA/V}$$

9/06/2014

3

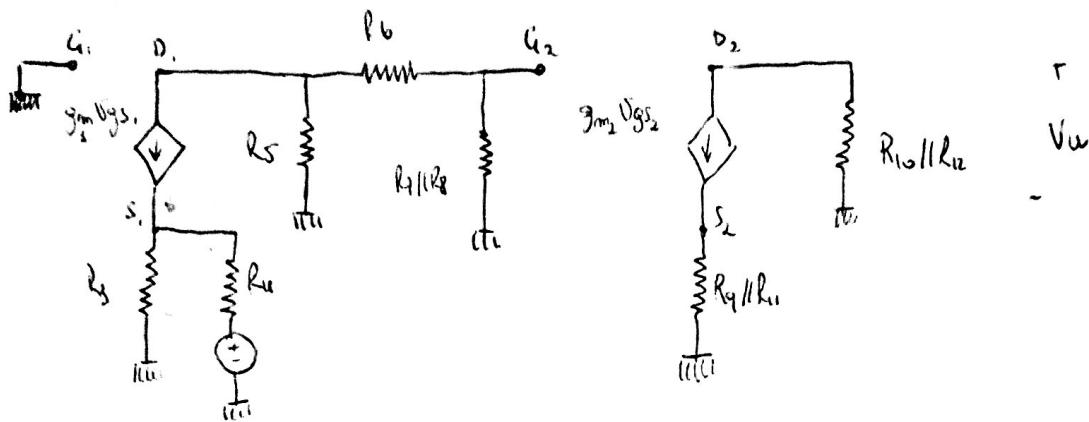

$$\bullet V_u = -g_{m_2} V_{gs_2} \cdot R_{10} \| R_{12}$$

$$\bullet V_{gs_2} = V_{g_2} - U_{n_2} = V_{g_2} - g_m V_{gs_2} \cdot R_9 \| R_u \rightarrow V_{gs_2} = \frac{V_{g_2}}{1 + g_{m_2} (R_9 \| R_u)}$$

$$\bullet V_{g_2} = -g_{m_1} V_{gs_1} \cdot \frac{R_5}{R_5 + R_6 + R_7 \| R_8} \cdot R_7 \| R_8$$

$$\bullet V_{gs_1} = -V_{s_1}$$

$$\left\{ \begin{array}{l} V_{s_1} = I_3 R_3 \\ V_{s_1} - V_i = R_u I_u \\ g_{m_1} V_{gs_1} = I_3 + I_u \\ -g_{m_1} V_{gs_1} = \frac{V_{s_1}}{R_3} + I_u \rightarrow -g_{m_1} V_{s_1} = \frac{V_{s_1}}{R_3} + \frac{V_{s_1}}{R_u} - \frac{V_i}{R_4} \rightarrow V_{s_1} \left(g_{m_1} + \frac{1}{R_3} + \frac{1}{R_u} \right) = \frac{V_i}{R_4} \end{array} \right.$$

$$\bullet V_{s_1} = \frac{V_i}{R_u} \cdot \left(g_{m_1} + \frac{1}{R_3} + \frac{1}{R_u} \right)^{-1}$$

$$\bullet \frac{V_u}{V_i} = - \frac{\frac{g_{m_1} R_{10} \| R_{12}}{1 + g_{m_2} (R_9 \| R_u)}}{\frac{g_{m_1} R_5 \cdot R_7 \| R_8}{R_5 + R_6 + R_7 \| R_8}} \cdot \frac{\left(g_{m_1} + \frac{1}{R_3} + \frac{1}{R_u} \right)^{-1}}{R_4} = \boxed{-23,62}$$

125
19

09/06/2014

(1)

$$Y = \overline{AB}(\bar{C} + \bar{D}) + \overline{DE}(B + A\bar{C})$$




$$Y = (A + \bar{B})(\bar{C} + \bar{D}) + (\bar{D} + \bar{E})(B + A\bar{C})$$

$$Y = A\bar{C} + A\bar{D} + \bar{B}\bar{C} + \bar{B}\bar{D} + B\bar{D} + A\bar{C}\bar{D} + B\bar{E} + A\bar{C}\bar{E}$$

$$Y = A\bar{C} + \bar{D} + A\bar{D} + \bar{B}\bar{C} + B\bar{E} + A\bar{C}\bar{E}$$

$$Y = \bar{D} + A\bar{C} + \bar{B}\bar{C} + B\bar{E} = \bar{D} + B\bar{E} + \bar{C}(A + \bar{B})$$

16 mosfet

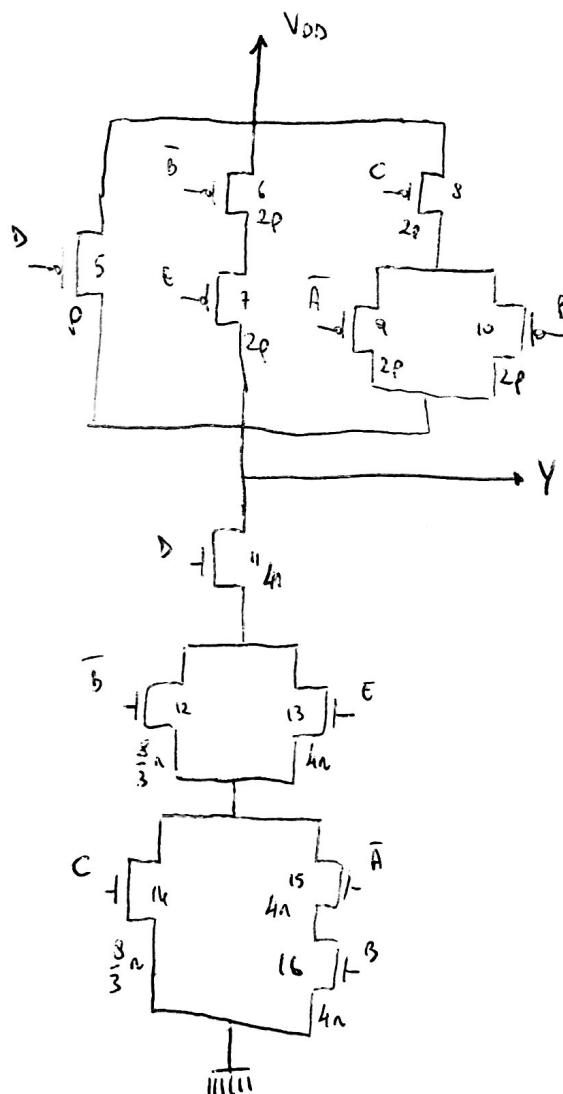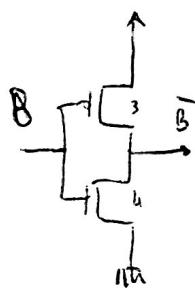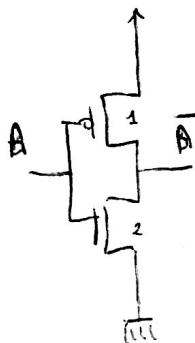

• INVERTER IN BASE

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_3 = P = 5$$

$$\left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_4 = n : 2$$

• PUN

- WORST CASE: $Q_6, Q_7 \rightarrow Q_8, Q_9 \rightarrow Q_9, Q_{10}$

$$\binom{W}{L}_{6,7,8,9,10} = x$$

$$\frac{1}{x} + \frac{1}{x} = \frac{1}{p} \rightarrow \frac{2}{x} = \frac{1}{p} \rightarrow x = 2p = 10$$

- WORST CASE 2: Q_5

$$\binom{W}{L}_5 = p = 5$$

• PCN

- WORST CASE: $\begin{cases} Q_{11}, Q_{12}, Q_{13}, Q_{16} \rightarrow \text{NON POSSIBILE PERMUTAZIONE} \\ Q_{11}, Q_{13}, Q_{15}, Q_{16} \rightarrow \text{NON POSSIBILE} \end{cases}$

$$\binom{W}{L}_{11,13,15,16} = y$$

$$\frac{1}{y} + \frac{1}{y} + \frac{1}{y} + \frac{1}{y} = \frac{4}{n} \rightarrow \frac{4}{y} = \frac{1}{n} \rightarrow y = 4n = 8$$

- WORST CASE 2:

Passo seguente 2 percorsi:

① Q_{11}, Q_{12}, Q_{14}

$$\binom{W}{L}_{11,14} = y$$

$$\frac{1}{y} + \frac{1}{y} + \frac{1}{4n} = \frac{1}{n} \rightarrow \frac{2}{y} = \frac{3}{4n} \Rightarrow 3y = 8n \Rightarrow y = \frac{8}{3}n = \frac{16}{3}$$

② Primo calcolo $\binom{W}{L}_{11} = p$ e poi $\binom{W}{L}_{12}$

- Q_{11}, Q_{13}, Q_{14}

$$\binom{W}{L}_{11} = z$$

$$\frac{1}{z} + \frac{1}{2n} + \frac{1}{4n} = \frac{1}{n} \rightarrow \frac{1}{z} = \frac{1}{n} - \frac{1}{2n} \rightarrow \frac{1}{z} = \frac{1}{2n} \rightarrow z = 2n = 4$$

- Q_{11}, Q_{12}, Q_{14}

$$\binom{W}{L}_{11} = k$$

$$\frac{1}{k} + \frac{1}{2n} + \frac{1}{4n} = \frac{1}{n} \rightarrow \frac{1}{k} = \frac{4-1-2}{4n} \Rightarrow k = 4n = 8$$

\rightarrow SCELGO QUESTA

CALCULO LF AREA

①

$$\frac{16}{3} + \frac{16}{3} = \frac{32}{3} = 10,667$$

②

$$4 + 8 = 12$$

09/06/2016

①

EJERCICIO c)

$$Q_1 = 1 \rightarrow D = 'Hf$$


$$U_{G_1} = 0V \quad U_{S_1} = 0V$$

$$U_{G_1} = 0V \leftarrow V_i = 1V$$

 $Q_1 = OFF$

$$U_{G_2} = V_{cc} \quad U_{S_2} = V_{cc}$$

$$U_{G_2} = 5V \Rightarrow V_i = -1V$$

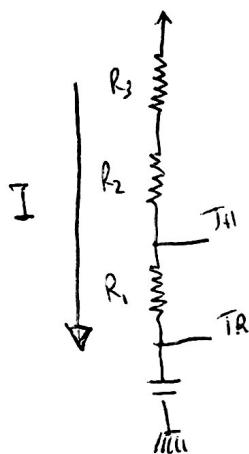 $Q_2 = OFF$ 

$$\bullet V_i = \frac{1}{3} V_{cc} = \frac{5}{3} V$$

$$\bullet V_f = V_{cc}$$

$$\bullet V_{common}$$

$$\text{so } V_{TH} = \frac{2}{3} V_{cc} = \frac{10}{3} V$$

$$I = \frac{V_{cc} - V_{TH}}{R_2 + R_3} = \frac{1}{660} A$$

$$\bullet V_{common} = V_{TH} - R_1 I = \frac{85}{33} V$$

VERIFICO CHE $V_i \leq V_{common} \leq V_f \rightarrow OK$


$$T_1 = \tau_1 \ln \left(\frac{V_i - V_f}{V_{common} - V_f} \right)$$

$$T_1 = R_{V_1} \cdot C = [R_1 + R_2 + R_3] \cdot C = 1600 \cdot C = \frac{1}{6250} s$$

$$T_1 = 5.095259698 \cdot 10^{-5} s$$

$$Q_1 = 0 \rightarrow D = 0$$
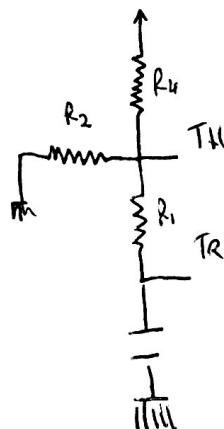
$$\begin{aligned} V_{e2} &= 0V & V_{S2} &= V_{ce} & V_{eS2} &= -V_{ce} = -5V < V_{t2} = -1 & \rightarrow Q_2 \text{ ON} \\ V_{G1} &= V_{cc} & V_{S1} &= 0V & V_{GS1} &= 5V > V_{t1} = 1V & \rightarrow Q_1 \text{ ON} \end{aligned}$$



$$\cdot V_i = \frac{8.5}{33} V$$

$$\cdot V_{com} = \frac{5}{3} V$$

$$\cdot V_f = V_{ce} \cdot \frac{R_f}{R_f + R_c} = \frac{1}{2} V$$

Verifico che: $V_i > V_{com} > V_f \rightarrow \text{OK}$

$$T_2 = T_2 \ln \left| \frac{V_i - V_f}{V_{com} - V_f} \right|$$


$$T_2 = R_{V2} \cdot C = [R_1 + R_2 / R_c] \cdot C = 590 \cdot C = \frac{54}{1000000} \text{ s}$$

$$T_2 = 3.399635473 \cdot 10^{-5} \text{ s}$$

$$\cdot T = T_1 + T_2 = 8.496695171 \cdot 10^{-5} \text{ s}$$

$$\boxed{\cdot f = \frac{1}{T} = 11712.05 \text{ Hz}}$$

CIRCUITO A)

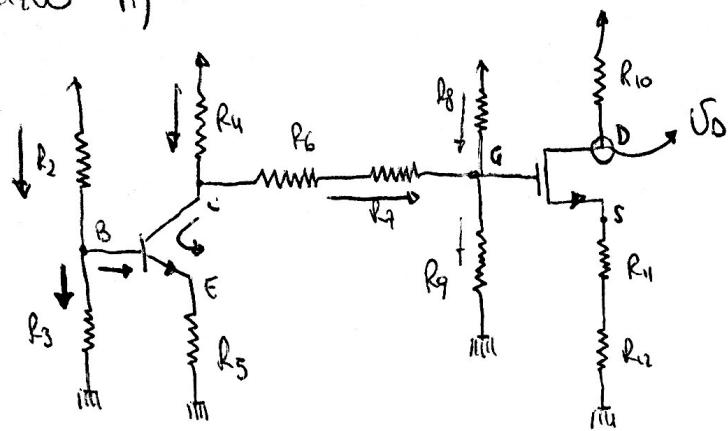

$$\bullet I_B = \frac{V_{cc} - V_D}{R_{10}} = 6 \text{ mA}$$

$$\bullet I_E = 0, \quad I_S = I_B = 6 \text{ mA}$$

$$\bullet U_S = (R_{11} + R_{12}) I_S = 6 \text{ V}$$

$$\bullet U_{ES} = V_T + \sqrt{\frac{I_B}{k}} = 2 \text{ V}$$

VERIFICO LA SATURAZIONE: $U_{DS} > U_{ES} - V_T \rightarrow 4 \text{ V} > 1 \text{ V} \quad \text{OK}$

$$\bullet U_{ES} = V_{cc} - U_S \rightarrow V_{cc} = U_{ES} + U_S = 6 \text{ V}$$

$$\bullet I_8 = \frac{V_{cc} - V_D}{R_8} = 1 \text{ mA}$$

$$\bullet I_9 = \frac{V_D}{R_9} = 3 \text{ mA}$$

$$\bullet I_7 = I_9 - I_8 = 2 \text{ mA}$$

$$\bullet U_C = V_{cc} + (R_6 + R_7) I_7 = 7 \text{ V}$$

$$\bullet I_4 = \frac{V_{cc} - V_C}{R_4} = 6 \text{ mA}$$

$$\bullet I_C = I_u - I_7 = 2 \text{ mA}$$

POTENZIALE Z.A.D $I_C \gg I_B \Rightarrow I_E \approx I_C = 2 \text{ mA}$

$$\bullet U_E = R_S I_E = 2 \text{ V}$$

VERIFICO ZAD $\rightarrow V_{ce} > V_{cesat} \Rightarrow 5 \text{ V} > 0,2 \text{ V} \rightarrow \text{OK}$

$$\bullet I_B = \frac{I_C}{h_{FE}} = 6,8965 \mu\text{A}$$

$$\cdot V_B = 2V_{BE} + V_E = 2.7 \text{ V}$$

$$\cdot I_3 = \frac{V_B}{R_3} = 10 \mu\text{A}$$

$$\cdot I_2 = I_3 + I_B = 16,8965 \mu\text{A}$$

$$\cdot R_2 = \frac{V_{CE} - V_B}{I_2}, 727961,41 \Omega \approx 727959,18 \Omega$$


PUNTI DI FILO

Q₁:

$$h_{FE} = 300 \quad h_{F'E} = 290 \quad h_{ie} = 6.8 \text{ k}\Omega \quad I_C = 2 \text{ mA} \quad V_{CE} = 5 \text{ V}$$

Q₂:

$$I_D = 4 \text{ mA} \quad V_{DS} = 6 \text{ V} \quad g_m = 2K |V_{GS} - V_r| = 8 \text{ mA/V}$$

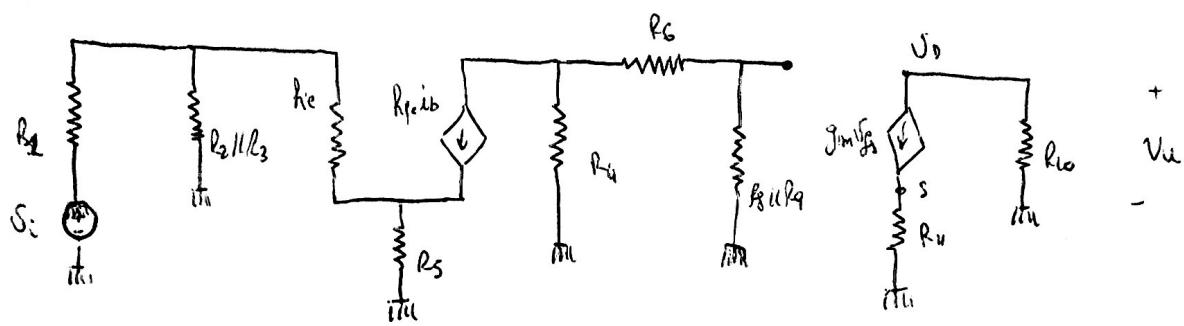


$$\cdot V_o = -g_m V_{gs} \cdot R_L$$


$$\cdot V_{gs} = V_g - V_s = V_g - g_m V_g R_{11} \rightarrow V_{gs} = \frac{V_g}{1 + g_m R_{11}}$$

$$\cdot V_g = -h_{fe} i_b \frac{R_4}{R_u + R_6 + R_8 \parallel R_9} \cdot R_8 \parallel R_9$$
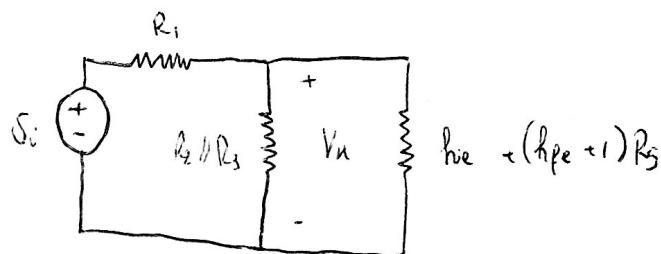
$$\cdot i_b = \frac{V_K}{h_{ie} + (h_{fe} + 1) R_S}$$


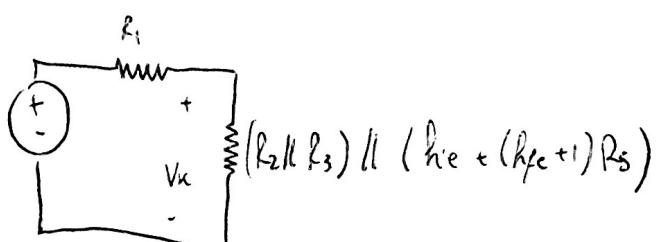
$$\cdot V_o = V_{ie} \cdot \frac{(R_2 \parallel R_3) \parallel (h_{ie} + (h_{fe} + 1))}{R_1 + [(R_2 \parallel R_3) \parallel (h_{ie} + (h_{fe} + 1) R_S)]}$$



$$\cdot \frac{V_o}{V_i} = \frac{g_m R_L}{1 + g_m R_{11}} \cdot \frac{h_{fe} \cdot R_u \cdot R_8 \parallel R_9}{R_u + R_6 + R_8 \parallel R_9} \cdot \frac{1}{h_{ie} + (h_{fe} + 1) R_S} \cdot \frac{(R_2 \parallel R_3) \parallel (h_{ie} + (h_{fe} + 1) R_S)}{R_1 + [(R_2 \parallel R_3) \parallel (h_{ie} + (h_{fe} + 1) R_S)]} = 6,77$$

17/02/2014

(1)

ESPECIALLY 3)

$$Y = (\overline{A + \bar{D}})(\bar{B}D + \bar{C} + \bar{E}) + (\overline{B + \bar{D}})(AD + \bar{C}) + A\bar{C}D + \bar{A}\bar{E}$$



$$Y = (\bar{A} \cdot D)(\bar{B}D + \bar{C} + \bar{E}) + (\bar{B} \cdot D)(AD + \bar{C}) + A\bar{C}D + \bar{A}\bar{E}$$

$$Y = \bar{A}\bar{B}D + \bar{A}\bar{C}D + \bar{A}D\bar{E} + A\bar{B}D + \bar{B}\bar{C}D + A\bar{C}D + \bar{A}\bar{E}$$

$$Y = \bar{B}D + \bar{C}D + \bar{A}\bar{E} + \bar{B}\bar{C}D$$

$$Y = \bar{B}D + \bar{C}D + \bar{A}\bar{E}$$
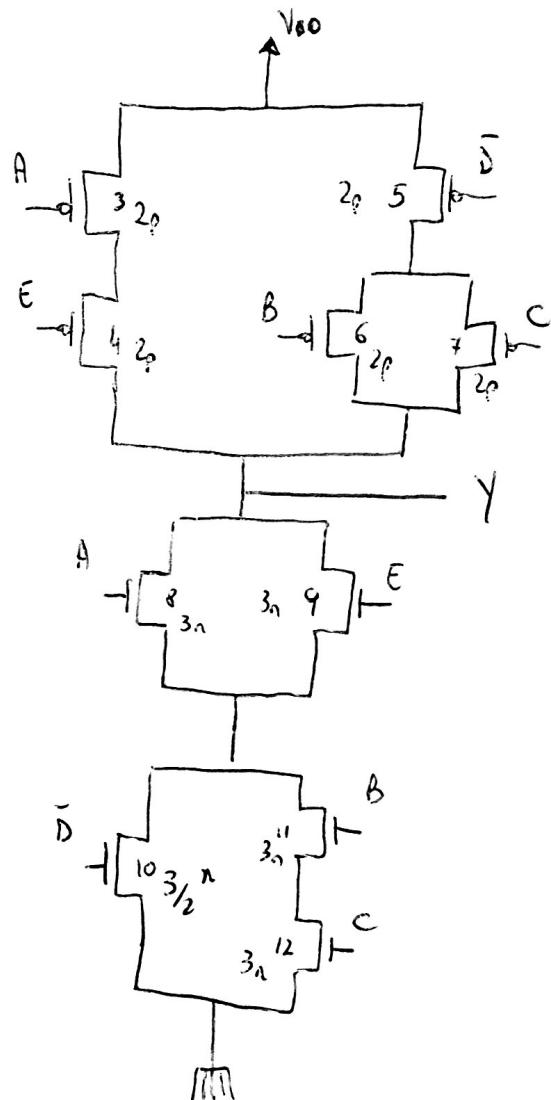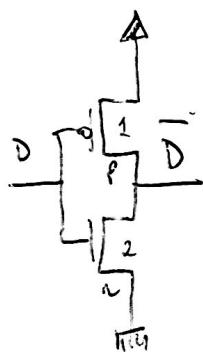
$$Y = \bar{A}\bar{E} + D(\bar{B} + \bar{C})$$



• INVERTER & BASE

$$\left(\frac{W}{L} \right)_1 = P = 5$$

$$\left(\frac{W}{L} \right)_2 = N = 2$$

• PUN

- WORST CASE : $Q_3, Q_4 \circ Q_5, Q_6 \circ Q_5, Q_7$

$$\binom{W}{L}_{3,4,5,6,7} = x$$

$$\frac{1}{x} + \frac{1}{x} = \frac{1}{p} \rightarrow \frac{2}{x} = \frac{1}{p} \rightarrow x = 2p = 10$$

• PDN

- WORST CASE : $Q_8, Q_{11}, Q_{12} \circ Q_9, Q_{11}, Q_{12}$

$$\binom{W}{L}_{8,9,11,12} = x$$

$$\frac{1}{x} + \frac{1}{x} + \frac{1}{x} = \frac{1}{n} \rightarrow \frac{3}{x} = \frac{1}{n} \rightarrow x = 3n = 6$$

- WORST CASE ② , $Q_8, Q_{10} \circ Q_9, Q_{10}$

$$\binom{W}{L}_{10} = 4$$

$$\frac{1}{y} + \frac{1}{3n} = \frac{1}{n} \rightarrow \frac{1}{y} = \frac{3-1}{3n} \rightarrow y = \frac{3n}{2}$$

17/02/2014


(1)

ESERCIZIO C)

$$Q=1 \rightarrow D=1\text{Hz}$$

$$U_{C_1} = 0V \quad U_{S_1} = 0V \quad U_{CS_1} = 0V < U_{T_1} = 1V \quad Q_1 = OFF$$
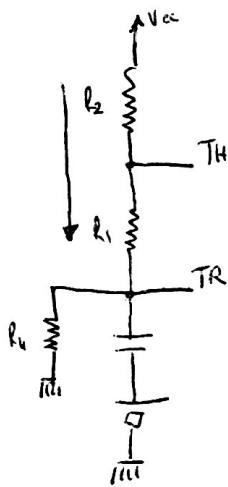
$$U_{C_2} = 0V \quad U_{S_2} = V_{cc} = 5V \quad U_{CS_2} = -5V < U_{T_2} = -1V \quad Q_2 = ON$$



$$\bullet \quad U_i = \frac{1}{3}V_{cc} - U_A = \frac{7}{6}V$$

$$\bullet \quad U_f = V_{cc} \cdot \frac{R_4}{R_1 + R_2 + R_4} - U_A = \frac{29}{22}V$$

$$\bullet \quad V_{com} \approx V_{TH} = \frac{2}{3}V_{cc} = \frac{10}{3}V$$

$$I_2 = \frac{V_{cc} - V_{TH}}{R_2} = \frac{1}{450}A$$

$$V_{IR} = V_{TH} + R_1 I_2 = \frac{35}{12}V$$

$$\bullet \quad V_{com} = V_{IR} - U_A = \frac{29}{12}V$$

VERIFICHE CHE $U_i < V_{com} < U_f \rightarrow OK$

$$T_1 = T_1 \ln \left(\frac{U_i - U_f}{V_{com} - U_f} \right)$$

$$T_1 = R_1 \cdot C = \left[R_1 \parallel (R_1 + R_2) \right] \cdot C = \frac{10000}{11} \cdot C = \frac{1}{11000} \text{ s}$$


$$T_1 = 5,177576769 \cdot 10^{-5} \text{ s}$$

$$Q_1 = 0 \rightarrow D = 0$$

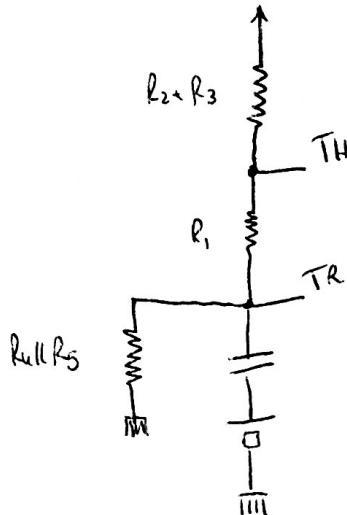(2)

$$U_{E_{S_1}} = U_{CC} \quad U_{S_1} = 0V \quad U_{E_{S_1}} = U_{CC} - 5V > V_{TH} + 1V \quad Q_1 \text{ ON}$$

$$U_{E_{S_2}} = U_{CC} \quad U_{S_2} = U_{CC} = 5V \quad U_{E_{S_2}} = 0V > V_T = -1V \quad Q_2 \text{ OFF}$$



$$\cdot I_i = \frac{29}{12} V$$

$$\cdot U_{COM} = \frac{7}{6} V$$

$$\cdot U_f = U_{CC} \cdot \frac{R_1(R_2+R_3)}{R_1+R_2+R_3+R_1R_2R_3} - V_A = -\frac{16}{53} V$$

VERIFICO che $I_i > U_{COM} > U_f \rightarrow OK$

$$T_2 = T_2 \ln \left(\frac{U_i - U_f}{U_{COM} - U_f} \right)$$


$$T_2 = R_{V_2} \cdot C = \left[(R_{ULLS}) \parallel (R_1 + R_2 + R_3) \right] C = \frac{5000}{53} \cdot C = \frac{1}{106000} \text{ s}$$

$$T_2 = 5.923356511 \cdot 10^{-6} \text{ s}$$

$$T = T_1 + T_2 = 5.76991062 \cdot 10^{-5} \text{ s}$$

$$f = \frac{1}{T} = 17331.2916 \text{ Hz}$$

28/06/2013

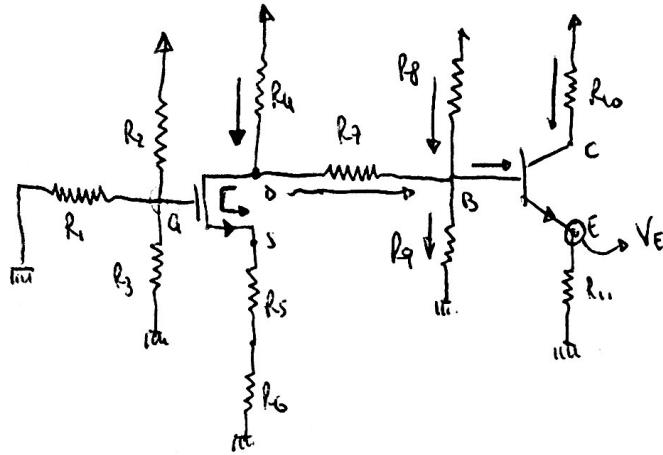

- $I_E = \frac{V_E}{R_{E1}} = 2 \text{ mA}$

- IPOTIZZATO Z.A.D $\rightarrow I_C \gg I_B \Rightarrow I_C \approx I_E = 2 \text{ mA}$

- $V_{CE} - V_C = R_{10} I_C \rightarrow V_L = V_{CE} - R_{10} I_C = 13 \text{ V}$

VERIFICO ZAD $\rightarrow V_{CE} > V_{CESA} \rightarrow 5 \text{ V} > 0.2 \text{ V}$

- $I_B = \frac{I_C}{h_{FE}} = 6,8965 \mu\text{A}$

- $V_{BE} = U_B - V_E \rightarrow V_B = V_{BE} + V_E = 8.7 \text{ V}$

- $I_S = \frac{V_{CE} - V_B}{R_8} = 0,31 \text{ mA}$

- $I_Q = 0,87 \text{ mA}$

- $I_7 + I_8 = I_9 + I_6 \rightarrow I_7 = I_9 + I_6 - I_S = \frac{411}{725000} \text{ A} \approx 0,56689 \text{ mA}$

- $V_C = V_{CE} \cdot \frac{R_1 || R_3}{R_2 + R_1 || R_3} = 9 \text{ V}$

IPOTIZZATO SATURAZIONE : $V_{ES} = V_T + \sqrt{\frac{I_D}{K}} =$

- $V_S = (R_S + R_6) I_D$

- $V_{ES} = 9 - (R_S + R_6) I_D$

$$I_D = K(9 - (R_S + R_6) I_D - 1)^2 \rightarrow I_D = K(R_S + R_6) I_D^2 - K 16(R_S + R_6) I_D + 64 K$$

$$K(R_S + R_6) I_D^2 - (1 + 16K(R_S + R_6)) I_D + 64K = 0 \rightarrow 250 I_D^2 - 5 I_D + 0,016 = 0$$

$0,016 \text{ A} = 16 \text{ mA}$

$I_S, I_D \leftarrow 16 \text{ mA}$

Adesso avranno varie possibilità:

$$U_{S_1} = 4V \quad U_{S_2} = 16V$$

$$U_{AS_1} = 5V \quad U_{AS_2} = -7V$$

Affinché sia in saturazione occorre che $U_{AS} > V_T \Rightarrow$ scegli $I_D = 6mA$

Adesso che ho scelto $I_D^* = 6mA$, ricavo V_D

$$\bullet I_H = I_D + I_T = 6,566896552 \cdot mA$$

$$\bullet V_D = V_{ce} - R_H I_H = 9,779586207 V \rightarrow \text{VERIFICO } U_{DS} > V_{AS} - V_T \rightarrow 5,779586 V > 4V \text{ OK}$$

$$\bullet R_T = \frac{V_D - V_B}{I_T} = 1904,3795 \Omega$$

PUNTI DI RIFERIMENTO

Q₁:


$$I_D = 6mA \quad U_{DS} = 5,779586207 V \quad g_m = 2k |U_{AS} - V_T| = 2 \frac{mA}{V}$$

Q₂:

$$h_{ie} = 6,8 k\Omega \quad h_{re} = 300 \quad h_{fe} = 290 \quad I_C = 2mA \quad V_{ce} = 5V$$

28/06/2013

(3)

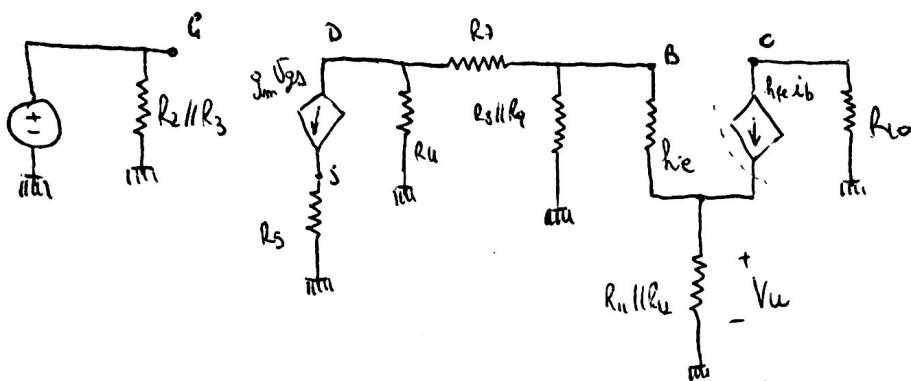

$$\cdot V_u = (h_{fe} + 1) i_b \cdot (R_1 || R_2)$$




$$\cdot i_p = -g_m V_{gs} \cdot \frac{R_4}{R_4 + R_7 + R_p}$$

$$\cdot i_b = i_p \cdot \frac{R_8 || R_9}{R_5 + R_8 || R_9}$$

$$\cdot V_{gs} = V_g - V_D = V_g - g_m V_{gs} R_5$$

$$V_{gs} = \frac{V_g}{1 + g_m R_5}$$

$$\cdot V_g = V_i$$

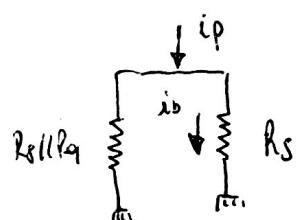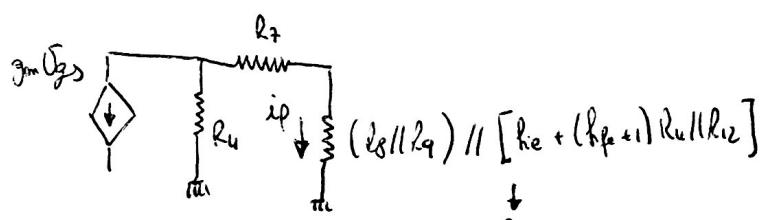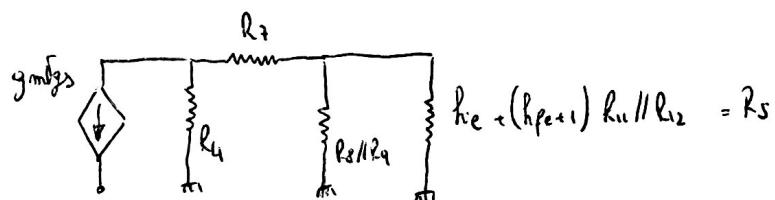

$$\frac{V_u}{V_i} = -(h_{fe} + 1) \frac{(R_1 || R_2)}{R_8 || R_9 + h_e + (h_{fe} + 1) \cdot (R_1 || R_2)} \cdot \frac{\frac{g_m R_4}{R_4 + R_7 + [(R_8 || R_9) // (h_e + (h_{fe} + 1) (R_1 || R_2))]} \cdot \frac{1}{1 + g_m R_5}}{C}$$

$$\boxed{\frac{V_u}{V_i} = -1.99308}$$

28/06/13

ESEMPIO 8)

$$Y = (\bar{A} + \bar{C}\bar{D}) (\bar{B}\bar{C} + D) + (\bar{D} + \bar{E}) (\bar{A}\bar{B} + C) + \bar{D} (\bar{E} + \bar{A})$$


$$Y = (\bar{A} + \bar{C} + \bar{D}) (\bar{B}\bar{C} + D) + \bar{D}\bar{E} \cdot (\bar{A}\bar{B} + C) + \bar{D}\bar{E} + \bar{D}\bar{A}$$

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{D} + \bar{B}\bar{C} + \bar{C}\bar{D} + \bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{D}\bar{E} + C\bar{D}\bar{E} + \bar{D}\bar{E} + \bar{D}\bar{A}$$

$$Y = \bar{D}\bar{E} + \bar{B}\bar{C} + \bar{A} + \bar{C}\bar{D}$$

$$Y = \bar{A} + \bar{C}(\bar{B} + D) + \bar{D}\bar{E}$$

14 mosfet

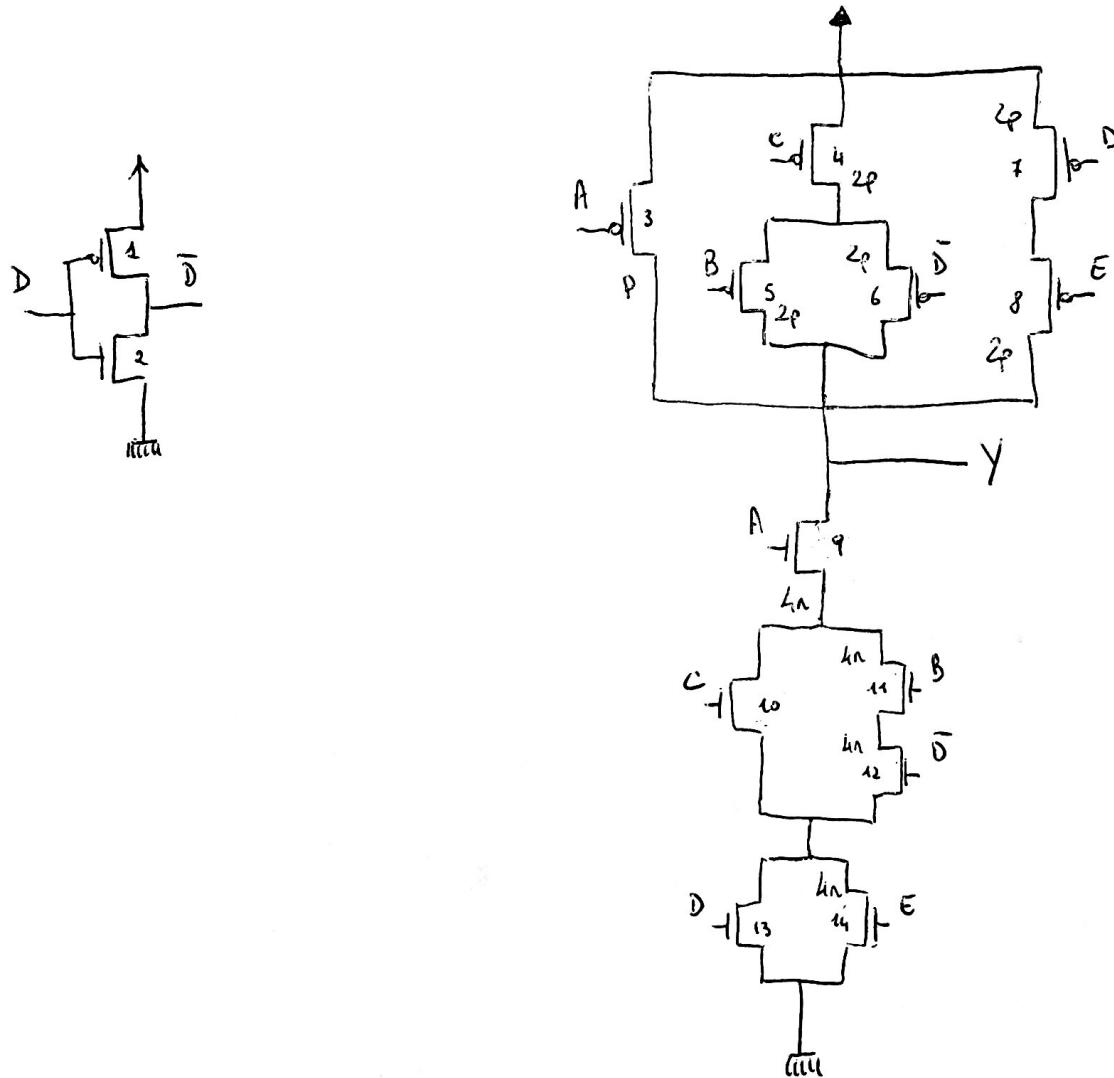

• INVERTER DI BASE

$$\cdot \left(\frac{W}{L} \right)_1 = P = 5$$

$$\cdot \left(\frac{W}{L} \right)_2 = n = 2$$

• PUN

- WORST-CASE $Q_4, Q_5 \circ Q_4, Q_6 \circ Q_7, Q_8$

$$\left(\frac{W}{L}\right)_{4,5,6,7,8} = x$$

$$\frac{1}{x} + \frac{1}{x} = \frac{1}{p} \rightarrow \frac{2}{x} = \frac{1}{p} \rightarrow x = 2p = 10$$

- WORST-CASE 2 Q_3

$$\left(\frac{W}{L}\right)_3 = y \rightarrow \frac{1}{y} = \frac{1}{p} \rightarrow y = p = 5$$

• PDN

WORST-CASE:



$$\left(\frac{W}{L}\right)_{9,10,12,14} = x$$

$$\frac{1}{x} + \frac{1}{x} + \frac{1}{x} + \frac{1}{x} = \frac{1}{n} \rightarrow \frac{4}{x} = \frac{1}{n} \rightarrow x = 4n = 8$$

WORST-CASE ②

Ci sono due percorsi:

$$1) Q_9, Q_{10}, Q_{13}$$

$$2) Q_9, Q_{10}, Q_{14} \text{ e poi } Q_9, Q_{10}, Q_{13}$$

$$1) \left(\frac{W}{L}\right)_{10,13} = y \rightarrow \frac{1}{y} + \frac{1}{y} + \frac{1}{4n} = \frac{1}{n} \rightarrow \frac{2}{y} = \frac{3}{4n} \rightarrow 8n = 3y \Rightarrow y = \frac{8n}{3} = \frac{16}{3}$$

$$2) \left(\frac{W}{L}\right)_{10} = z \rightarrow \frac{1}{z} + \frac{1}{4n} + \frac{1}{4n} = \frac{1}{n} \rightarrow \frac{1}{z} = \frac{2}{4n} \rightarrow z = 2n = 4$$

$$\left(\frac{W}{L}\right)_{13} = k \rightarrow \frac{1}{k} + \frac{1}{2n} + \frac{1}{4n} = \frac{1}{n} \rightarrow \frac{1}{k} = \frac{4-1-2}{4n} \rightarrow k = 4n = 8$$

SCELGO IL PERCORSO AD AREA MINIMA

$$1) \frac{8n}{3} + \frac{8n}{3} = \frac{16}{3} + \frac{16}{3} = \frac{32}{3} \approx 10,67 \rightarrow \text{SCELGO QUESTO}$$

$$2) 4n + 2n = 6n = 12$$


28/06/13

①

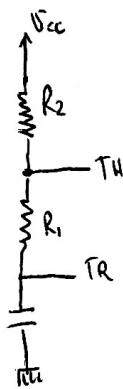EJERCICIO C)

$$Q=1 \rightarrow D=1\text{Hz}$$

- $V_{GS_1} = 0 \quad V_{DS_1} = 0V \quad V_{GS_2} = 0V < V_T = 1V \quad Q_1 = OFF$
- $V_{GS_2} = 0 \quad V_{DS_2} = V_{DD} \quad V_{DS_2} = -5V < V_T = -1V \quad Q_2 = ON$



$$\boxed{\cdot V_i = \frac{1}{3} V_{DD} = \frac{5}{3} V}$$

$$\boxed{\cdot V_f = V_{DD} = 5V}$$

$$\cdot V_{GS_{min}} \approx V_{TH} = \frac{2}{3} V_{DD}$$

$$I = \frac{V_{DD} - V_{TH}}{R_2} = \frac{1}{1200} A$$

$$\boxed{\cdot V_{DS_{min}} = V_{TH} - R_L I = \frac{5}{2} V = 2,5 V}$$

$$\cdot \text{VERIFICO } V_i < V_{GS_{min}} < V_f \rightarrow OK$$

$$T_1 = T_1 \ln \left(\frac{V_i - V_f}{V_{GS_{min}} - V_f} \right)$$

$$T_1 = [R_1 + R_2] \cdot C = [3000 \cdot C] = 3 \cdot 10^{-4} s$$


$$T_1 = 8,630462176 \cdot 10^{-5} s$$

$$Q = 0 \rightarrow D = 0$$

$$\begin{aligned} \cdot U_{C_{S_1}} &= V_{CC} & U_{S_1} &= 0V & U_{C_{S_1}} = V_{CC} = 5V & > U_{T_1} = 1V \\ \cdot U_{C_{S_2}} &= V_{CC} & U_{S_2} &= V_{CC} & U_{C_{S_2}} = 0V & > U_{T_2} = -1V \end{aligned}$$

Q_1 ON

Q_2 OFF

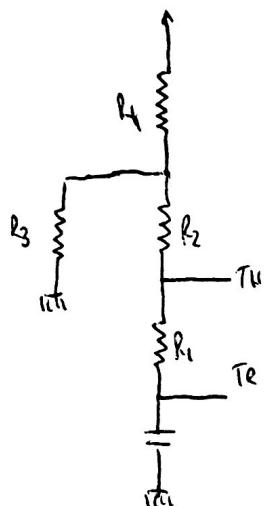

$$\cdot V_i = 2,5 \text{ V}$$

$$\cdot V_{com} = \frac{5}{3} \text{ V}$$

$$\cdot V_f = V_{CC} \cdot \frac{R_3}{R_3 + R_L} = \frac{1}{2} \text{ V}$$

$$\bullet \text{VERIFICO CHE } V_i \gg V_{com} > V_f \rightarrow \text{OK}$$

$$T_2 = T_1 \ln \left(\frac{V_i - V_f}{V_{com} - V_f} \right)$$

$$T_2 = R_{V_2} \cdot C = [R_1 + R_2 + R_3 / (R_L)] \cdot C = 3450 \cdot C = 3,45 \cdot 10^{-4} \text{ s}$$

$$T_2 = 1,859537928 \cdot 10^{-4}$$

$$T = T_1 + T_2 = 2,722584145 \cdot 10^{-4} \text{ s}$$

$$\boxed{f = \frac{1}{T} = 3672,98106 \text{ Hz}}$$


28/01/14

(1)

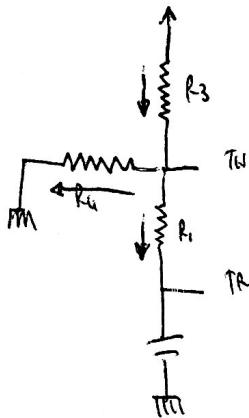ESERCIZIO c)

$$Q_1 \rightarrow D = \text{H2}$$

$$V_{A_1} = V_{CC} \quad U_{S_1} = V_{CC} \quad U_{DS_1} = 0V > U_{T_1} = -1V \quad Q_1 = \text{OFF}$$



$$\cdot V_i = \frac{1}{3} V_u = \frac{5}{3} V$$

$$\cdot V_f = V_{CC} \cdot \frac{R_u}{R_3 + R_u} = 4V$$

$$\cdot V_{\text{comm}} \quad \text{et} \quad V_{TH} = \frac{2}{3} V_u = \frac{10}{3} V$$

$$I_3 = \frac{V_{CC} - V_{TH}}{R_3} = \frac{1}{600} A \quad I_u = \frac{V_{TH}}{R_u} = \frac{1}{1200} A$$

$$I_1 = I_3 - I_u = \frac{1}{1200} A$$

$$\cdot V_{\text{comm}} = V_{TH} - R_1 I_1 = \frac{5}{2} V$$

VERIFICO CHE: $V_i > V_{\text{comm}} > V_f \rightarrow \text{OK}$


$$T_1 = T_1 \ln \left(\frac{V_i - V_f}{V_{\text{comm}} - V_f} \right)$$

$$T_1 = R_{V_1} \cdot C = [R_1 + R_3 // R_u] \cdot C = 1800 \cdot C = \frac{9}{5000} A$$

$$T_1 = 7,952989561 \cdot 10^{-4} A$$

$$Q = 0 \rightarrow D = 0$$
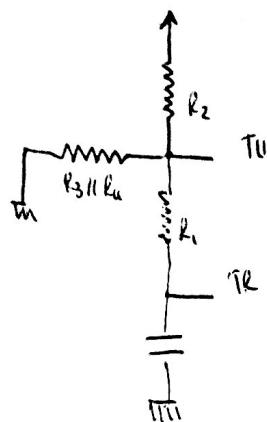
$$U_{A_1} = 0 \quad U_{S_1} = V_{cc} \quad U_{cas_1} = -V_{cc} = -5V \quad \angle U_{r_1} = -1V \quad \rightarrow Q_1 = ON$$



$$U_i = \frac{5}{2} V$$

$$U_{cas_1} = \frac{5}{3} V$$

$$U_f = V_{cc} \cdot \frac{R_3 // R_4}{R_2 + R_3 // R_4} = \frac{10}{17} V$$

VERIFICO CHE $U_i > U_{cas_1} > U_f \rightarrow OK$

$$T_2 = T_2 \ln \left(\frac{U_i - U_f}{U_{cas_1} - U_f} \right)$$


$$T_2 = R_{B2} \cdot C = [R_1 + R_2 // R_3 // R_4] \cdot C = \frac{29000}{17} \cdot C = \frac{29}{17000} \text{ s}$$

$$T_2 = 9.766503877 \cdot 10^{-4} \text{ s}$$

$$T = T_1 + T_2 = 1.771949362 \cdot 10^{-3} \text{ s}$$

$$f = \frac{1}{T} = 564,35 \text{ Hz}$$

EJERCICIO A)

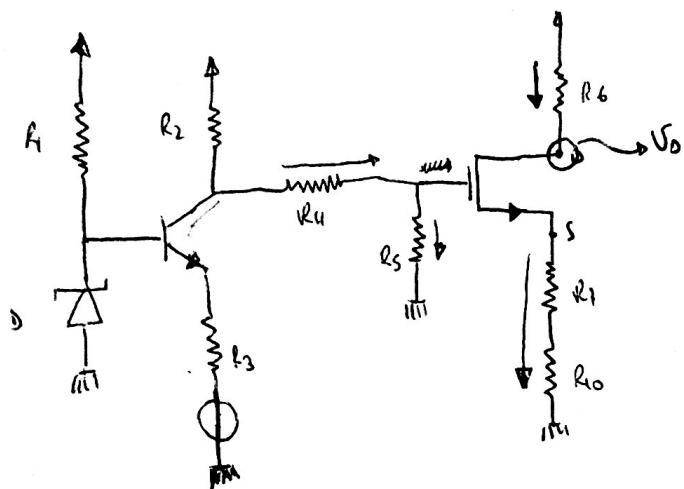

$$\cdot I_0 = \frac{V_{cc} - V_0}{R_6} = 2 \text{ mA}$$

$$\cdot I_a = 0 \rightarrow I_s = I_0 = 2 \text{ mA}$$

$$\cdot V_S = (R_1 + R_0) I_s = 6 \text{ V}$$

PIOTIZO SATURACIONE $\bar{V}_{DS} = V_t + \sqrt{\frac{I_D}{K}} = 3 \text{ V}$

$$\cdot V_a = V_{DS} + V_S = 7 \text{ V}$$

$$\cdot I_S = \frac{V_E}{R_S} = 1 \text{ mA}$$

VERIFICO ZATUZIONE $\bar{V}_{DS} > V_{DS} - V_T \rightarrow 5 \text{ V} > 2 \text{ V} \rightarrow \text{OK}$

PIOTIZO ZENER IN BREAKDOWN $\rightarrow V_B = V_t$

$$\cdot I_B = \frac{V_{cc} - V_B}{R_1} = 4.03 \text{ mA}$$

PIOTIZO Q. ZAD $\Rightarrow I_C \gg I_B \Rightarrow I_C = I_B$

$$\cdot V_{BE} = V_B - V_S \Rightarrow V_B = V_B - V_{BE} = 6 \text{ V}$$

$$\cdot I_E = \frac{V_E}{R_3} = 2 \text{ mA}$$

~~$I_B = I_C = 6.8965 \mu\text{A}$~~

~~$I_E = I_C =$~~

$$I_C = V_a + R_u I_u = V_a + R_u (I_2 - I_c) = V_a + R_u \frac{V_{cc} - V_c}{R_2} - R_u I_E = V_a + R_u \frac{V_{cc}}{R_2} - \frac{R_u}{R_2} V_c - R_u I_E$$

$$\begin{aligned} \text{• } V_{\text{B}} &= \frac{V_{\text{A}} + R_{\text{L}} V_{\text{A}} - R_{\text{L}} I_{\text{C}}}{R_2} \\ \text{• } V_{\text{O}} &= \left(\frac{V_{\text{A}} + R_{\text{L}} V_{\text{A}} - R_{\text{L}} I_{\text{C}}}{R_2} \right) \left(1 + \frac{R_{\text{L}}}{R_2} \right)^{-1} \\ \text{• } I_{\text{C}} &\rightarrow (R_{\text{L}} + R_{\text{S}}) I_{\text{S}} \\ \text{• } V_{\text{C}} &= V_{\text{A}} - R_{\text{L}} I_{\text{C}} \\ \text{• } I_{\text{B}} &= \end{aligned}$$

$$\text{• } I_{\text{L}} = I_{\text{C}} + I_{\text{S}} = 3 \text{ mA}$$

$$\text{• } V_{\text{C}}: V_{\text{A}} - R_{\text{L}} I_{\text{L}} = 9 \text{ V}$$

~~VERIFICO~~ → A.D. → $V_{\text{A}} > V_{\text{C}_{\text{SAT}}} \rightarrow 5 \text{ V} > 0.2 \text{ V} \rightarrow \text{OK}$

$$\text{• } I_{\text{B}} = \frac{I_{\text{C}}}{h_{\text{FE}}} = 6.8965 \mu\text{A}$$

$$\text{• } I_{\text{L}} = I_{\text{C}} - I_{\text{B}} = 4.0236 \text{ mA}$$

VERIFICO IPRESI SUL GENERATOR $I_t > 0 \rightarrow \text{OK}$

$$\rightarrow R_{\text{L}} = \frac{V_{\text{A}} - V_{\text{C}}}{I_{\text{S}}} = 2000 \Omega$$

QUNTI DI LAVORO

Q₁:


$$h_{\text{FE}} = 300 \quad h_{\text{FE}} = 280 \quad h_{\text{E}} = 6.8 \text{ k}\Omega \quad I_{\text{C}} = 2 \text{ mA} \quad V_{\text{A}} = 5 \text{ V}$$

Q₂:

$$I_{\text{D}} = 2 \text{ mA} \quad U_{\text{DS}} = 5 \text{ V} \quad g_{\text{m}} = 2k(V_{\text{GS}} - V_{\text{T}}) = 2 \frac{\text{mA}}{\text{V}}$$

D:
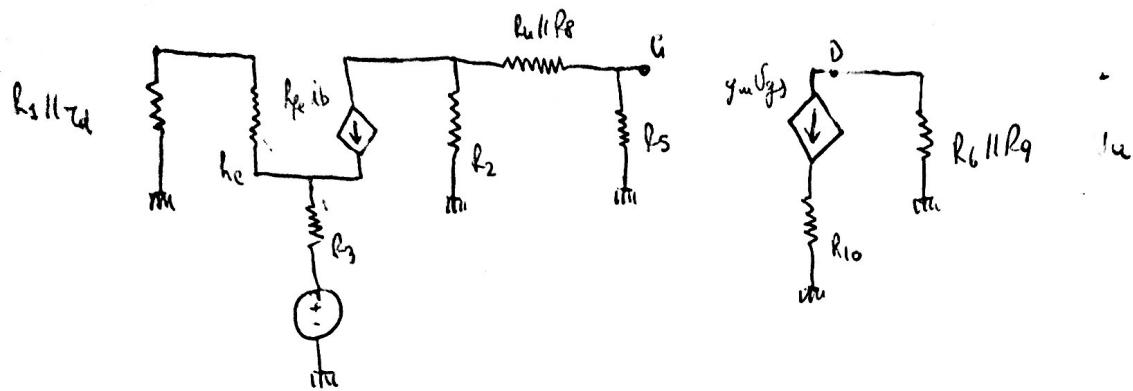
$$r_{\text{d}} = \frac{U_{\text{F}}}{I_{\text{D}}} = 6.462185767 \text{ V}$$




$$\cdot V_u = -g_m V_{DS} (R_D || R_S)$$

$$U_{gs} = U_g - U_A = U_g - g_m U_{gs} R_{lo} \Rightarrow U_{gs} = \frac{U_g}{1 + g_m R_{lo}}$$

$$\bullet \quad \text{Jg} = - h_{pe} i_b \cdot \frac{R_2 \cdot R_5}{R_2 + R_{11} \| R_8 + R_5}$$

$$\cdot i_b(h_{fe}+1) = \frac{U_i}{R_1 || R_d + R_e + (h_{fe}+1)R_3}$$

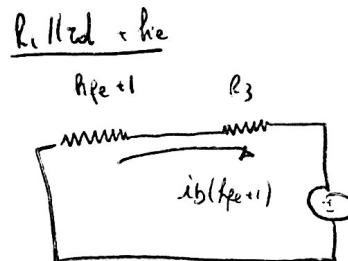

$$\frac{V_{\text{in}}}{V_i} = - \frac{g_m R_2 (f_T || f_B)}{1 + g_m R_2} \cdot \frac{\frac{f_T}{R_2} \cdot R_2 \cdot R_5}{R_2 + f_T || f_B + R_5} \cdot \frac{1}{R_1 || r_d + f_T + (f_T + 1) R_3} = \boxed{-6,29649}$$


13/02/2012

(SCHALTUNG C)

Folger: 1:

$$Q_1 = 1 \rightarrow D = 1 \text{ Hz}$$

- $V_{C_4} = V_{CC}$ $V_{S_4} = 0$ $V_{AS_4} = V_{CC} = 5V > V_{T_H} = 2V$ $Q_4 \text{ ON}$ $\rightarrow V_{D_4} = 0 = V_{D_3}$
- $V_{G_2} = 0V$ $V_{S_2} = V_{CC}$ $V_{AS_2} = -V_{CC} = -5V < V_{T_2} = -2V$ $Q_2 \text{ ON}$ $\rightarrow V_{D_2} = V_{CC} = V_{G_3}$
- $V_{G_3} = V_{CC}$ $V_{S_3} = V_{CC}$ $V_{AS_3} = 0 \Leftrightarrow V_{T_3} = -2V$ $Q_3 \text{ OFF}$
- $V_{U_1} = 0$ $V_{S_1} = 0$ $V_{AS_1} = 0 < 2V$ $Q_1 \text{ OFF}$

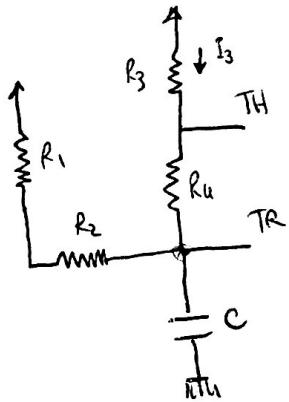

$$V_i = \frac{1}{3} V_{CC} = \frac{5}{3} V$$

$$V_f = V_{CC} = 5V$$

$$\text{Osz. param.: zu calculate } \text{as } V_{IH} = \frac{2}{3} V_{CC} = \frac{10}{3} V$$

$$I_3 = \frac{V_{CC} - V_{IH}}{R_3} = 1,6667 \text{ mA}$$

$$V_{\text{comm}} = V_{IH} - R_u I_3 = 1,9666 \text{ V}$$

$$\text{Verifica: } V_i < V_{\text{comm}} < V_f \rightarrow \text{OK}$$

$$T_1 = \gamma_1 \cdot \ln \left(\frac{V_i - V_f}{V_{\text{comm}} - V_f} \right)$$

$$T_1 = R_{V_1} \cdot C = [(R_3 + R_u) \parallel (R_1 + R_2)] \cdot C = 9.2475 \cdot 10^{-6} \text{ s}$$

$$T_1 = 8.7193 \cdot 10^{-5} \text{ s}$$

Apotesi 2)

(2)


$$Q = 0 \rightarrow I = 0$$

$$\cdot U_{g_2} = 0 \quad U_{S_2} = U_{cc} \quad U_{es_2} = -U_{cc} = -5V < V_{T_2} = -2V \quad Q_2 = ON \quad U_{D_2} = U_{cc} = U_{S_3}$$

$$\cdot U_{g_3} = 0 \quad U_{S_3} = U_{cc} \quad U_{es_3} = -U_{cc} = -5V < V_{T_3} = -2V \quad Q_3 = ON \quad U_{D_3} = U_{cc}$$

$$\cdot U_{g_4} = 0 \quad U_{S_4} = 0 \quad U_{es_4} = 0 < V_{T_4} = 2V \quad Q_4 = OFF$$
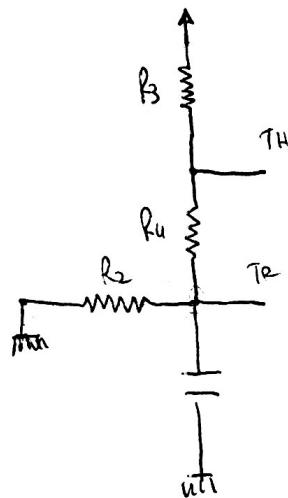
$$\cdot U_{C_1} = U_{cc} \quad U_{S_1} = 0 \quad U_{es_1} - U_{cc} > V_{T_1} = 2V \quad Q_1 = ON$$



$$V_i = 1.9666 \text{ V}$$

$$U_{common} = \frac{5}{3} \text{ V}$$

$$U_f = U_{cc} \cdot \frac{R_2}{R_2 + R_3 + R_u} = 1.36 \text{ V}$$

$$V_i > U_{common} > U_f \rightarrow OK$$

$$T_2 = T_2 \cdot \ln \left(\frac{V_i - U_f}{V_{common} - U_f} \right)$$

$$T_2 = R_{S_2} \cdot C = [(R_3 + R_u) // R_2] \cdot C = 0.49504 \text{ ms}$$

$$T_2 = 337.725 \mu\text{s}$$


$$T = T_1 + T_2 = 626.9396 \mu\text{s}$$

$$f = \frac{1}{T} = 2353.275 \text{ Hz}$$

ESERCIZIO c)

Ipotesi 1:


$$Q=1 \rightarrow D=1\text{Hz}$$

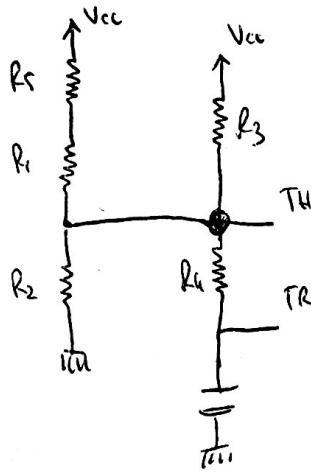

$$V_i = \frac{1}{3} V_{cc} = \frac{5}{3} \text{ V}$$

$$V_f:$$

THEVENIN

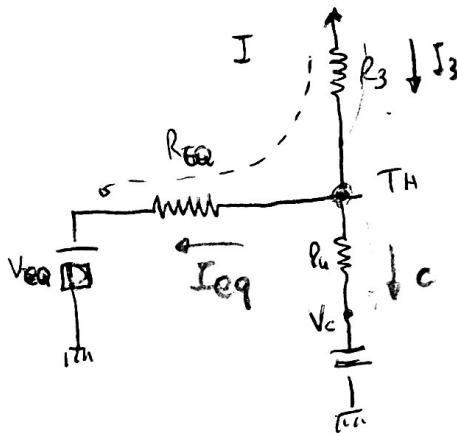

$$V_{EQ} = V_{cc} \cdot \frac{R_2}{R_2 + R_1 + R_S} = 3.1161 \text{ V}$$

$$R_{EQ} = R_2 || (R_1 + R_S) = 328.8951 \Omega$$

$$I = \frac{V_{cc} - V_{EQ}}{R_3 + R_{EQ}} = 2.9303 \cdot 10^{-6} \text{ A}$$

$$V_{tf} = V_{cc} - R_3 I = 3.359 \text{ V}$$

$$\bullet V_{common} \text{ con } V_{TH} = \frac{2}{3} V_{cc} = \frac{10}{3} \text{ V}$$

$$I_3 = \frac{V_{cc} - V_{TH}}{R_3} \quad I_{EQ} = \frac{V_{TH} - V_{EQ}}{R_{EQ}}$$

$$I_C = I_3 - I_{EQ}$$

$$V_{common} = V_{TH} - R_u I_C$$

$$\begin{cases} I_3 = 2.97619 \cdot 10^{-6} \text{ A} \\ I_{EQ} = 2.620757 \cdot 10^{-6} \text{ A} \\ I_C = 3.55632 \cdot 10^{-5} \text{ A} \end{cases}$$

$$\rightarrow V_{common} = 3.134 \text{ V}$$

$$T_1 = T_1 \ln \left(\frac{V_i - V_f}{V_{common} - V_f} \right)$$


$$T_1 = R_u C = \left[R_u + R_3 || R_2 || (R_1 + R_S) \right] C = 3.54033 \text{ ms}$$

$$T_1 = 7.162589 \text{ ms}$$

(2)

Istreak 2:

$$Q = 0 \rightarrow D = 0$$

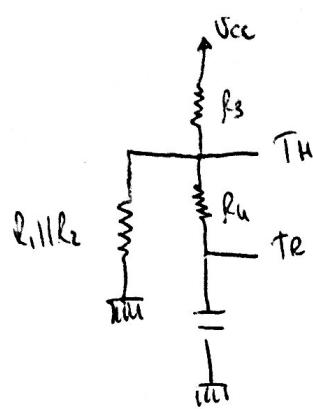

$$V_i = 3,136 \text{ V}$$

$$V_{\text{comm}} = \frac{5}{3} \text{ V}$$

$$V_f = V_{cc} \cdot \frac{R_1 || R_2}{R_3 + R_1 || R_2} = 0.243722 \text{ V}$$

$$T_2 = T_2 \ln \left(\frac{V_i - V_f}{V_{\text{comm}} - V_f} \right) =$$


$$\bar{T}_2 = R_{\text{L}} \cdot C = \left[R_4 + R_3 || (R_1 || R_2) \right] = 3.28886 \text{ ms}$$

$$T_2 = 2.3305 \text{ ms}$$

$$T = T_1 + \bar{T}_2 = 9.473124 \text{ ms}$$

$$f = \frac{1}{T} = 105.5618 \text{ Hz}$$

10/01/2012

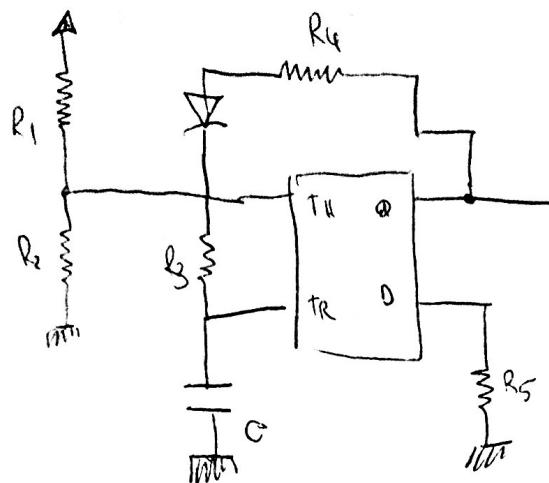


Ipotesi 1:

$$Q=1 \rightarrow D = 1H27$$

\rightarrow Dloss ON
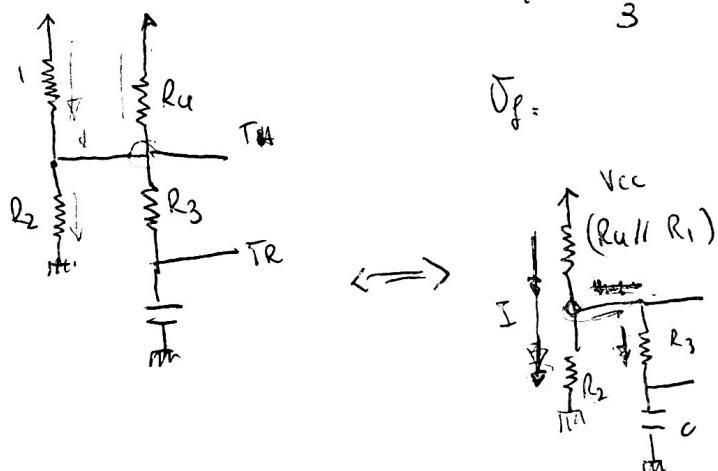
$$I_i = \frac{V_{cc}}{3} = \frac{5}{3} V$$



$$I_f \cdot V_{cc} \cdot \frac{R_2}{R_2 + R_1 \| R_4} = 3.9965 V$$

$$V_{comn} = \alpha V_{TR} = \frac{2}{3} V_{cc}$$

$$I_{1\mu} = \frac{V_{cc} - V_{TR}}{R_4 \| R_1} = 2.7686 \cdot 10^{-3} A$$

$$V_{com} = R_1 V_{TR} - R_3 I_3 = 3.0629 V$$

$$I_2 = \frac{V_{TR}}{R_2} \rightarrow I_3 = I_{1\mu} - I_2 = 1.2335 \cdot 10^{-3} A$$

$$\text{Verifico: } I_i < V_{comn} < V_f \rightarrow \text{OK}$$

- - -


$$T_1 = T_{1\mu} \left(\frac{V_i \cdot V_{com}}{V_{com} \cdot V_f} \right) = 376.07022 \mu s$$

$$T_1 = R_{v1} C = \left[R_3 + (R_1 \| R_4) \parallel R_2 \right] \cdot C = 695.3517 \mu s$$

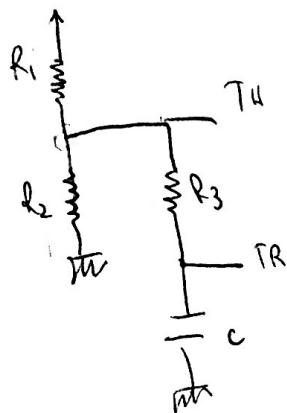(2)

Ipoteg. 2:

$$Q=0 \rightarrow D=0 \rightarrow D \text{ OFF}$$



$$V_i = 3.0619 \text{ V}$$

$$V_{\text{com}} = \frac{5}{3} \text{ V}$$

$$V_f = V_{\text{com}} - \frac{R_2}{R_1+R_2} = 1.610256 \text{ V}$$

$$T_2 = T_2 \ln \left(\frac{V_i - V_f}{V_{\text{com}} - V_f} \right) = 1.877156 \text{ ms}$$

 T_2

$$T_2 = R_2 C = \left[R_3 + R_1 \parallel R_2 \right] = 1799.48718 \Omega$$

$$T = T_1 + T_2 = 2.253226 \text{ ms}$$

$$f = \frac{1}{T} = 443.808 \text{ Hz}$$